



Designed to Help You Boost Your Analog Design Power

Table of Contents

| | | | |
|------------------------------------|-----|-------------------------------------------|-----|
| Welcome to Apex | 585 | The packages..... | 650 |
| Where we live..... | 586 | Linear basics..... | 651 |
| Quality at Apex..... | 587 | Class C outputs..... | 652 |
| DC-DC Converters | 588 | Class AB outputs..... | 654 |
| The packages..... | 589 | Complex construction..... | 656 |
| Linear power delivery..... | 590 | Monolithic types..... | 658 |
| PWM power delivery..... | 591 | Selector guides..... | 659 |
| Basic converter block..... | 592 | Amplifier selection..... | 661 |
| Basic converter operation..... | 593 | Electrical limitations..... | 663 |
| Defining Apex converters..... | 594 | Non-linear model..... | 664 |
| What's inside..... | 595 | Common non-linear cases..... | 665 |
| Shorted output response..... | 596 | False summing node | 668 |
| Ceramic capacitors..... | 598 | Reading the specs..... | 669 |
| Shutdown Plus pin..... | 600 | Common mode voltage..... | 670 |
| DHC 6W singles..... | 601 | Op amp protection | 671 |
| DHC 6W duals..... | 604 | Input protection networks..... | 672 |
| DB 20W family..... | 607 | Gain switching..... | 674 |
| Triplets are coming..... | 610 | To invert or not with I/P protection..... | 676 |
| PWM Amplifiers | 612 | Flyback diodes..... | 677 |
| The packages..... | 613 | Transient voltage protection..... | 678 |
| Linear vs. PWM power delivery..... | 614 | SOA | 679 |
| The H-Bridge..... | 617 | SOA graph..... | 680 |
| Switching concerns..... | 619 | Output transistors..... | 681 |
| Evaluation kits..... | 620 | Load fault to consider..... | 682 |
| What's inside..... | 621 | What's current limit..... | 683 |
| Block diagrams..... | 622 | Thermal modeling..... | 688 |
| Transfer function..... | 626 | Where to set Tj max..... | 689 |
| The integrator..... | 627 | What is the internal power..... | 691 |
| Samples at work..... | 628 | DC vs. AC vs. reactance..... | 693 |
| The frequencies involved..... | 631 | Calculating the power..... | 694 |
| Filter design..... | 632 | When to sweep the frequency..... | 700 |
| Response with real parts..... | 636 | Thermal capacity & averaging..... | 701 |
| Filter termination required..... | 637 | Proper mounting or not..... | 702 |
| What is -3db..... | 638 | Motor reversal..... | 705 |
| Matching networks..... | 640 | Single Supply Operation | 706 |
| Half bridges..... | 643 | Internal limitations..... | 707 |
| Heatsinking PWMs..... | 644 | Basic techniques..... | 708 |
| Selector guide..... | 648 | Taking care of CMV..... | 709 |
| The Apex Linear World | 649 | PA21 is ideal..... | 712 |

| | | | |
|--------------------------------------|-----|---------------------------------------|-----|
| PA21 protection alternatives..... | 713 | Valve control..... | 790 |
| Asymmetrical supplies..... | 714 | Programmable torque drive..... | 791 |
| Basic Stability | 715 | Howland single Vs bridge torquer..... | 792 |
| Eliminate coupling..... | 716 | ATE | 793 |
| Ground loops..... | 717 | Low drift PZT tester..... | 794 |
| Supply wire impedance..... | 718 | Linear high power PPS..... | 799 |
| Supply bypassing..... | 719 | A PWM alternative..... | 800 |
| Output stages vs. stability..... | 720 | Remote sensing..... | 801 |
| Loop Stability | 722 | Driven ground..... | 802 |
| Feedback theory..... | 723 | Very high voltage PPS..... | 803 |
| External phase compensation..... | 725 | High power AC PPS..... | 804 |
| Open, closed and loop gains..... | 726 | Signal Sources | 806 |
| Inductors in the feedback loop..... | 728 | PB58 voltage regulator..... | 807 |
| Capacitive loading..... | 734 | 400Hz servo supply..... | 811 |
| Stability Testing | 746 | Low power telephone ringer..... | 812 |
| Ringing test..... | 747 | High power telephone ringer..... | 813 |
| Peaking test..... | 748 | Thermo-electric cooler..... | 814 |
| High Speed Techniques | 749 | Deflection | 815 |
| Techniques and strays..... | 750 | Magnetic deflection waveforms..... | 816 |
| Slew rate vs. power bandwidth..... | 751 | Basic magnetic deflection..... | 817 |
| Effects of compensation..... | 752 | V-to-I bridge..... | 822 |
| Cable loads..... | 753 | Electrostatic deflection..... | 823 |
| High Power Techniques | 754 | Dynamic focusing..... | 824 |
| This is no laughing matter..... | 755 | PZT Drive | 825 |
| Bridge basics..... | 757 | 860Vp-p single Vs bridge..... | 826 |
| Bridge power calculations..... | 759 | ±1KV bridge..... | 827 |
| A weird & dangerous bridge..... | 760 | Composite amplifier..... | 828 |
| External current buffers..... | 761 | Audio/Noise Cancellation | 837 |
| Parallel operation..... | 765 | Fast and low distortion..... | 838 |
| Parallel and bridge together..... | 769 | Foldover can help..... | 839 |
| Current Outputs | 770 | PWM aircraft audio..... | 840 |
| Inductance concerns..... | 771 | SA51 PWM audio..... | 841 |
| PWM current output..... | 772 | Sonar transducer..... | 842 |
| Op amp current output..... | 773 | Tools for you..... | 843 |
| Howland for grounded loads..... | 774 | Beat the discrete..... | 844 |
| Motion Control | 781 | Top of the line is on line..... | 845 |
| Z-axis position..... | 782 | | |
| Brush motor specifications..... | 783 | | |
| Fitting the op amp to the motor..... | 784 | | |
| Simple speed control..... | 788 | | |
| PWM antenna position | 789 | | |



APEX MICROTECHNOLOGY CORPORATION

DC-DC Converters α PWM Amplifiers α Power Op Amps

Power Integrated Circuits with Technical Support

Since 1981, Apex has been designing and manufacturing hybrid (chip and wire) power amplifiers. Careful attention to process development and control has made Apex the world leader in hybrid power. The products consistently perform per the data sheet. The product line now boasts the highest current, the highest voltage and highest wattage hybrids to be found anywhere in the industry.

The expertise in handling large power levels electrically and thermally has been adapted to high reliability DC-DC converters. Unique construction techniques make these converters especially impervious to demanding environmental conditions. The Apex design philosophy provides converters with no de-rating over their entire operating temperature range.

Pulse Width Modulation (PWM) amplifiers share the same reliability as their linear counterparts but utilize switching technology to greatly extend the delivered power range while keeping wasted heat in the same area as the linears.



The present Apex facility is 55,000 sq. ft. on ten acres zoned such that we can double our size. Current sales are about \$14M and we can do \$25M in this building. Almost half the area and third the cost of the building are clean room related. This class 100,000 clean room keeps the ICs clean.

Apex extends an invitation to you all to visit us and take a tour of our home to see first hand how we design and manufacture the world's best power integrated circuits.



- Total Quality Management
- Certified Mil-Std-1772 in 1989
- Certified ISO9001 in 1994

Sigma Plus has led to consistent increases in quality and performance for Apex and our customers. *Sigma Plus*, our Total Quality Management program, continues to produce measurable quality improvements, a culture based on teamwork, and increased value for our customers.

In alignment with *Sigma Plus*, we have instituted training and development in the fundamentals of our business, further supporting Apex teams with the tools they need to perform at high productivity and quality levels. With a firm foundation of *Sigma Plus* quality tools that solve the “how” of continuous improvement, team members are now learning the “why” with Open Book Management. As a result, Apex teams are gaining greater understanding of their personal impact on organizational systems and how they can directly improve organizational performance. By giving team members a stake in the outcome, they gain personal satisfaction and ownership of the products and services they provide to you, our customers.


We will continue to improve our systems and processes to exceed our customers’ expectations. Feedback systems that identify internal and external customers’ needs and expectations keep Team Apex focused on customer value. Team members have increased their job skills and have become functionally cross-trained to quickly adapt to changes that anticipate customer needs.

DC-DC Converters

Transform


Isolate

Regulate

 

As you can see, these welded all steel packages are *rugged*. This is the first indicator that these converters are no ordinary breed. They are designed from top to bottom to give reliable performance in the most demanding environments.


LINEAR POWER DELIVERY

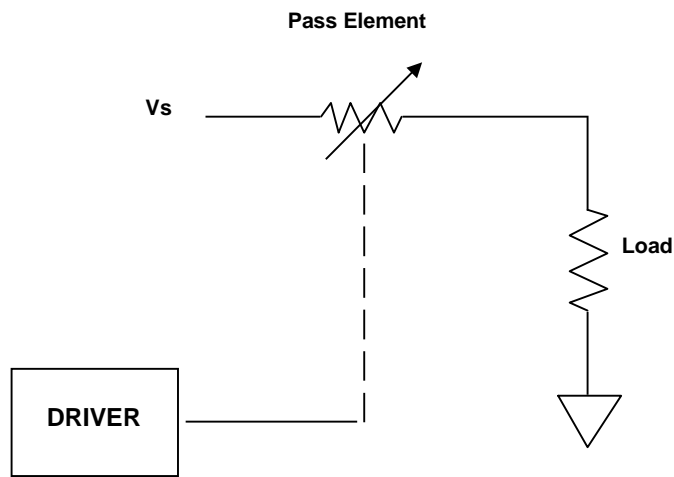

The most popular DC-DC converter application vividly demonstrates why the DC-DC converter is the only reasonable choice compared to a linear regulator. This function is providing 5V for logic or computer circuits from a 28V bus.


Let us assume the load requires 1A @ 5V or 5W. A linear regulator would pass the 1A while having 23V across it, thus wasting 23W. With an input power of 28W, efficiency is less than 18%! Unless the application also just happens to need a 23W heater, you pay twice; once to generate the 23W and again to get rid of it. Typical efficiencies of these DC-DC converters reduce this waste heat by better than an order of magnitude.

PWM POWER DELIVERY

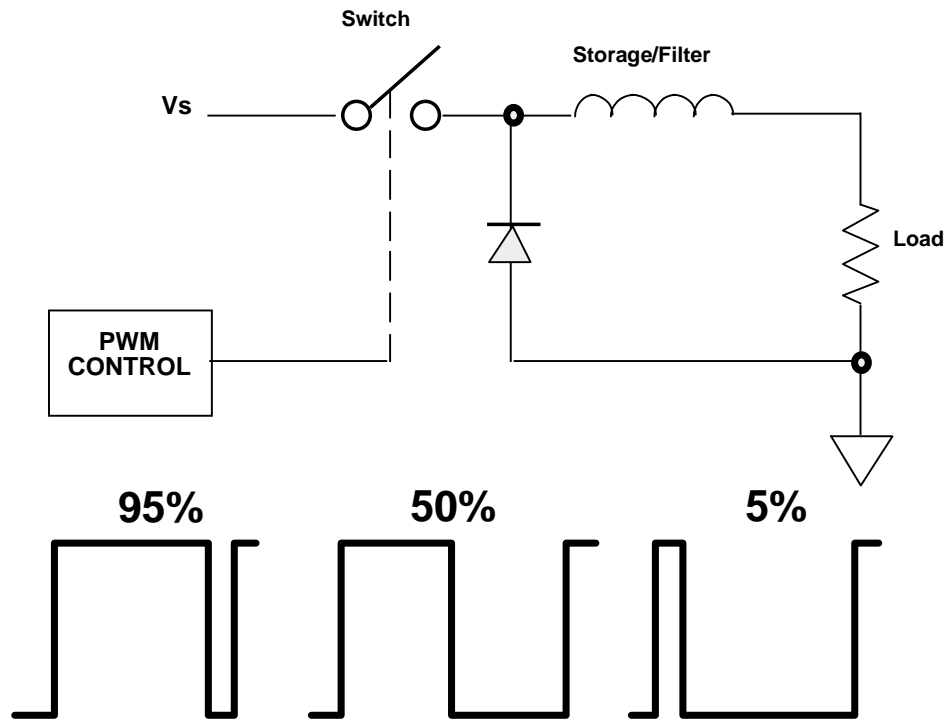

These figures illustrate the most basic pwm operation. The PWM control block converts the DC input into a variable duty cycle switched drive signal. If high output is commanded, the switch is held on most of the period. When the switch is on, losses are simply a factor of the on resistance of the switch plus the inductor resistance. As less output is commanded the duty cycle or percent of on time is reduced. When the switch is off, losses now include heat generated in the flyback diode. At most practical supply voltages this diode loss is still small because the diode conducts only a portion of the time, and voltage drop is a small fraction of the supply voltage.

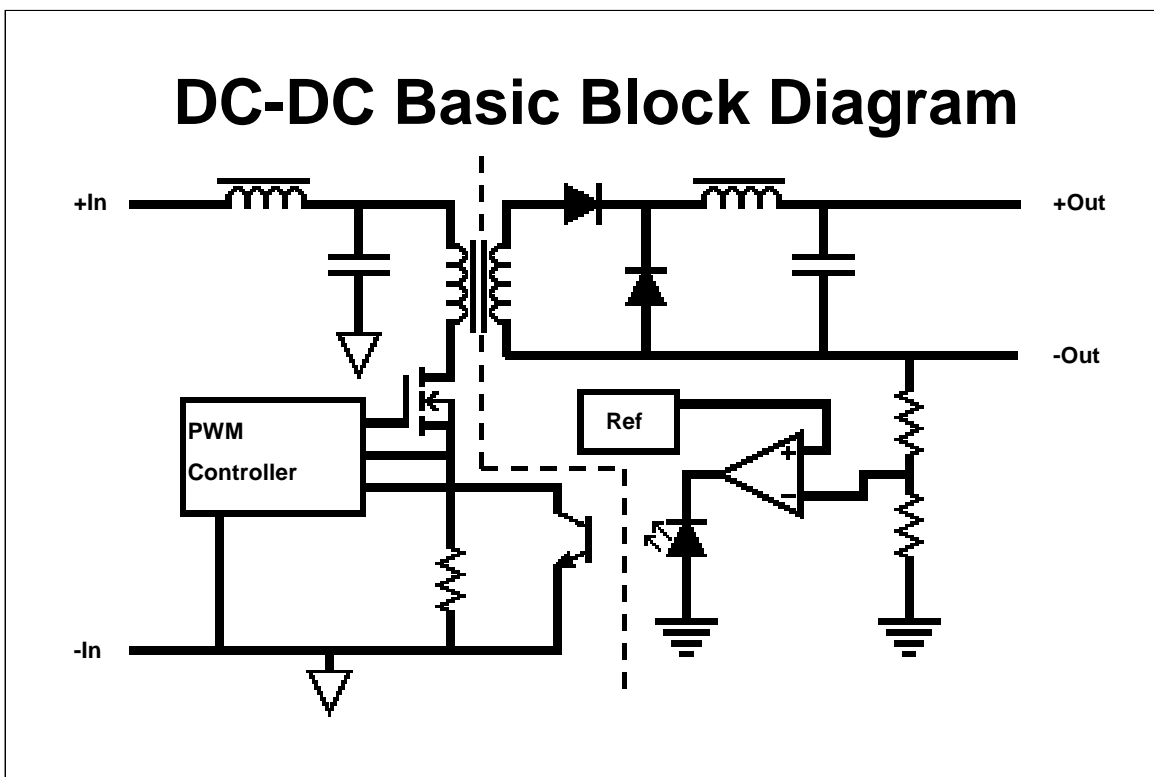
The job of the inductor is both storing energy and of filtering. In this manner the load sees very little of the switching frequency, but responds to the regulator loop whose frequencies are significantly below the switching frequency.



The basic blocks of the DC-DC converter consist of input and output filters, the PWM controller, a reference, an error amplifier, power isolation with rectification and error feedback isolation. The input filter reduces the effect of internal current pulses on the supply bus. Depending on the application, additional external filtering may be required. The output filter keeps most of the voltage pulses inside the converter. The need for dedicated external filter components right at the converter is unusual because there are almost always supply bypass capacitors local to the powered circuitry.

The error amplifier integrates the difference between the output voltage and the reference voltage and signals the PWM controller to lengthen the pulse if the output is low or shorten the pulse if the output is high. While this example shows optical isolation of the feedback signal, Apex also uses a time based transformer isolation technique. The optical technique requires fewer parts but great care must be taken in the design of the dynamic range to avoid saturation or starvation over temperature and operating life.

Note that this diagram uses two types of “ground” symbols, but an isolation barrier separates each type. Although cluttered, it would have been more correct to draw this diagram without ground symbols at all. Each half of this device is a floating two terminal circuit where either terminal could be “grounded” to local external circuits. It would be possible to operate on a negative input voltage or to output a negative voltage.

 

Here's the challenge of setting up the pulse width modulator: Get enough dynamic range to deliver the specified output (while maintaining regulation) even though three variables are moving over wide ranges.

If output current remains constant, the average energy into the filter inductor must remain constant. As input voltage rises, the energy delivered to the inductor in a given time increases. Inductor current is proportional to time. The controller must shorten the pulse width to close the regulation loop.

If the input voltage is constant but output current decreases, less energy must be delivered to the inductor. Again, the only variable the controller has to work with is pulse width - shorter again.

Even if input and output are rock solid, there are changes of internal losses due to temperature variations. FET on resistance, diode forward drops, copper losses, and core losses are the main factors changing over temperature. Even though some of these tend to cancel, losses typically increase a little at -55°C and increase even more at $+125^{\circ}\text{C}$. Either case calls for increasing the pulse width to maintain regulation.

APEX DC-DC Converters

- 28V input
- Hi-Rel design and construction
- No derating over specified temperature
- Fault tolerant with fault flag
- 500V isolation
- 100% temperature tested
- Programmable Vstart and remote S/D
- Hermetic packages


The classic 28V bus is usually anything but 28V. That's why the high-to-low input range of Apex converters spans 2.5:1 to over 4.5:1. Transient protection levels go even higher than that.

Some manufacturers rate the wattage of their converters based on their capability within a moderate temperature range and wait for you to ask about derating if you need to run them at higher temperatures. Not so with Apex converters: The temperature range is on the data sheet and the converter delivers full power over the entire range. And the majority of Apex models cover -55°C to +125°C!

Apex converters are not merely characterized over temperature, but are 100% temperature tested- -like a hi-rel product should be.

DC/DC CONVERTERS

 - ① Surface Mount Magnetics
- ② 100% Ceramic Capacitors
- ③ Reflow Soldered Components
- ④ Welded Package,
Hermetically Sealed
- ⑤ Low Thermal Resistance,
Ceramic on Solid Steel



HIGH RELIABILITY BUILT IN, APEX'S LIFETIME WARRANTY

We know our customers really put our converters to the test. That's why Apex's DHC2800 and DB2800 Series DC-DC Converters utilize all ceramic capacitors and surface mount magnetics to provide hybrid reliability across the full military temperature range and to 5000g of acceleration. The built-in ruggedness of Apex DC-DC Converters allows Apex to offer the only lifetime product warranty in the industry.

All Apex DC-DC Converter products are sold in single unit quantities to assist your circuit design evaluation. Our Evaluation Orders program even allows you to purchase up to three DC-DC Converter units and should they not meet your design needs, and they have not been damaged or soldered, you can return them to Apex within 30 days of the invoice date to receive a full credit.

PRODUCT DESIGN HIGHLIGHTS

- Commercial grade parts designed for military ruggedness
- Withstands 5000g acceleration
- 100% ceramic capacitors offer higher reliability
- DHC Series: Input meets MIL-STD-704A requirements (80V transient play through)
- DB Series: Input meets MIL-STD-704D requirements (80V transient survival)
- -55°C to +125°C full power operation
- Fault Tolerant
- Full short circuit protection
- Fully isolated
- Output voltage adjustment standard
- Remote shutdown provides on/off capabilities


Upon a Shorted Output you would:

- A. Run hot with current $> 100\%$
- or
- B. Run cool with low duty cycle

With power devices, deciding what to do about the dreaded short circuit on the output is always interesting. Do you have the space and the cooling capacity to simply set a current limit safely above the required output power level and let the unit run hot? While quite rare, there are a few applications where a load fault is so unlikely that no safety provisions are required for the power stage.

With low duty cycle fault response, Apex DC-DC converters bring a new level of confidence. Imagine watching the input current to a converter driving near full load. It's time to run the load fault test- -the current meter DROPS! The first time you see this, it looks *wrong*. But it isn't wrong, its low duty cycle fault response at work.

Low Duty Cycle Fault Response

 

With a normal load impedance corresponding to a near full load, we see moderate width pulses and the average current as expected for the efficiency of the converter. While it is not graphed, the error feedback signal is also at a moderate level.

When the load impedance plunges to zero or near zero, the error feedback signal swings to its maximum. It actually calls for a pulse width longer than the controller is capable of producing. The low duty cycle circuit picks up on this allowing one pulse out, but then it puts the converter to sleep for about 10 times the maximum pulse width. Even though internal heat generation during this big pulse is higher than before the fault condition, reducing the duty cycle to about 10% makes the average heat generation less than when running at full load. This low average power mode of operation is continued as long as the fault is present. Normal operation resumes when the fault is cleared.

CERAMIC CAPS ONLY

- Improved hi-temp reliability
- Improved time and temperature stability
- Smaller values than tantalum/electrolytic
- Added application flexibility

Electrolytic and tantalum capacitors are known to excel at packing lots of capacitance in a small space. Like most other things in our world, there are trade-offs required. Apex designers kept high reliability as their prime design goal while making component selections.

Electrolytic and especially tantalum capacitors simply can't come close to matching the reliability performance of ceramic in the upper areas of the full military temperature range. These high density capacitors excel in temperatures suitable for habitation, but Apex converters go a lot further.

Ceramic capacitors also exhibit a lower temperature coefficient and are more stable over time. This makes temperature characterization of your circuit easier because the dynamic performance of the converter is more stable over temperature.


Now for the trade-off part: Ceramic capacitors can't even think of the volumetric efficiencies of electrolytic or tantalum types, so capacitor values are limited to fit in the hybrid package. It turns out though that these smaller values yield flexibility akin to an op amp featuring external compensation. Dynamic or transient performance can be tailored to fit the application.

Response Curves-Your Choice

No Cap

100uF

1000uF

 

DHC2805S Load Transient Response Curves


The choice really is yours. Is your application fast and sensitive to 0.75 peak deviations from 5V? Or is it a slower system which is more sensitive to longer term 10mV deviations; maybe where the 5V is used as an analog reference?

Please note the time scale changes between the graphs. In applications where the output is used as an analog reference voltage, using no external capacitor may be the way to go. Settling time in this graph is under 100µs. Even though the peak deviation is high, a system running at 100Hz will likely never see the short transient.

For faster systems, the use of an external capacitor will greatly reduce the peak deviation, but with a settling time in the millisecond range.

Shutdown+ Pin

 - Shutdown with an open collector
- Program Vstart with a resistor
- Monitor faults with a J-FET



Would you like to gain some control over turn-on sequencing of your system? The Shutdown+ pin has three functions which can all be used in all combinations. The first function is that of programming a low voltage start-up point. Installing only one resistor to ground will set the level according to:

$$R = 210K/(V_{start}-9.5)$$

This means with an open or several hundred Kohms, start-up is about 9.5V. The 9.5V level is increased by $210K/R$, so 21Kohms yields about 19.5V start-up.

The second function is really a digital over-ride of the analog function above. Use an open collector transistor to ground the pin and the function is now a remote shutdown.

Would you like to know when something is putting your converter in a hurt? The Shutdown+ pin is also an output function: A load fault condition will cause a negative pulse on the pin from above 10V to below 1V for around 100ms for each power pulse in the low duty cycle fault response mode of operation.

DHC2800S Series

| | | | |
|----------|--------|------|-------|
| DHC2803S | 12-50V | 5W | 1.52A |
| | 13-50V | 6W | 1.82A |
| DHC2805S | 12-50V | 6W | 1.2A |
| DHC2812S | 11-50V | 5W | .417A |
| | 16-40V | 5.4W | .45A |
| DHC2815S | 11-50V | 5W | .333A |
| | 16-40V | 5.4W | .36A |
| DHW2805S | 16-40V | 7.5W | 1.5A |

This is the smallest series of converters from Apex (electrical and mechanical). They fit in an industry standard footprint with the exception that an NC pin is used to implement the Adjust/Comp function. If an existing application makes no connection to the NC pin, the DHC2800 series will drop in. These models are also available with an NC option.

The DHC2803S can be extended to 6W if minimum input is raised to 13V.


The DHW2805S is the same basic converter optimized for greater power at a reduced input voltage range.

Data as of July 1999.

DHC2800S Special Features

- MHE2800/ASA2800 Compatible
- -55°C to +125°C temperature range
- Mil-Std-704 (80V survive only)
 - DHC2805S plays thru 80V
- +/-10% Adjust range
- 1 inch square package

DHC2800S Block Diagram

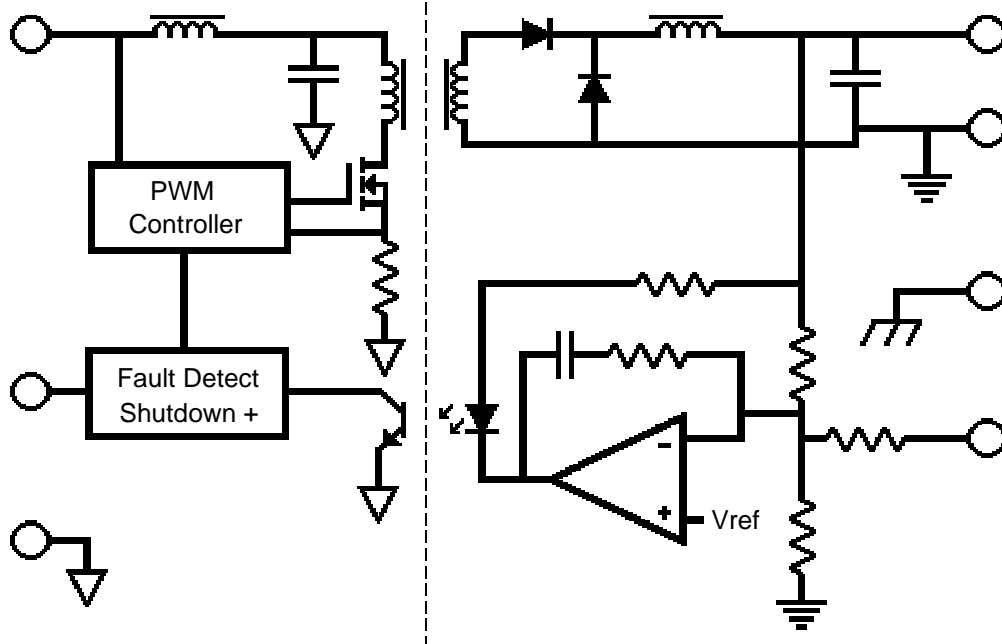

The DHC converters feature a transformer isolated feed forward topology operating at 400KHz to allow its extremely wide input voltage range.

The external connection through a resistor to the summing junction of the error amplifier can be used for voltage adjustment. These models are also offered with no connection to this pin.

DHC2800D Series

| | | | | Unbal |
|----------|--------|------|-------------|-------|
| DHC2812D | 11-50V | 5W | $\pm .208A$ | .333A |
| | 16-40V | 5.4W | $\pm .225A$ | .36A |
| DHC2815D | 11-50V | 5W | $\pm .167A$ | .267A |
| | 16-40V | 5.4W | $\pm .18A$ | .288A |


Again, this is the smallest series of converters from Apex (electrical and mechanical). They fit in an industry standard footprint with the exception that an NC pin is used to implement the Adjust/Comp function. If an existing application makes no connection to the NC pin, the DHC2800 series will drop in. These models are also available with an NC option.

The current ratings labeled “ \pm ” are for balanced currents on the positive and negative sides. The “Unbal” column indicates the maximum current for a single output. The other output may then supply current bringing total delivered watts up to the converter rating. As an example the DHC2812D running on 32V can be loaded to 0.36A on one side and 0.09A on the other side. To maintain regulation, the lighter load must draw at least 20% of the total power regardless of the total watts.

DHC2800D Special Features

- MHE2800/ASA2800 Compatible
- -55°C to +125°C temperature range
- Dual Tracking Regulation
- Mil-Std-704 (80V survive only)
- +/-10% Adjust range
- 1 inch square package

DHC2800D Block Diagram

 

The input section of these dual converters is just like the input of the singles. On the output section, note the top transformer winding along with the lower op amp form a regulated positive output in a similar fashion to the single converter.

The lower transformer winding is the heart of the negative output. In the middle we have the unique feature of the DHC duals: the second op amp and the power MOSFET provide tracking regulation for the negative output.

DB2800S Series

| | | | |
|---------|------|-----|------|
| DB2803S | 3.3V | 18W | 5.5A |
| DB2805S | 5V | 20W | 4A |
| DB2812S | 12V | 23W | 1.9A |
| DB2815S | 15V | 22W | 1.5A |


This series of converters from Apex takes a jump in electrical and mechanical size. The extremely rugged MO-127 package was developed by Apex to meet high power requirements. Total footprint area is 3 square inches and the pins are dual-in-line.

Data as of July 1999.

DB2800S Special Features

- Kelvin remote sensing
- 16 to 40V Input range
- -55°C to 125°C temperature range
- Mil-Std-704D (80V survive only)
- +/-10% Adjust range
- Rugged MO-127 package
- Synchronizable-up to 3 directly

DB2800S Block Diagram

 

The DB converters feature a current mode push-pull topology operating at 500KHz. The larger 12 pin package allows better filtering, Kelvin sensing, synchronization and output voltage adjustment.

Coming Soon - 30W Triples

5V 4A +/-15V .33A


5V 4A +/-12V .41A

1.35" x 2" Dual-in-line package

Dual supply outputs use linear regulators

Requires no minimum load

Triple Block Diagram

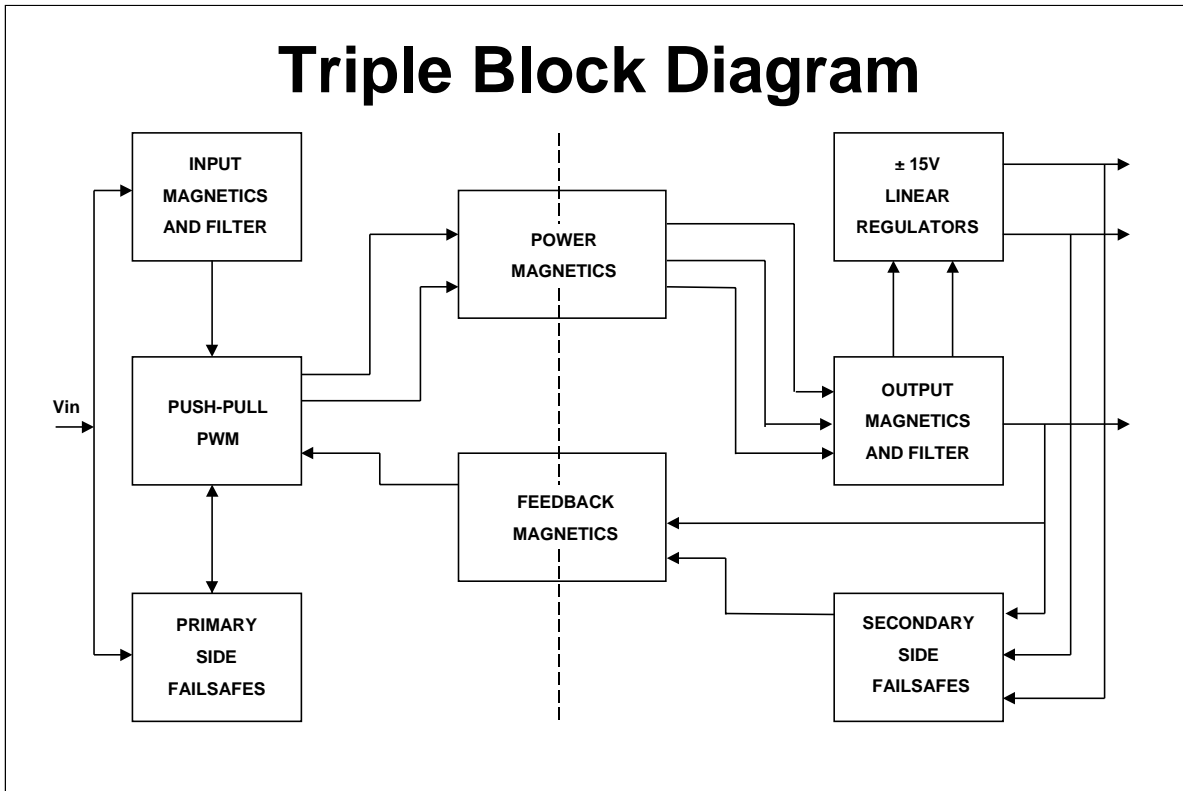

The number one design goal of this family of converters was SURVIVAL through any transient up to 80V, not just the converter, but for all outputs to stay within data sheet absolute maximums for logic and linear parts likely to be used with the converter.

Central to this survivability is the load fault protection circuit. Upon sensing an over current situation the converter shuts down for about 20ms. On restart, current limiting is increased about 50% for 100 μ seconds to help bring up heavy capacitive or difficult to handle loads. If the over current still exists after about 2ms, the cycle start over. The converter then runs about a 10% duty cycle during fault conditions eliminating overheating even at case temperatures of +125°C.

The remainder of the failsafe circuits concentrate primarily on orderly turn on and off. Whether these on-off sequences are initiated by normal power up, load faults or transients, the converter never outputs enough voltage to damage standard logic or linear parts.


PWM

Pulse Width Modulation

- More Work
- Less Waste


As delivered power levels approach 200W, sometimes before then, heatsinking issues become a royal pain. PWM is a way to ease this pain.

LINEAR POWER DELIVERY

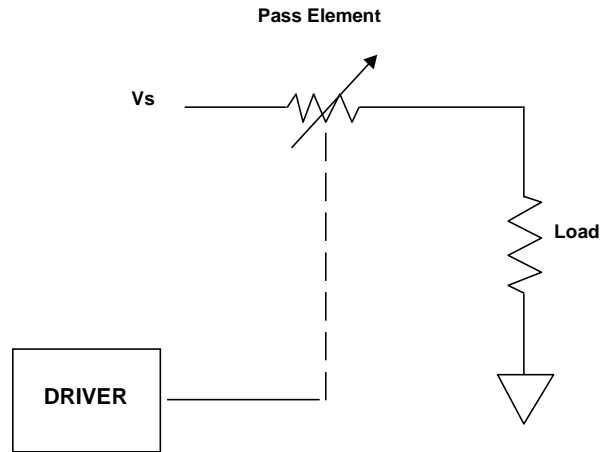

As power levels increase the task of designing variable drives increases dramatically. While the array of linear components available with sufficient voltage and current ratings for high power drives is impressive, a project can become unmanageable when calculation of internal power dissipation reveals the extent of cooling hardware required. Often the 20A drive requires multiple 20A semiconductors mounted on massive heatsinks, usually employs noisy fans and sometimes liquid cooling is mandated.

This slide illustrates the linear approach to delivering power to the load. When maximum output is commanded, the driver reduces resistance of the pass element to a minimum. At this output level, losses in the linear circuit are relatively low. When zero output is commanded the pass element approaches infinity and losses approach zero. The disadvantage of the linear circuit appears at the midrange output levels and is often at its worst when 50% output is delivered. At this level, resistance of the pass element is equal to the load resistance which means heat generated in the amplifier is equal to the power delivered to the load! We have just found the linear circuit to have a maximum efficiency of 50% when driving resistive loads to mid-range power levels. When loads appear reactive, this efficiency drops even further.

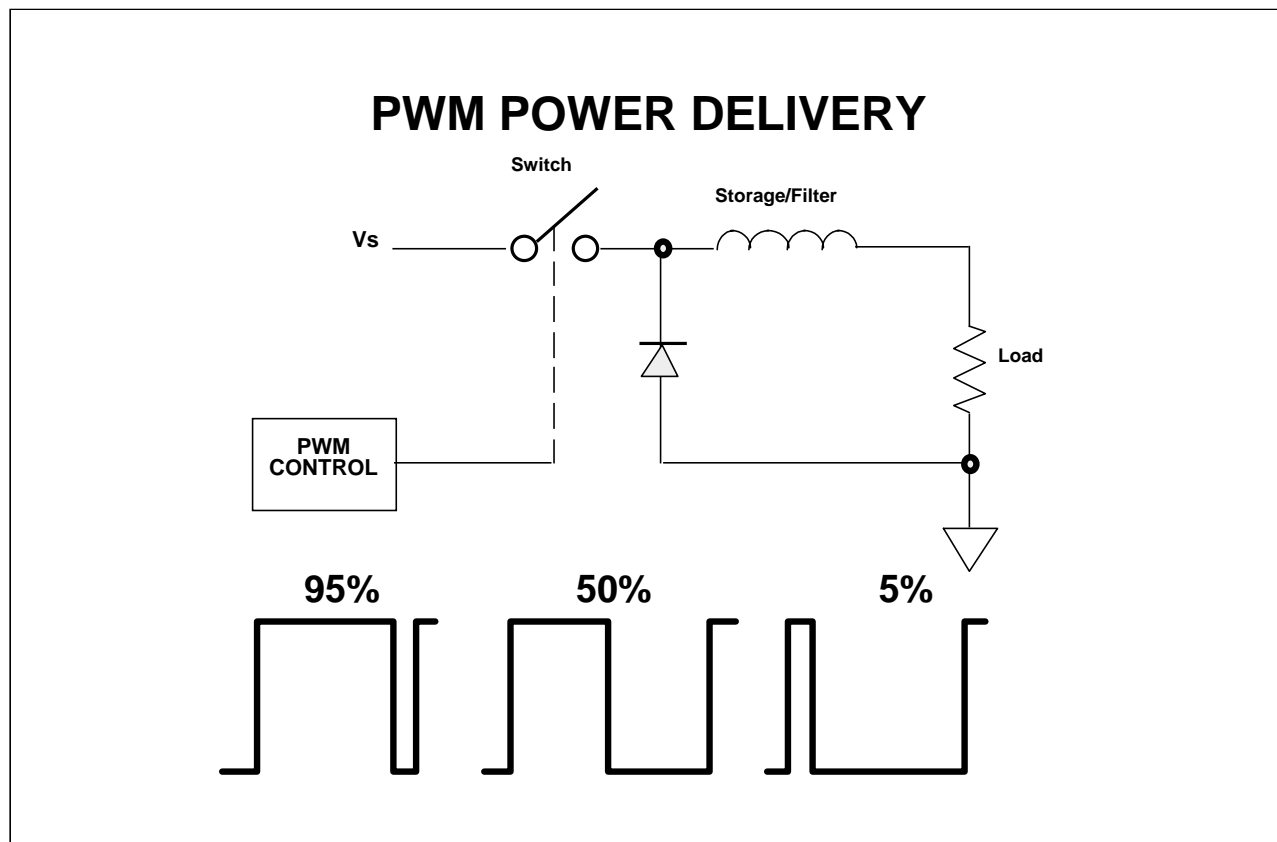

These figures illustrate the most basic PWM operation. The PWM control block converts an analog input level into a variable duty cycle switch drive signal. If high output is commanded, the switch is held on most of the period. The switch is usually both on and off once during each cycle of the switching frequency, but many designs are capable of holding a 100% on duty cycle. In this case, losses are simply a factor of the on resistance of the switch plus the inductor resistance. As less output is commanded, the duty cycle or percent of on time is reduced. Note that losses now include heat generated in the flyback diode. At most practical supply voltages this diode loss is still small because the diode conducts only a portion of the time and voltage drop is a small fraction of the supply voltage.

The job of the inductor is both storing energy during the off portion of the cycle and of filtering. In this manner the load sees very little of the switching frequency, but responds to frequencies significantly below the switching frequency. When the load itself appears inductive, it is often capable of performing the filtering itself.

With the PWM circuit, the direct (unfiltered) amplifier output is either near the supply voltage or near zero. Continuously varying filtered output levels are achieved by changing only the duty cycle. This results in efficiency being quite constant as output power varies compared to the linear circuit. Typical efficiency of PWM circuits range from 80 to 95%.

CONTRASTING DISCRETE LINEAR, HYBRID LINEAR AND HYBRID PWM 1KW DESIGNS

| | Discrete Linear | Hybrid Linear | Hybrid PWM |
|-----------------------------------|--------------------|------------------|---------------|
| <i>Wasted Heat</i> | 500W | 500W | 100W |
| <i>\$/Year ¹</i> | \$438 | \$438 | \$88 |
| <i>Package Count ²</i> | 8 x TO-3 | 2 x PA03 | 1 x SA01 |
| <i>Heatsink</i> | 0.11°C/W | 0.11°C/W | .55°C/W |

Almost all power amplifiers (low duty cycle sonar amplifiers are a notable exception) must be designed to withstand worst case internal power dissipation for considerable lengths of time compared to the thermal time constants of the heat sinking hardware. This forces the design to be capable of cooling itself under worst case conditions. Conditions to be reckoned with include highest supply voltage, lowest load impedance, maximum ambient temperature, and lowest efficiency output level, and in the case of reactive loads, maximum voltage to current phase angle.

Consider a circuit delivering a peak power of 1KW. A 90% efficient PWM circuit generates 100W of wasted heat when running full output, and around 50W driving half power. The theoretically perfect linear circuit will generate 500W of wasted heat while delivering 500W. Table 1 shows three possible approaches to this type design. In all three cases it is assumed ambient temperature is +30°C and maximum case temperature is +85°C. It also assumes power ratings of the TO-3 devices to be 125W each. Heatsinks for linear designs require multiple sections mounted such that heat removed from one section does not flow to other sections.


¹ Continuous operation at a cost of \$.10/KWH. If equipment is located in a controlled environment total cost will be considerably higher.

² Package count must be doubled for the discrete design if bipolar output is required.

Benefits Resulting From PWM Efficiency

- Operating cost savings
- Capital cost savings
- Reduced heatsinking 5:1
- Smaller, lighter finished product

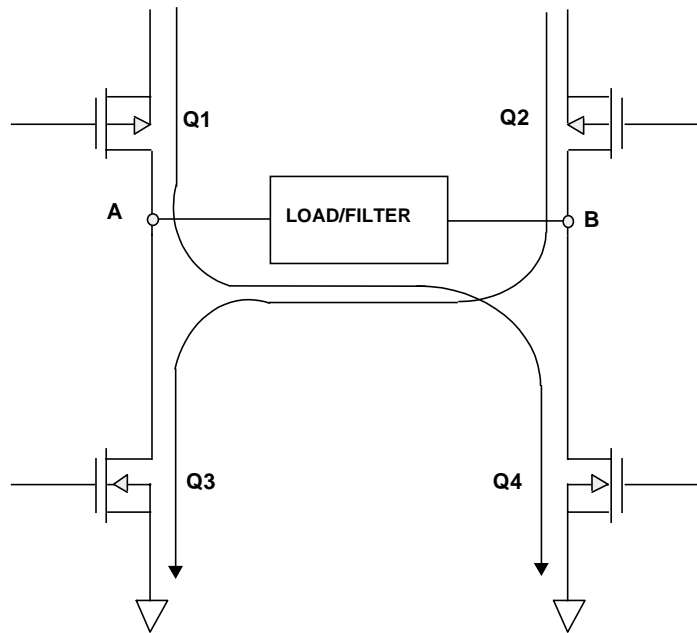H-BRIDGE PROVIDING BIPOLAR OUTPUT FROM A SINGLE SUPPLY




The simple form of a PWM circuit examined thus far is very similar to a number of switching power supply circuits. If the control block is optimized for producing a wide output range rather than a fixed output level, the power supply becomes an amplifier. Carrying this one step further results in the PWM circuit employing four switches configured as an H-bridge providing bipolar output from a single supply. This does mandate that both load terminals are driven and zero drive results in 50% of supply voltage on both load terminals.

The H-bridge switches work in pairs to reverse polarity of the drive even though only one polarity supply is used. Q1 and Q4 conduct during one portion of each cycle and Q2 and Q3 are on during the remainder of the cycle.

Note that if Q1 and Q3 turned on simultaneously, there is nothing to limit current. Self-destruction would be only microseconds away. The fact that these transistors turn on faster than they turn off means a "dead time" needs to be programmed into the controller.


H-BRIDGE WAVEFORMS

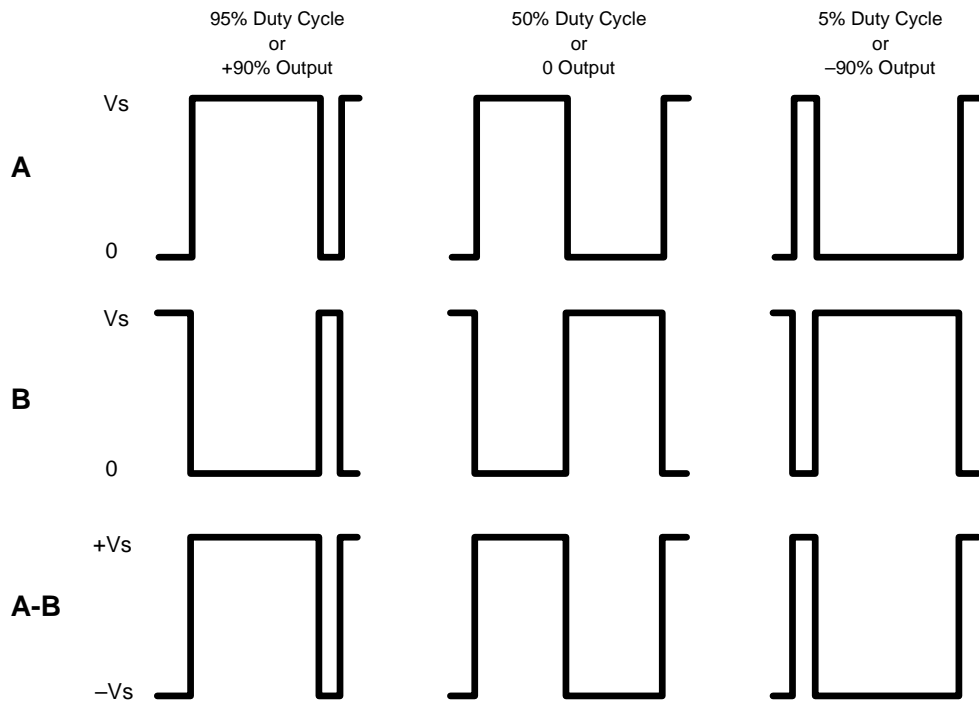


Changing duty cycle through 50% is a continuous function, meaning there is no inherent cause of crossover distortion as exists in a linear circuit. While the three waveforms seem a complex way to describe an analog drive signal, notice that waveform A is just the output of the “most basic” circuit we looked at earlier. Furthermore, A-B looks the same, the only difference is the bottom of the waveform is labeled “- V_s ” rather than “0”.

H-Bridge Waveforms

TEK-NO-WIZ

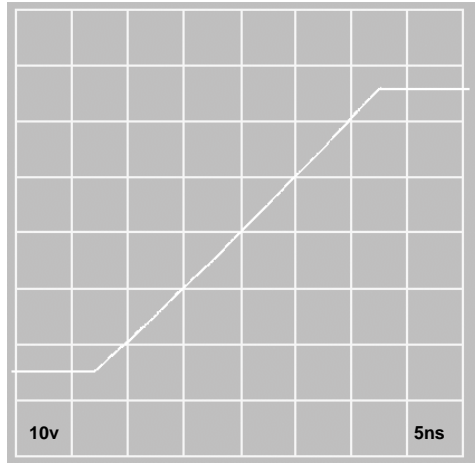

$$PBW = \frac{SR}{6.238 \cdot V_p}$$

 

~20nH


$$V = \frac{L \cdot di}{dt}$$

National had their FAST and DAMN FAST buffers, but they can't hold a candle to these guys. In fact, that's the problem with switchers- -they move voltages and currents around so fast it's difficult to keep the noise down. Here are a few items you may not have had a chance to use lately.

From the analog world we borrow the equation relating slew rate to power bandwidth. If your PWM amplifier switches 50V in 25ns, the slew rate is 2000V/us. With peak voltage of 50V, this is over 6MHz. With 5 or 10 amps flowing, those transitions contain RF energy similar to a moderate radio transmitter. Spending a few minutes thinking like an RF designer may be worthwhile.

Currents are also changing very rapidly in these circuits. The picture above is of voltage, but keep in mind this voltage is on one end of an inductor where a power MOSFET just interrupted current flow. Look at the positive going transition: the lower MOSFET was conducting and the inductor is driving the voltage positive, above the positive supply, to maintain the previous current flow. The path will be through the body diode of the upper MOSFET, into the supply bypass capacitor. If current changes 5A in the same 25ns, two 1 inch capacitor leads will develop an 8V spike. On high speed PWMs this spike will cause the controller to freak out, rendering the circuit useless.

Layout Sensitive? You Bet Your ...

 


Apex has an Eval Kit for every PWM model

Evaluation Kits for PWM amplifier prototyping are a must. A bad layout will produce ample frustration and can cause dead amplifiers!

At a minimum, each kit provides a PC board, a way to get the amplifier plugged in, a moderate sized heatsink, and enough hardware to get it all put together. Several models also provide chip capacitors for low inductance bypass of the supplies.


SA01

 

The four huge transistors are the FETs of the H-bridge.

Not quite as obvious, is a unique advantage of hybrid construction which discrete designs can only dream of. Mounted right on top of each FET is a temperature sensor, exactly where the heat is generated.


SA01 BLOCK DIAGRAM

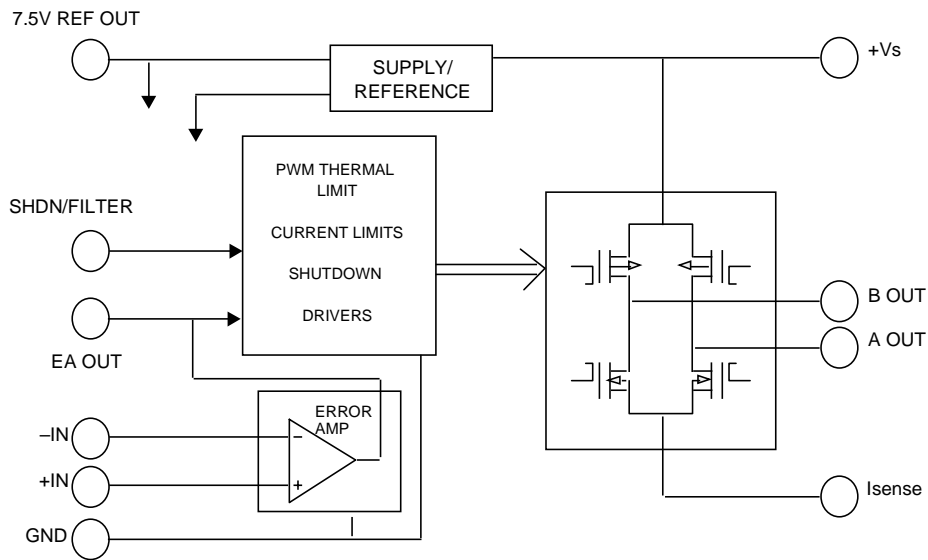

As EA goes more positive, high state of A OUT increases and high state of B OUT decreases.

PWM circuits are taking the same general course of development traveled by op amps and many other electronic functions. Concepts were brought to life using discrete components and were followed by modules, hybrids and then monolithics. The first hybrid on the scene in PWM technology is the SA01 from Apex. The amplifier contains all the functions needed to implement a wide variety of control circuits.



PWM BLOCK

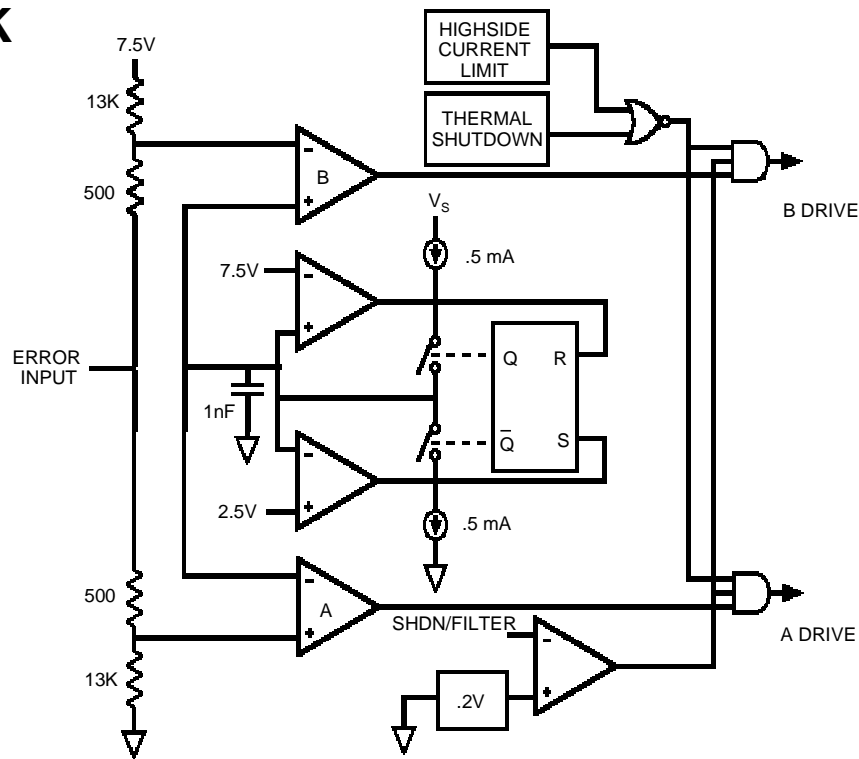

The oscillator portion of the PWM controller consists of two comparators, two switched current sources charging the timing capacitor and a flip-flop. When voltage on the timing capacitor reaches 7.5V, the upper comparator resets the flip-flop which opens the upper current source and connects the lower one. When the timing capacitor voltage reaches 2.5V, the lower comparator sets the flip-flop to start the next cycle.

Comparators A and B modulate the driver output duty cycle based on the voltage relationship of the PWM input voltage and the very linear triangle. For initial examination of operation, imagine the 500Ω resistors are shorted. When the input voltage is midrange, there are equal portions of the triangle wave above and below the input, thus a 50% duty cycle is generated at each comparator output. When the input voltage moves half way between midrange and the 7.5V peak of the triangle, 1/4 of the waveform is above the input and 3/4 is below the input generating a 75% duty cycle at the A comparator. With the inputs of the B comparator looking at the input and triangle voltages in the opposite polarity, it generates a 25% duty cycle. Note the circuit is arranged such that a positive going input voltage results in a larger percent on time for the A driver.



PWM WAVEFORMS

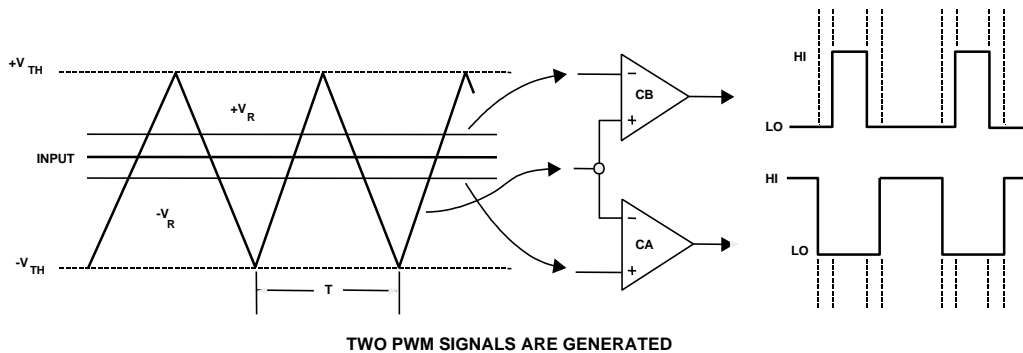 

With the 500Ω resistors actually in the circuit, the input voltage seen directly at the comparators is modified slightly, which modifies the duty cycle in a similar way. The A comparator sees a voltage a little more negative than the actual input. The basic function of positive going input creating a longer A duty cycle means this negative offset produces a slightly shorter duty cycle. In the same manner, the B duty cycle is also shortened to produce a dead band where all switches are off. Voltage drops across the two 500Ω resistors change as the input signal varies, but as one drop decreases, the other increases so total dead band time is relatively constant.

The and gates generating both A and B outputs can be disabled by either of two lines. The first of these lines represents activation of the thermal shutdown or the high side current limit. The second line is the comparison of the SHDN/FILTER input and a $0.2V$ reference. This configuration makes operation of both functions asynchronous and also allows operation to resume anywhere in the cycle when those lines return to their normal state.

Alternate Ramp Generator

  

The switched current source method of ramp generation is elegant in that the slopes are very linear and the end points are set with reference quality voltages. The circuit above is much less expensive and has less non-linearity than one would expect at first glance.

When used to generate duty cycle information, the total time above and below the input signal level is what counts- -not the non-linearity of one individual slope. Another way to look at it is that the upward slope has a non-linearity, the downward slope has another and the sum of both determine total non-linearity. It turns out there is a good amount of cancellation between the two such that the non-linearity of the sum is less than 1%.

We will discover other open loop errors are far greater; therefore, PWM amplifiers are almost never run open loop. Once the loop is closed, all of these errors are reduced to insignificant levels.

The alternate ramp generator also allows digital drive circuits to override the ramp waveform if desired.

Basic PWM Transfer Function

$$V_o = \frac{V_{mid} - V_{in}}{V_{pk}} * V_s - I_o * R_{on}$$

V_o = output voltage

V_{mid} = ramp midpoint

V_{in} = input voltage

V_{pk} = 1/2 ramp V_{p-p}

V_s = supply voltage

I_o = output current

R_{on} = total on resistance

- Poor load regulation
- No line regulation
- Temperature sensitive

- Close the loop!


The PWM controller output is duty cycle information only, It is proportional to the input signal level with respect to the end points of the ramp. The power MOSFETs convert this to power pulses and the filter integrates the area under the pulses to provide an analog output. Given a fixed duty cycle, the amplitude of the pulses, and hence the analog output level, is controlled by the power supply voltage and the MOSFET losses.

Those of us accustomed to working with power op amps take power supply rejection for granted; at least at low frequencies, so supply voltage changing a few percent is of no concern. In a similar fashion, we tend to not worry about op amp output impedance because it is reduced by the loop gain of the amplifier. Notice the assumption that nobody runs an op amp open loop; at least when looking for an analog output.

OK, we have learned that open loop performance of a PWM is very different than an op amp: its open loop gain is not $\approx 100\text{db}$, it is the ratio between the peak ramp voltage and the supply voltage and its supply rejection is not 60 to 100db, it is zero db. Accuracy and open loop operation of a PWM amplifier do NOT go together.

Closing this loop can be done locally in the voltage mode and with most models in the current mode. The alternative is closing the loop with system components. This often involves mechanical components, velocity or position sensors and a computer.

Pure Integrator: Key to Accuracy

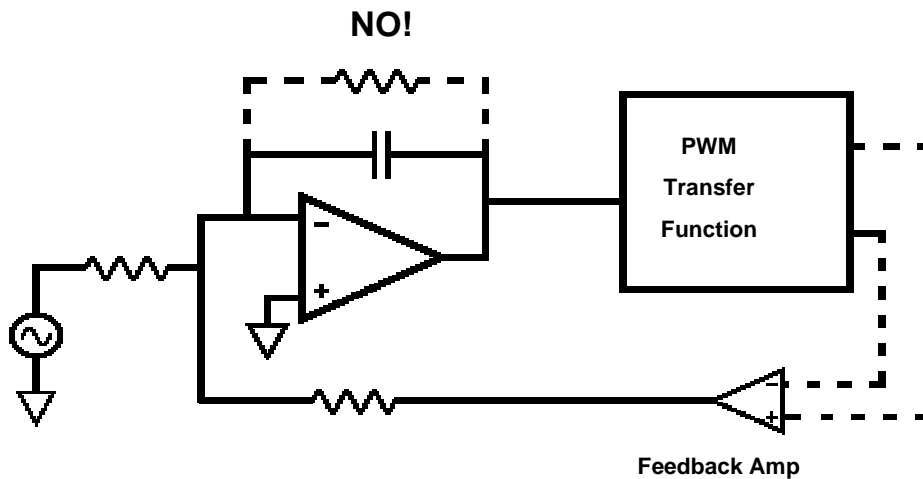


Lets go back to some basic op amp theory for a moment: The open loop gain (the voltage ratio of the output pin to difference of the input pins) of an op amp is extremely high (100db is 100K:1). This means the input pin voltage above is approaching zero. If there is no DC feedback and no current in or out of the input pin, then current through the two resistors must be equal. The PWM output is accurately scaled to the input signal.

The beauty of this analysis is the lack of discussion about the output level of the integrator. As long as all the circuit scaling insures we do not saturate any stage, the integrator takes care of all the variables: supply changes, ramp non-linearity, MOSFET losses, and changes in load impedance.

Sometimes it is a temptation to add resistive feedback. If this is done, DC feedback current lowers accuracy. To find this current we must know the output voltage of the integrator. Start with the PWM output and go backward through the transfer function. The worst case is when the output is near the supply voltage which demands the integrator output be near one of the ramp peaks. The resulting DC feedback current is now causing a mismatch between the input signal and the feedback amplifier currents. Not only is there a gain error, but supply variations and ramp inaccuracies creep in.


PWM VOLTAGE CONTROL

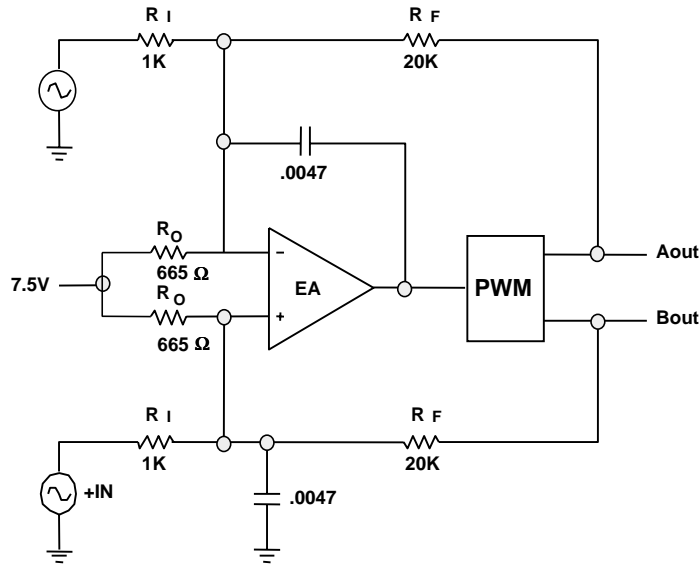

This is a differential input, voltage controlled output circuit resembling the familiar differential op amp configuration. Signal gain is simply R_F/R_I . Two pull-up resistors are used to bias error amplifier inputs within the common mode range. Select this value to get 5V bias when both inputs are zero, and both outputs are 1/2 the supply voltage (50/50 duty cycle.) At zero drive to the load, this differential stage is rejecting 1/2 the supply voltage present on both outputs. This means resistor ratio matching becomes critical. It should also be noted that even though the signal gain is 20, the gain of offset errors is 50 because the effective input resistance is the parallel combination of the signal input resistor and the pullup resistor.

While the specific load is not indicated here, it must be remembered that the SA01 output needs to be filtered. In fact, if the load were purely resistive, this circuit will NOT work! The load would receive full power one direction the first half cycle and full power of the opposite polarity the next. Many common loads such as motors and magnetic bearings will provide adequate filtering on their own. If this is not the case, filtering must be added.

PWM MOTION CONTROL

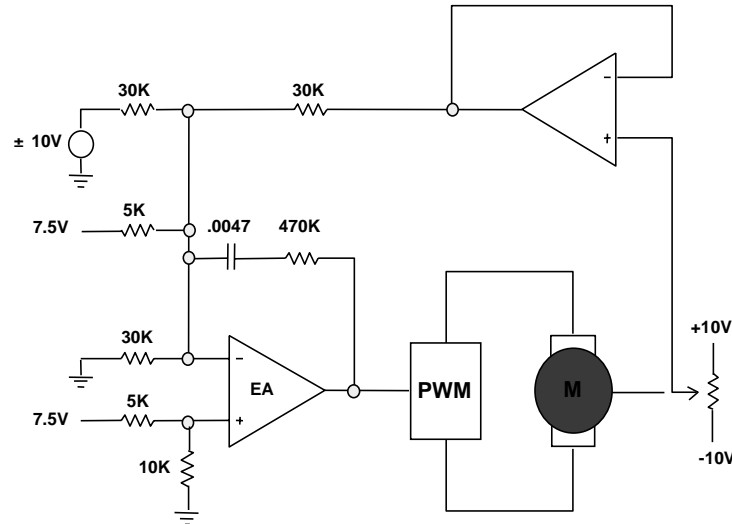

While one of the simplest forms of position sensing is shown here, options such as optical encoders, LVDT sensors, tachometers and variable capacitance transducers are all viable ways to sense speed or position. Again, error amplifier inputs are biased to 5V. While 20Kohm input and feedback resistors would have set proper gain and static biasing for the inverting input, they would have allowed common mode violations. This could happen if the system was at one position extreme while a very quick command came in to travel to the opposite extreme. The three 30Kohm resistors prevent common mode problems by increasing impedance from the summing junction to the two 10V signal levels (at the output and at the input) while adding an impedance to ground to form an equivalent 10Kohm impedance to match the 10Kohm leg on the non-inverting input.

The 0.0047 μ F and 470Kohm values shown here are ballpark values only. In closing the loop in this manner, the inertia of the motor, gear train and load, plus the responses of other electronic components of the application, all enter into the stability/response considerations.

Compare: PWM & Linear Amps


| | | |
|---------------|------------|---------------|
| V or I input | OK | OK |
| V or I output | OK | OK |
| Supplies | Single | Single/Dual |
| Max Power | Several KW | Fractional KW |
| Efficiency | High | Low |
| Noise | High | Low |
| Speed | Low | High |

Think about the two previous pages a moment.

They are both basically op amp circuits where the driving op amp has a specialized output stage labeled PWM. In fact there are many applications where linear and PWM solutions would both work. The keys to the decision may be on the last two lines above: IF THE APPLICATION DOES NOT REQUIRE LOW NOISE AND HIGH SPEED, PWM AMPLIFIERS CAN PROVIDE A SOLUTION.

The next item to consider is cost. On a cost per watt capability basis, PWM amplifiers are generally less expensive than linears. With PWM capability starting at 200W, they are not the most likely candidates for a 5W job. At a few hundred watts, PWM amplifiers are very attractive. In between these levels, you may want to think more about the options because both linear and PWM amplifiers will likely work.

PWM Frequency Relationships

 

The alternate ramp generator illustrated the relationship between oscillator and switching frequencies. Some PWM data sheets (such as the SA01) do not mention oscillator frequency because there is no divide by two circuit.

Signal frequency is that of the power drive to the load, power bandwidth. Between the load and the PWM amplifier is the low pass filter (or at least the model of one if the load is also the filter). On the input side of the filter we have the switching frequency. We then go down the slope to a point where the attenuation is adequate. The frequency band we cover while going down the slope is required spacing between the switching and signal frequencies.

Pure theory says filter slope can be increased simply by adding more poles. This is true to a point. We would probably question an eight pole filter in the small signal world. Do you really need that? Can you find high enough quality components to make it work? Can you afford it in terms of size and cost?

In the PWM world these questions are not only valid but are many orders of magnitude more important because power levels have gone from mW to KW! Rule of thumb: Allow a decade between switching and signal frequencies.

Power Design.xls

| Filter Design for PWM Amplifiers | | READ ME | Using the Complex Load: | |
|----------------------------------|-----------|-------------------------------|-------------------------|--------------------------|
| CAUTION! | | Refer to Applications Note 32 | | |
| Input Data | | Order Calculation | | 60 Load All Data For N=1 |
| Model | SA03 | Atten. @ Fsw | 39.085 db | 61 Load All Data For N=2 |
| Vs | 90 Volts | 22.5 N(exact) | 2.6052 | 62 Load All Data For N=3 |
| Fsw | 22.5 KHz | N(recommended) | 3 | 63 Load All Data For N=4 |
| Fmin | 0.001 KHz | | | 64 Load All Data For N=5 |
| Fcutoff | 4 KHz | | | 83 Load All Data For N=6 |
| Rload | 10 Ohms | Matching network | | |
| Cload | 0 uF | Cm = | 0 uF | |
| Lload | 0 mH | Lm = | 0 mH | |
| Vripple | 1 Vpk | Rm = | 10 Ohms | Read Me |
| Signal | 85 Units | | | No |
| Sig as ? | V peak | Note/W | | Auto Sweep on Load? |
| Notes: | | | | |
| 46 Print Filter | | 55 Show Attenuation in db & % | | |
| 56 Show Attenuation Graph | | 66 Show Filter Components | | |

So maybe filter design is not at the top of your list of most cherished jobs. Application Note 32 and the Power Design spreadsheet can help. Enter data describing the amplifier circuit, the load and desired attenuation. Placing the cursor in cells with red triangles will display notes of explanation. The order Calculation section converts your maximum ripple spec into db attenuation and by examining the switching and signal frequencies, it calculates the order, or number of poles needed. The matching networks calculated will cause reactive loads to appear resistive to the output of the filter, Finally, the actual filter components are calculated and the response is graphed.

Single Ended vs Differential


| Component Calculations | | | | | | | | | | | | | |
|------------------------|--------------------------------------------------|-----------|---------------------------|-----------|-------|--------------------------------------------------|-----------|---------------------------|-----------|--|--|--|--|
| | Differential Filter | | Single-ended Filter | | | Differential Filter | | Single-ended Filter | | | | | |
| N = 1 | L = | 0.1989 mH | | 0.3979 mH | N = 2 | L = | 0.2813 mH | | 0.5627 mH | | | | |
| | P-P Ripple = | 5.0265 | Amps out of the amplifier | | | C = | 5.6269 uF | | 2.8135 uF | | | | |
| | Avg. I _{out} for thermal calculations = | | 1.2566 | | | P-P Ripple = | 3.5543 | Amps out of the amplifier | | | | | |
| | | | | | | Avg. I _{out} for thermal calculations = | | 0.8886 | | | | | |
| N = 3 | L1 = | 0.2984 mH | | 0.5968 mH | | | | | | | | | |
| | C = | 10.61 uF | | 5.305 uF | N = 4 | L1 = | 0.3045 mH | | 0.609 mH | | | | |
| | L2 = | 0.0995 mH | | 0.1989 mH | | C1 = | 12.551 uF | | 6.2755 uF | | | | |
| | P-P Ripple = | 3.351 | Amps out of the amplifier | | | L2 = | 0.2153 mH | | 0.4307 mH | | | | |
| | Avg. I _{out} for thermal calculations = | | 0.8378 | | | C2 = | 3.0454 uF | | 1.5227 uF | | | | |
| | | | | | | P-P Ripple = | 3.2838 | Amps out of the amplifier | | | | | |
| N = 5 | L1 = | 0.3074 mH | | 0.6148 mH | | Avg. I _{out} for thermal calculations = | | 0.821 | | | | | |
| | C1 = | 13.484 uF | | 6.7418 uF | | | | | | | | | |
| | L2 = | 0.2749 mH | | 0.5499 mH | | Read me if you plan to use N=6 | | | | | | | |
| | C2 = | 7.1174 uF | | 3.5587 uF | N = 6 | L1 = | 0.3089 mH | | 0.6179 mH | | | | |
| | L3 = | 0.0615 mH | | 0.1229 mH | | C1 = | 14 uF | | 7 uF | | | | |
| | P-P Ripple = | 3.2532 | Amps out of the amplifier | | | L2 = | 0.3089 mH | | 0.6179 mH | | | | |
| | Avg. I _{out} for thermal calculations = | | 0.8133 | | | C2 = | 9.562 uF | | 4.781 uF | | | | |
| | | | | | | L3 = | 0.1508 mH | | 0.3016 mH | | | | |
| | | | | | | C3 = | 2.0595 uF | | 1.0297 uF | | | | |
| | | | | | | P-P Ripple = | 3.2369 | Amps out of the amplifier | | | | | |
| | | | | | | Avg. I _{out} for thermal calculations = | | 0.8092 | | | | | |

Single ended filters have at least an inductor between one output terminal of the PWM amplifier and the load while the other terminal of the load is tied directly to the other output of the PWM. Differential filters have at least an inductor between both PWM outputs and the load terminals.

While single ended filters have the advantage of using the same total inductance, but one fourth the total capacitance of the differential filter, this is not the end of the story. Unless the load is physically small (the electrical radiating surface) and physically close to the amplifier, the raw square waves will be broadcast to any circuit willing to listen. One PWM output goes directly to the load and with even ordered filters, both load terminals have AC tied to them. How long is your cable (transmission antenna) to the load?

The analysis function we will look at next handles only single ended filters. The data above shows how to translate to differential values if desired. Capacitors for differential will be twice those of single ended and inductors will be half.

What a Wonderful Word!

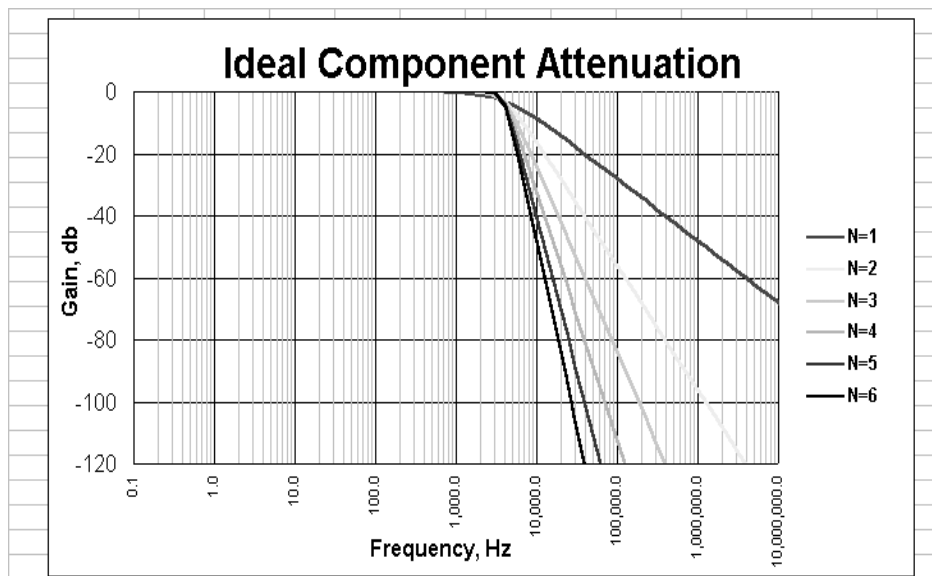


“Ideal” is a great word. In this case it means most of the work still lies ahead in finding components which work as advertised in the MHz range and whose losses won’t kill you at high current levels.

For capacitors, this usually means two and more often three parallel devices: high value/low frequency, low value/high frequency and lower value/higher frequency. You will probably want ceramic for the highest frequency ranges. For the larger capacitance values tantalum, or electrolytic types at higher temperatures, will work well.


Finding suitable inductors is also challenging. Air core inductors get away from the magnetic saturation problem and they have less tendency to become dummy loads at high frequency. The down side will be more turns of wire and more copper losses. When adding a magnetic core make sure the material can handle the high frequency components of the square wave at the switching frequency and can accommodate the flux density of the peak currents to be delivered to the load.

The Penalty of Real Parts

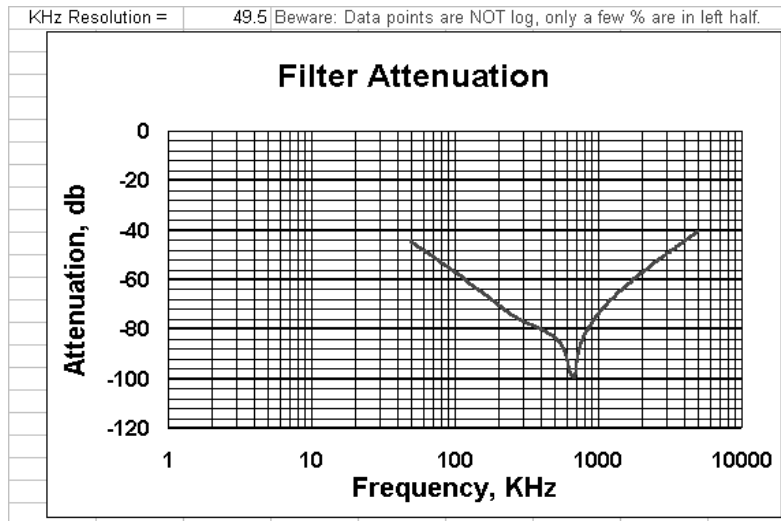

Attenuation is about as expected up to 200KHz, but then the parasitics come into play. We learned earlier that the extremely fast transition times of the PWM amplifiers means high frequency content is powerful well into the megahertz range. This graph is telling us spike content at the filter output is far from ideal. Is this OK? Or should we spend more on better filter components?

Light Test Load- -Oops!

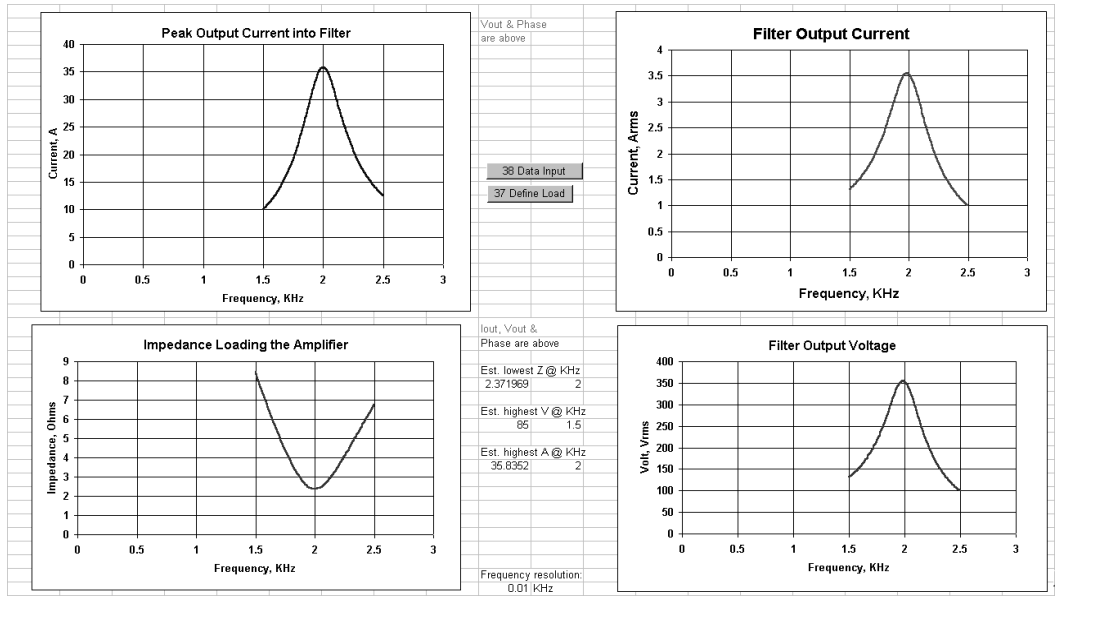


So, you're an old hand with linear power circuits; you fire up the prototype with a light load to make sure everything is working before connecting the real load.

While this procedure is commendable for linear drives and *may* work fine of a PWM drive, watch out for tuned circuits in the filter/match network/load. Replacing the designed 10 ohm load with 100 ohms produces the graphs above. At 2KHz impedance drops to ~2.5 ohms, peak current tops 35A, load voltage is ~355V and load current is 3.5A. 1200W delivered to the *light* 100 ohm load!

Be careful- -deadly voltages easily generated.

The second order filter driven at the designed cutoff frequency, with no load, is a series resonant circuit which presents a theoretical zero impedance to the amplifier and develops a theoretical infinite voltage at its center.

Right Load gets Right Results

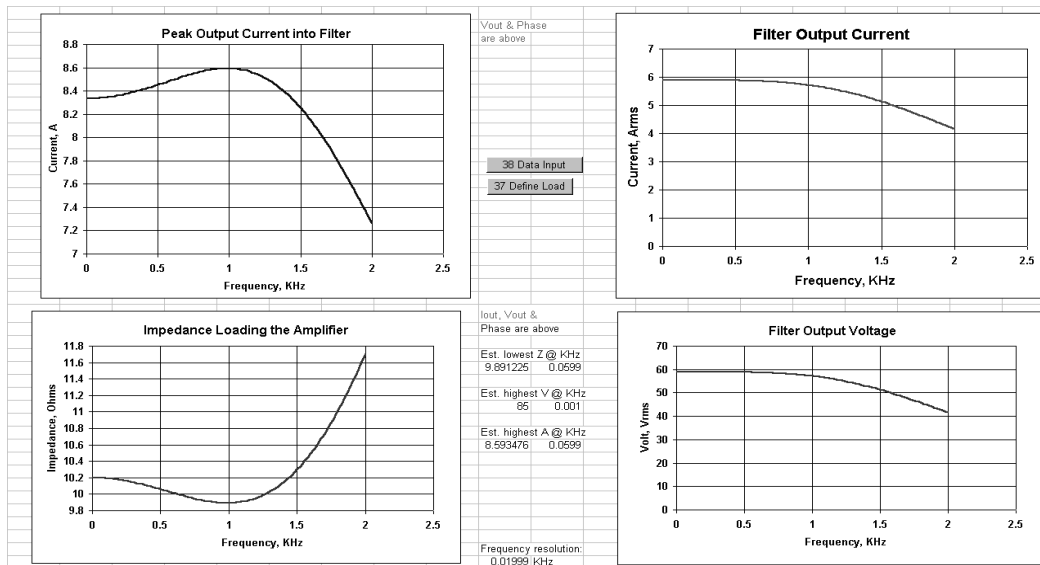


With proper termination of the filter we get a little min-band peaking amplifier output current but the catastrophic potential of bad filter termination has gone away.

While this operation is *proper*, is it what you wanted? The cutoff frequency of the filter is where the load voltage is down 3db. does -3db equal .707 or .5? Both, .707 is the voltage or current ratio and .5 is the power ratio. Many times the half power at maximum frequency is not acceptable.

Some designers routinely start their filter calculations at twice the required frequency of the application.


Power Out for Double Fc

 

Doubling the design cutoff frequency of the filter enables the circuit to deliver a lot more power at the desired 2KHz.

Yes, you could double again to achieve an even flatter pass band. No, there is no free lunch. Every time you move cutoff frequency up, you allow more switching frequency power in the load. Yes, you can add more poles to the filter. The question becomes one of cost in terms of money, extra loss in the filter, size and weight.


Power in the Matching Network

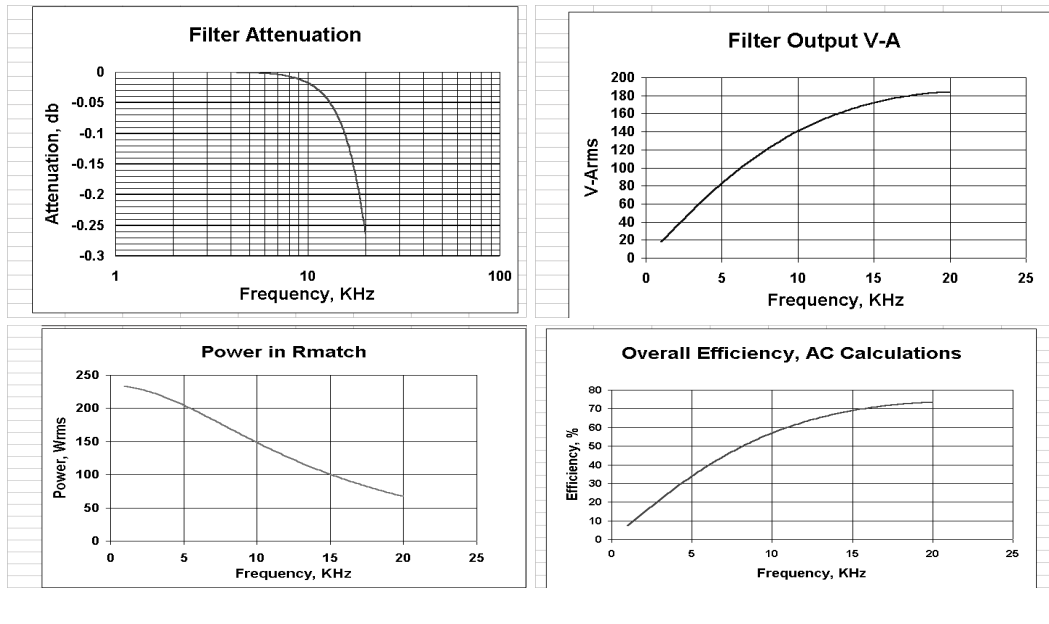

While the conjugate matching network performs almost like magic in terms of forcing the attenuation graph to near text book shape, there is a cost involved. This cost is slight when the load is mostly resistive but power dissipated in this network approaches power delivered to the load as the load approaches pure reactance.


These graphs are for an application driving a 1uF piezo stack with 12 ohms series resistance, to 75V peak from 1KHz to 20KHz. The filter cutoff frequency was designed for 40KHz providing quite flat response. The V-A output falls at low frequency because the load impedance is increasing. To keep filter termination impedance flat, the matching network impedance moves in the opposite direction giving rise to large power levels in the matching network resistor. As this power is not delivered to the load, efficiency is far from the desired level.

Without a Matching Network

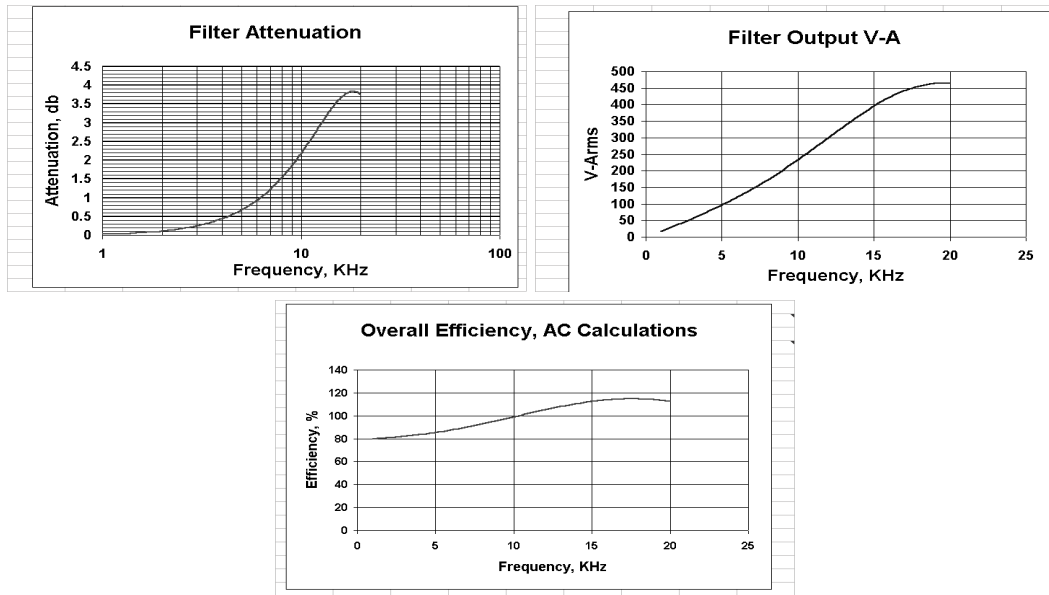

With no matching network we cannot lose any power there, but this leaves the filter with an improper termination. The result is a resonant circuit causing almost 4db peaking. In terms of V-A in the load near the upper end of the band, power goes from ~180 to over 450V-A. The efficiency graph looks like a patent should be applied for. The reason for this is recirculating currents in our newly formed resonant circuit.

Modified Matching Network

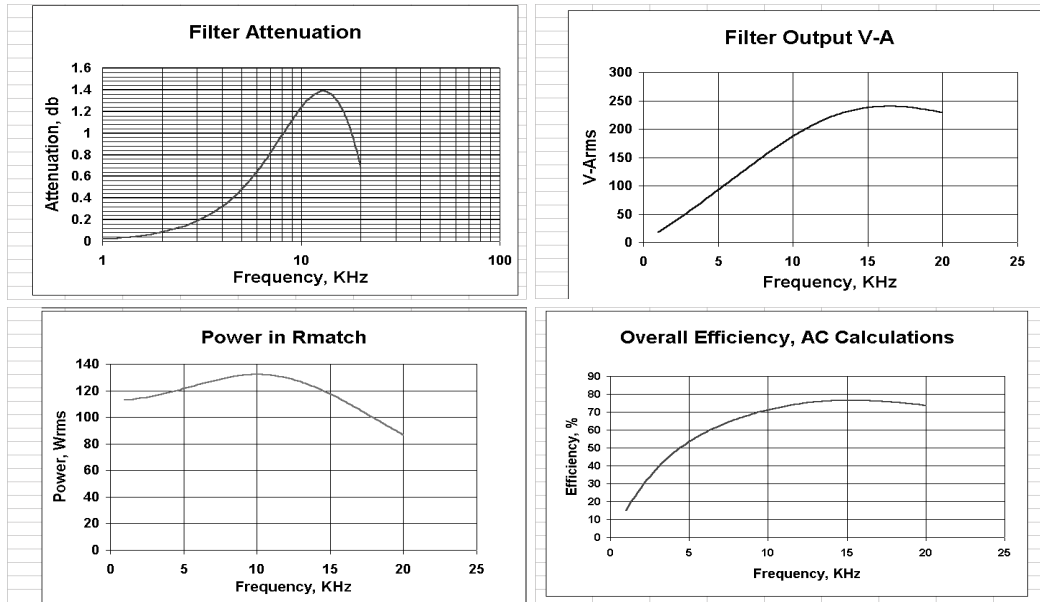

Here lies part of the beauty of the Power Design spreadsheet; it took more time to prepare this slide than it did to discover that doubling the resistor value in the matching network may provide a workable compromise.

Peaking at the load is down substantially from not using any network and wasted power is down substantially from using the ideal network.

Only Need ½ a PWM Amp?


- Unipolar, usually grounded loads
 - PPS, TEC, 3Ø motor
 - Heater, uni-directional speed control
 - Active loads, CD weld charger
 - Saves ~½ internal losses
 - Saves ~25% on cost
-
- SA13, 14, 16

While all Apex PWM amplifiers can be configured in the half-bridge mode, three models are built that way to save you money. These models are ideal for applications requiring only unipolar drive. This means the load is usually grounded. Three amplifiers driving a three phase motor, and active load circuits are exceptions to this rule.

Since load current flows through only one MOSFET at a time rather than two, efficiency is increased. By leaving out some of the internal components, a cost savings is realized.

Keep it Cool!

$$R_{on} = f(t_j)$$

 

The “on” resistance of a power MOSFET increases a little over two times as junction temperature rises from +25°C to +150°C. This means a larger heatsink increases both output capability and efficiency. If there’s good news to this story it’s the non-linearity of the curve: The first few degrees we lower temperatures buys the most. Here’s a way to approach the problem.

First order power dissipation in the PWM is a function of the output current and the voltage drop at that current. This is the PWM advantage over linear power delivery; supply voltage is not part of the equation. Start with the 60°C curve (interpolate if required). Find your current (PEAK if below 60Hz, otherwise RMS) and read the voltage drop. The product is power dissipation. The voltage drop divided by supply voltage approximates efficiency (quiescent current of both V_{cc} and V_s will reduce this a little). The heatsink rating is 60°C minus ambient temperature, divided by power.

Are these numbers all affordable? Remember that a bigger heatsink actually reduces the watts to be dissipated (unlike linear systems).

PWM Power Dissipation


| Calculating Power Dissipation for Apex PWM amplifiers | | | | | | | | | |
|-----------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------------------------------|---------------------|----------------------------|----------------|----------|----------|-----|--------------------------|-----------------------|
| Model | SA03 | Read Me | | Ta max = | 25 | Tj max = | 150 | Tc max = | 85 |
| Power for Sine Wave Outputs | | | | | | | | | |
| Vs | 90 Volts | | | Fswitch = | 22.5 KHz | | | ripple = | 0.444292 A |
| Fmin | 0.001 KHz | | | Iq Vcc = | 0.08 A | | | Iout = | 8.335271 A |
| Fmax | 2 KHz | | | Piq Vcc = | 1.2 W | | | Ifet = | 8.347104 A |
| Sig | 85 Units | | | Iq Vs = | 0.0665 A | | | Fhotspot = | 0.0599 KHz |
| Sig as ? | V peak | Note/W | | Piq Vs = | 5.985 W | | | Minimum Heatsink: | 2.608519 °C/W |
| | | | | Max delta Tj = | 125 | | | Max delta Tc = | 60 |
| General Procedure: First Filter Design Tune the filter Select the heatsink | | | | | | | | | |
| Actual HS: | | | | | | | | R PchFET | 0 Ohms |
| Approx. Power Out | 354.1725495 Wrms | | | | | | | R NchFET | 0.128717 Ohms |
| Estimated Internal Pwr | 19.63693269 W | | | | | | | Rwire | 0.05 Ohms |
| Estimated Case temp. | 45.27818631 °C | Read me | | | | | | Rtotal | 0.178717 Ohms |
| Est. Junction temp | 49 °C | Read me | | | | | | D.C. max | 99 % |
| Efficiency @ Fhotspot | 94.74680723 % (AC Amplifier Only) | NA | | | | | | Vpk out | 85 |
| Est. Vpk capability | 87.56261428 V | | | | | | | Ipk out | 8.593476 |
| Notes: | From B18 | | | | | | | | |
| Filter: | SA03, Vs= 90, Fsignal= 85V peak from .001 to 2KHz, RI= 10, CI= 9999999999999999, LI= 0, Cm= 9999999999999999, Ln | | | | | | | | |
| | 37 Define Load | | | | | | | | |
| | | Sweep the Frequency | | | | | | | |
| | | | 65 View Amp Out Last Sweep | | | | | | |
| | | | | 68 Print Data | | | | | |
| | | | | | | | | 71 View Load Last Sweep | |
| | | | | | | | | | Page down for charts. |

Did someone complain about lack of detail on the previous page? Here they are, and the inputs were transferred from the PWM Filter sheet. If you change a green cell value, blue cell answers will not be valid until you run a frequency sweep.

If you get errors when you do this at home, check the READ MEs. You need the Analysis Toolpak add-in. Now you can see in the upper half, quiescent powers calculated, plus output current, FET current, hotspot frequency and best of all, minimum heatsink.

A little lower, notice I have already input an acceptable heatsink value and operating points have been calculated. Please read the comments. The Power Output is assumes a properly terminated zero loss filter and a power factor of 1 in the load. Use button 82 to see efficiency including filter losses. If you enter too small a heatsink, most of these answers will be forced to ridiculously large numbers and a red TOO HOT warning will appear.

Find a Heatsink Rating

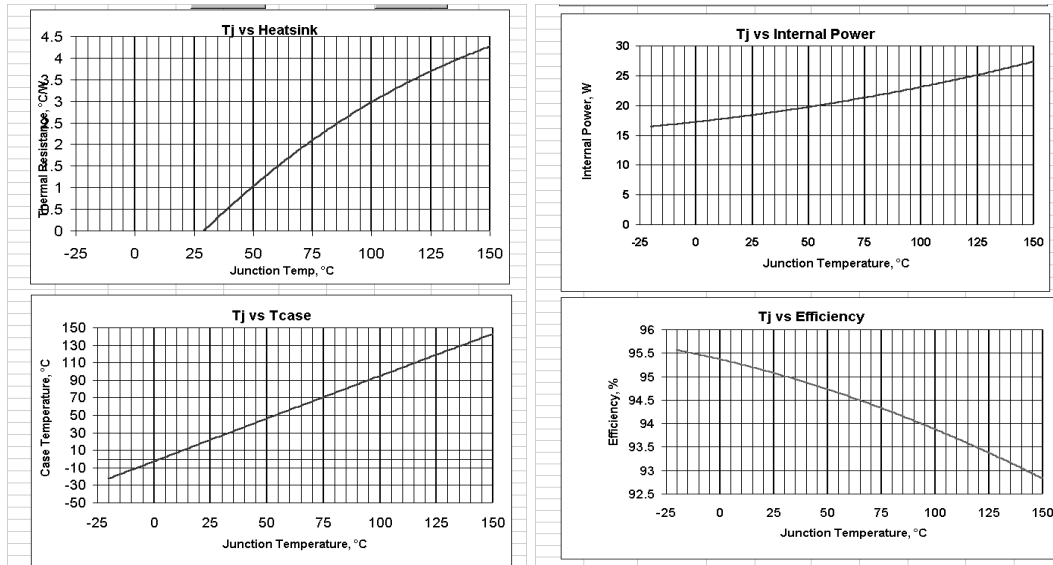

In the upper left graph it looks like a quite small heatsink will keep junction temperatures below maximum. However the graph below says there is little difference between junction and case temperatures and we surely want to keep case temperature a lot lower than 150°C.

On the top right we see that internal power dissipation of the amplifier changes with junction temperature - - or with the size of the heatsink. Below we see this same effect expressed in terms of efficiency. This is a relatively low power PWM application. With higher power applications the percentage point change shown on this graph will increase.

Find a Heatsink

Selecting an Apex Heatsink See ACCESSORIES INFORMATION data sheet for specifications

| | | | | | | |
|--------------------|-------------------------|----------------|----------------------------------------------|-----------------------------|------------------|--|
| Thermal Resistance | Package | | | | | |
| 2.3 | MO127 | | <input type="button" value="Update Result"/> | | | |
| READ ME | | | | | | |
| MO127 Heat-Sink | | | | Velocity Calculator: | | |
| | | | | 100 CFM | | |
| Apex PN | Price /1pc USD Domestic | No Wind Rating | Wind Speed in FPM | Water Flow in GPM | | |
| HS06 | \$42.30 | 0.96 | 0 | | 10 Inch Diameter | |
| HS11 | \$214.80 | 0.675 | 0 | 0 | 183.3464944 FPM | |
| HS18 | \$81.00 | 1 | 0 | | | |
| | | | | 9.5 Inch Width | | |
| | | | | 12 Inch Length | | |
| | | | | 126.3157895 FPM | | |

Believe me, heatsinking is NOT the most easiest science in our universe.

Let's start with "the" heatsink rating. The HS03 is rated at 1.7°C/W in free air. True, when power dissipation is about 45W, but check the actual curve at 10W and you'll find a rating more like 2.3°C/W. On top of that, "free air" means no obstructions to air flow and the flat mounting surface must be in the vertical plane. Demands for higher performance in smaller packages can be at odds with optimum heatsinking. Poor installation choices can easily reduce effectiveness 50%.


Moving on to this selector software. Air velocity curves from the heatsink data sheet (when available) have been approximated with polynomial expressions. While these errors are minor compared to the previous paragraph, it would be good to allow 10% for velocity ratings over 150 feet per minute and 20% below that.

Adding a fan to your design enables you to use smaller heatsinks. Please remember: Most fans are rated in cubic delivery and this rating varies with working pressure. A 5 inch diameter fan delivering 100 CFM produces over 700 FPM right at the fan. If this air is flowing through a 19 x 24 inch rack, theoretical velocity is down to 32 FPM, will vary with location and goes lower as the rack is sealed tighter.

The bottom line: Without case temperature measurements, your design effort is NOT complete!

PWM AMPLIFIERS

* Half Bridge

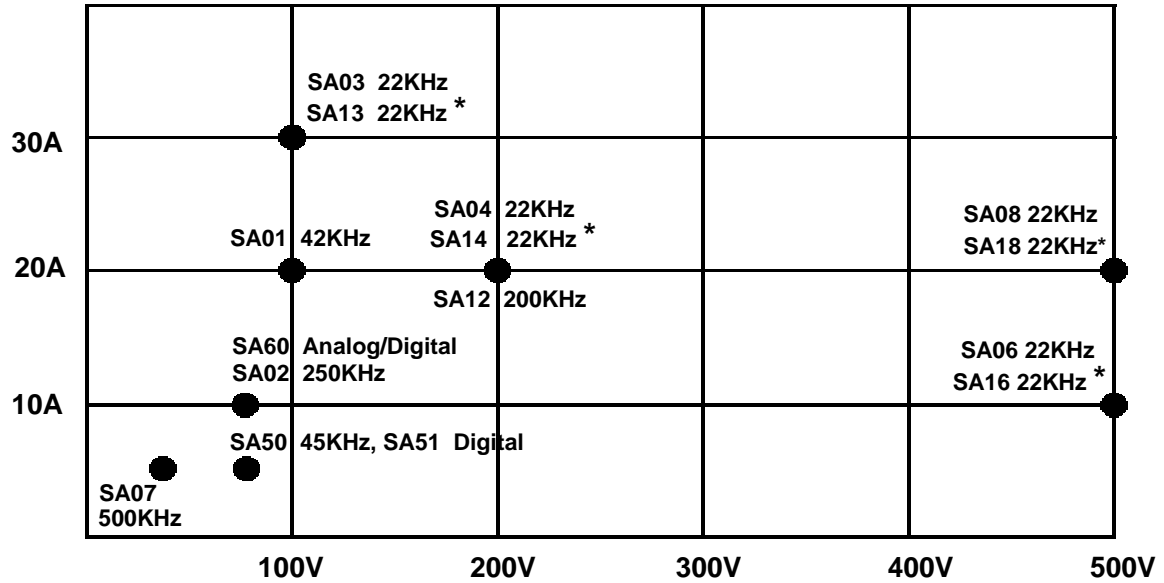


Data as of January 2000.

APEX'S WORLD OF POWER OP AMPS




APEX is the industry leader in monolithic and hybrid high current and high voltage power amplifiers. With more than 70 different models, we provide solutions for designs requiring output current greater than 1A or total supply voltages above 100V. When considering the cost versus performance trade-offs between using a power op amp versus discrete circuits, you must figure in design time, troubleshooting, procurement as well as production costs, not to mention labor, as well as the reliability factors. More often than not, you will find *it does not pay to be discrete!*

 

Apex offers a wide variety of packaging solutions to meet your needs. The 8-pin TO-3 is cost effective and easy to heatsink. The 10 and 12 pin Power Dips share the same rugged construction features but offer larger area for increased power handling capability. The power SIPS are easy on real estate and their flat back mates to a wide variety of heatsink options. The surface mount packages promise the ultimate in circuit density. All models featuring monolithic construction are also offered in chip form.

LINEAR OPERATION BASICS

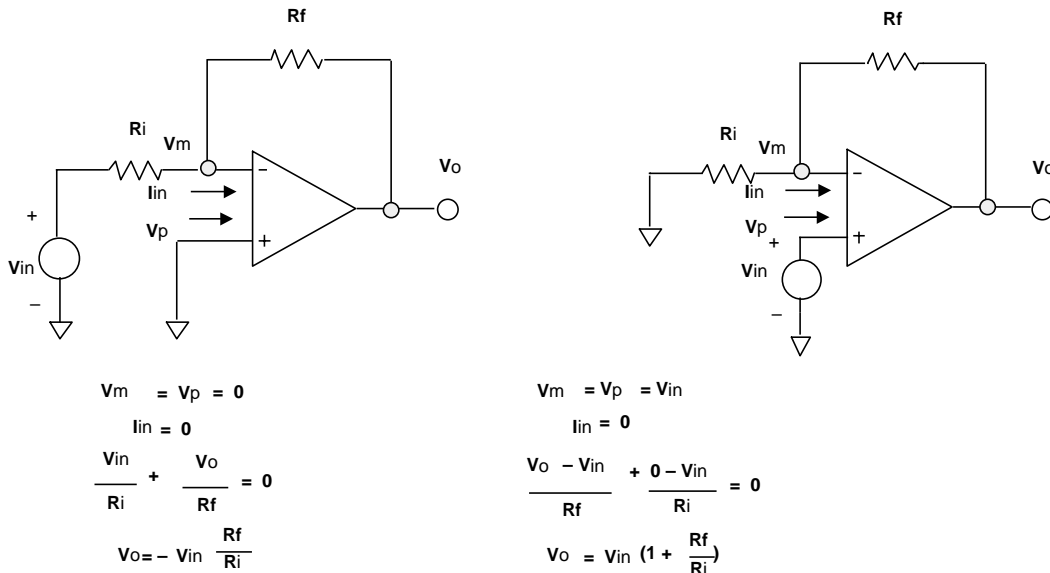

Before we discuss non-linear operation, we will cover some of the basics of linear operation for that mythical creature, the "ideal op amp". The three most important characteristics of an ideal op amp are:


1. Infinite input impedance
2. Zero output impedance
3. Infinite open loop gain

Let's review the inverting configuration in light of these three basic characteristics. #1 dictates that the input current into the op amp is 0. #3 implies that any voltage appearing between the input terminals will result in infinite output voltage. The resistive divider action of R_f and R_i causes a portion of the output voltage to be fed back to the inverting input. It is this **NEGATIVE FEEDBACK** action coupled with #3, open loop gain, that keeps the voltage between the two inputs at zero.

In the inverting configuration, this results in a "virtual ground" node. The concept of a virtual ground, coupled with the zero input current flow, allows the "closed loop gain" or transfer function of the circuit to be easily calculated. Current flow in R_i is equal to V_{in}/R_i . The same current is forced to flow through R_f , giving an output voltage of $-i_{in}R_f$.

In the non-inverting amplifier, the infinite open loop gain of the amplifier, coupled with negative feedback, force the inverting terminal to be equal to the non-inverting terminal. This sets up a voltage across R_i which develops a current that also flows through R_f . Therefore, the total output voltage is $s V_{in}/R_{in}$ current times the series combination of R_f and R_i .

Class C Output Stages

 


Class “C” output stages tie the bases or gates of the power devices together. Omitting the usual bias network between these bases reduces cost with the penalty of increased crossover distortion.

Assuming a resistive load and the drive stage voltage in the range of $\pm 0.6V$. There is no output current because the power devices need about a V_{be} to turn on. There is a dead band of about 1.2V which the driver must cross over before output current can change polarity. For MOSFET outputs this dead band is usually somewhere between 4 to 6V.


The good news is that because the output does not move, there is no feedback to the driver. It is running open loop during dead band transition and slews across as fast as it can. This means at low frequencies this distortion is quite low. Class “C” outputs are generally not recommended above 1KHz but this varies with tolerance of distortion.

PA51

 

With a minimum transistor count and no resistors, the class “C” amplifiers enjoy a roomy layout. The power transistors are soldered to silver thick film conductors. Small signal devices are epoxied and wire bonded to gold thick film conductors. Wire bonds are 1 mil and 5 mil diameter. The white ceramic substrate is beryllium oxide (BeO) which spreads the heat over a wide area before it travels through the steel header. The substrate is also solder attached.

Simple Class AB Outputs

 


The class “AB” output keeps some current flowing in the output transistors at all times to minimize crossover distortion. This area is still the largest contributor to total harmonic distortion but the “dead” band is gone.

The circuit is known as a V_{be} or V_{gs} multiplier. Think of this transistor as a non-inverting op amp with the V_{be} (V_{gs}) as an input and two about equal input and feedback resistors. If the multiplier transistor and the output transistors are tightly thermally coupled, distortion can be kept low and the possibility of thermal runaway is eliminated. This is one area where the hybrid really shines over a discrete circuit because these transistors are physically and thermally close to each other. Many Apex amplifiers also use thermistors to compensate for tracking differences due to the transistors being different types. Imagine the tracking differences when the multiplier and power transistors are in separate packages.


We refer to this as a simple amplifier because of the monolithic driver stage which may incorporate 50 to 100 transistors on a single chip.

PA12

 

The black areas are thick film resistors which are very cost effective because many resistors can be screened on a single pass and they require no wire bonding. Their intimate contact with the substrate makes them run cool. Wire size here jumps to 10 mils. On higher current products we also use 15 and 20 mil wire.


Complex Amplifier

 

Here is the most difficult and costly way to build a power op amp. Monolithic driver candidates are often lacking in performance above $\pm 15V$ and above $\pm 40V$ the picture is down right discouraging.


Being able to select each individual transistor for optimum overall performance of the power op amp results in DC accuracy under $1mV$, speeds to $1000V/\mu s$ or total supply voltages to $1200V$.

PA85

 


Real estate is at quite a premium with the complex designs. The only new thing added here is the blue glass layer covering most of the conductor traces. It has a two fold purpose: It is a bonding aid and an electrical insulator. This model happens to be a 450 volt part.

PA45

 

This photo represents the latest technology advance in power op amps. Having only one chip enhances reliability and lowers cost plus enables smaller packages all at the same time. This amplifier is a 150 volt, 5 amp model.


High Current Amplifiers

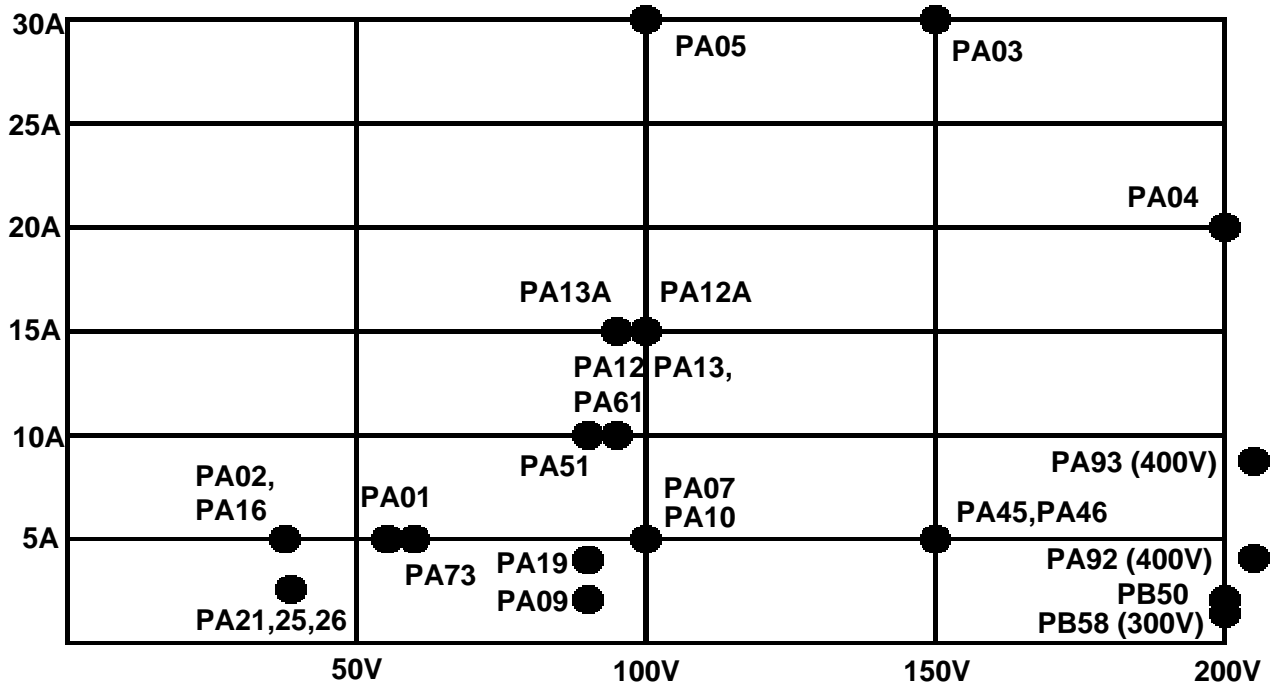

From the plastic packaged PA26 for USD\$17.30 to the PA03 for USD\$525, Apex covers a very wide spectrum of multiple ampere models. Typical power response ranges from 13KHz to 3.5MHz.

Data as of January 2000.

High Voltage Amplifiers

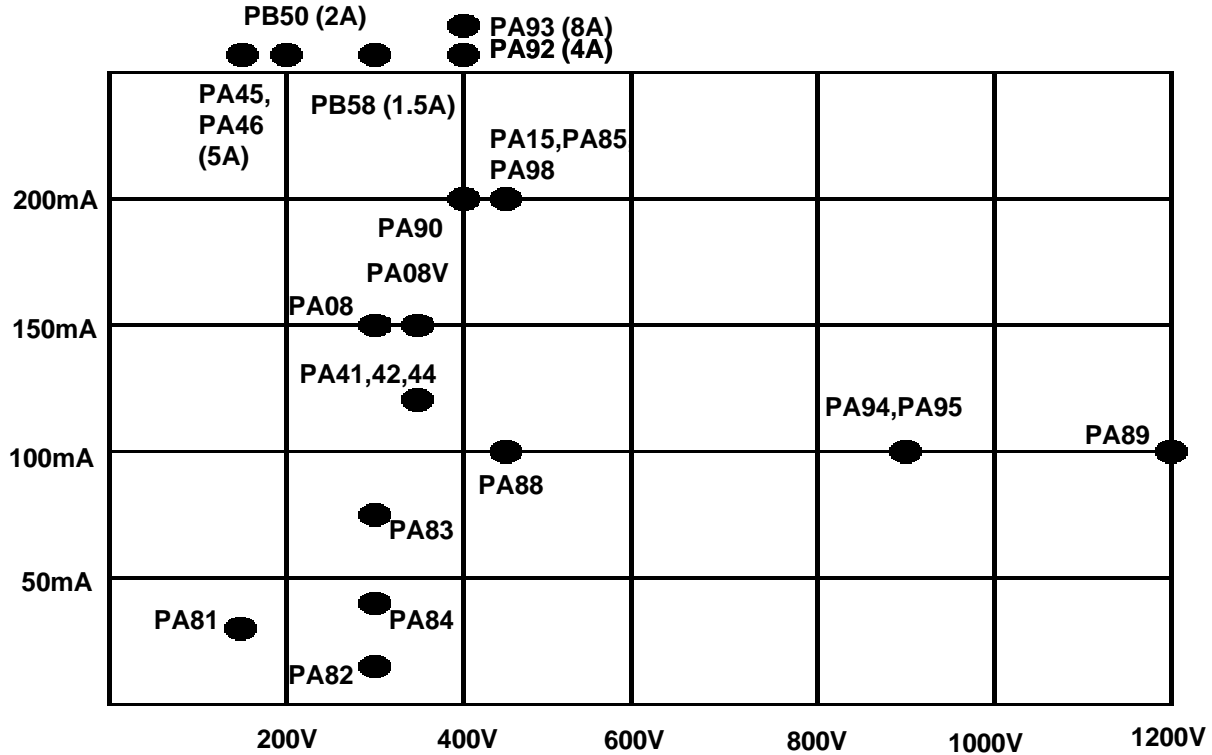

You are looking at the widest selection of high voltage op amps anywhere. From the surface mount PA44 for USD\$36.20 to the PA89 for USD\$525. Typical power response ranges from 5KHz to 500KHz.

Data as of January 2000.

Model Selection: Step 1

| Part Selection | | | | | | | | | | | | | | | |
|---------------------------|---------|--------------------------|------|-------------------------------|------------------|----------------------|---------------|-------------------------|--------------------|-----------|------------------|-----------|----------------------------|-----------------------|--------------------------|
| Most positive peak output | | 63 Volts | | Iout (A) | | 5.5 | | Freq. KHz | | 1.2 | | | | | |
| Most negative peak output | | -63 Volts | | | | | | | | | | | | | |
| DUAL | | Recommended for your use | | 83 Show me the best Amplifier | | | | | | | | | | | |
| Model | Vss Min | Vss Max | +Vs | -Vs | Iout Cont. Max A | Vdrop (Saturation V) | Common Mode V | Power Bandwidth KHz Typ | Slew Rate V/us Typ | Iq mA Max | Int. Power W Max | Pkg Style | Singles Price USD Domestic | Voltage Offset max mV | Eval Kit Sold Separately |
| SA60 | 0.1 | 80 | 66.3 | | 10 | 3.3 | | 25.0 | | 12 | 140 | SIP | \$ 134.95 | | EK06 |
| PA93 | 80 | 400 | 73.8 | -73.8 | 8 | 10.8 | 15 | 126.3 | 50 | 14 | 125 | SIP | \$ 202.05 | 10 | EK16 |
| PA04 | 30 | 200 | 69.9 | -69.9 | 20 | 6.9 | 8 | 126.3 | 50 | 90 | 200 | MO-127 | \$ 252.00 | 10 | EK04 |
| PA04+Vb | 30 | 200 | 67.6 | -67.6 | 20 | 4.6 | 8 | 126.3 | 50 | 90 | 200 | MO-127 | \$ 252.00 | 10 | EK04 |
| SA01 | 16 | 100 | 65.2 | | 20 | 2.2 | | 4.2 | | 78 | 185 | PD10 | \$ 375.00 | 10 | EK01 |
| SA12 | 16 | 200 | 64.8 | | 15 | 1.8 | | 2.3 | | 200 | 250 | MO-127 | \$ 481.50 | | EK17 |
| SA03 | 16 | 100 | 64.3 | | 30 | 1.3 | | 2.3 | | 73 | 300 | MO-127 | \$ 517.50 | | EK03 |
| SA04 | 16 | 200 | 64.8 | | 20 | 1.8 | | 2.3 | | 73 | 300 | MO-127 | \$ 517.50 | | EK03 |
| PA03 | 30 | 150 | 67.6 | -67.6 | 30 | 4.6 | 10 | 20.2 | 8 | 300 | 500 | MO-127 | \$ 525.00 | 2 | EK09 |
| SA06 | 16 | 500 | 70.7 | | 10 | 7.7 | | 2.3 | | 112 | 300 | MO-127 | \$ 628.50 | | EK05 |
| SA08 | 16 | 500 | 65.9 | | 20 | 2.9 | | 2.3 | | 90 | | MO-127 | \$ 634.20 | | EK15 |
| PA45 | 30 | 150 | 73.5 | -73.5 | 5 | 10.5 | 10 | 68.2 | 27 | 50 | 85 | TO-3 | \$ 44.80 | 10 | EK09 |
| PA46 | 30 | 150 | 73.5 | -73.5 | 5 | 10.5 | 10 | 68.2 | 27 | 50 | 75 | SIP | \$ 44.80 | 10 | EK12 |

Amplifier requirements have been entered into the yellow cells and the command button used to calculate suitability and sort by cost. For each parameter, the suitability ratio is 1 if the product meets (or exceeds) the requirements or is equal to requirement/capability. The sum of the ratios is used to sort the list.

In this example we see both switching and linear solutions meeting all the application requirements spanning more than a 4.5:1 price range. Vss min and max are data sheet specifications while +Vs and -Vs are estimations of supply requirements for this specific application (accounts for Vdrop or Saturation Voltage at the application output current). Note the blank cells where parameters do not apply to PWM amplifiers.

Here we find the SA60 is the “best” choice. However, the selection process knows nothing about noise tolerance of the application, space and weight limitations for heatsink and filter inductors, duty cycle of the output signal, accuracy requirements, military screening needs or - - - -. This is a good tool, but we still need an engineer to complete the job.

Even though Dilbert would have a fit, we may even find that talking to marketing would be a good idea. Note the last two lines where the output current spec is shaded because the amplifiers do not meet the application requirements. This indicates we may be able to reduce cost 3:1 if the output current specification could be reduced only 10%!

Apex Model Conventions

- PAxx Power Op Amp
 - No suffix Standard model
 - “A” suffix Improved performance via grade out
 - “M” suffix Military screened model
 - No design differences
- PBxx Power Booster
- SAxx Switching Amplifier (PWM)

The PA power op amps are indeed operational amplifiers following all the rules for these basic building blocks where in a properly designed circuit performance is controlled by feedback rather than op amp parameters.

The “A” suffix indicates electrical grade out for improved DC accuracy and sometimes voltage capability, temperature range or speed.

The “M” suffix indicates a part with identical design to the standard but with military screening added. Various models are offered as non-compliant (Apex verified), /883 (government verified) or SMD (government verified and controls the drawing).

The PB power boosters are a unique cost effective solution providing a programmable gain from 3 to 25 at voltages up to $\pm 150V$ and up to 2A. They are usually configured as the power stage of a composite amplifier which then acts like a power op amp. With the front end of the composite being a low cost typically $\pm 15V$ op amp, speed and accuracy are easily tailored to need of the application.

PWM amplifiers come to the rescue when internal power dissipation gets out of hand with linear devices.

ELECTRICAL LIMITATIONS


EFFECTS ON THE AMPLIFIER

- Slew Rate Limiting
- Output Saturation
- Current Limiting
- Shut Down
- Common Mode Requirements

Power amplifiers and small signal op amps share many limitations. Understanding the limitations of a standard op amp will help you design more accurate, reliable circuitry. It helps to have a good understanding of what happens to an amplifier when it operates outside of its linear region. Most of these electrical limitations can be traced to this common denominator.

NON-LINEAR OPERATION


OPEN LOOP MODEL

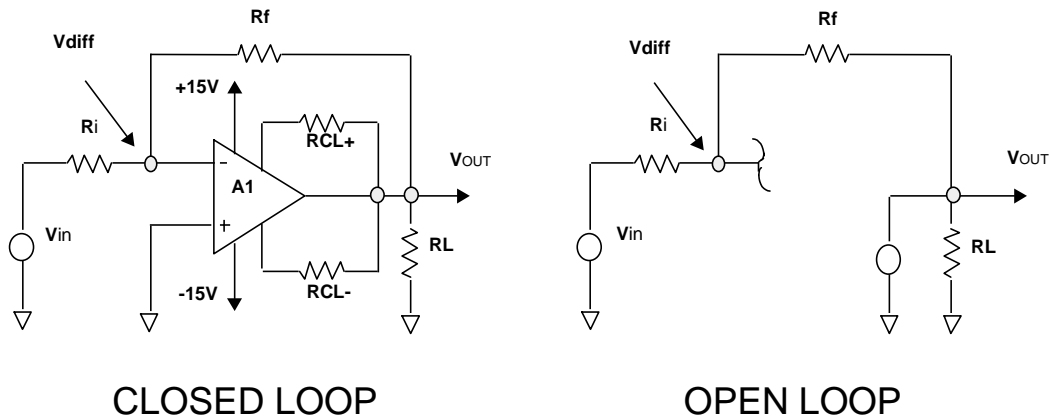


When an amplifier is operated in a closed loop it exhibits linear behavior. A violation of any of the limitations mentioned earlier will effectively open the loop. Once the loop is opened, V_{in} and V_{out} appear as two independent voltage sources. R_f and R_i function as a simple voltage divider between the two resistors. This voltage appears as a differential input voltage. In cases where the output stage is in a high impedance state, such as power off or thermal shutdown, V_{out} goes away and V_{in} is divided down by the series combination of R_{in} , R_f and R_{load} .

NON-LINEAR BEHAVIOR

SLEW RATE LIMIT

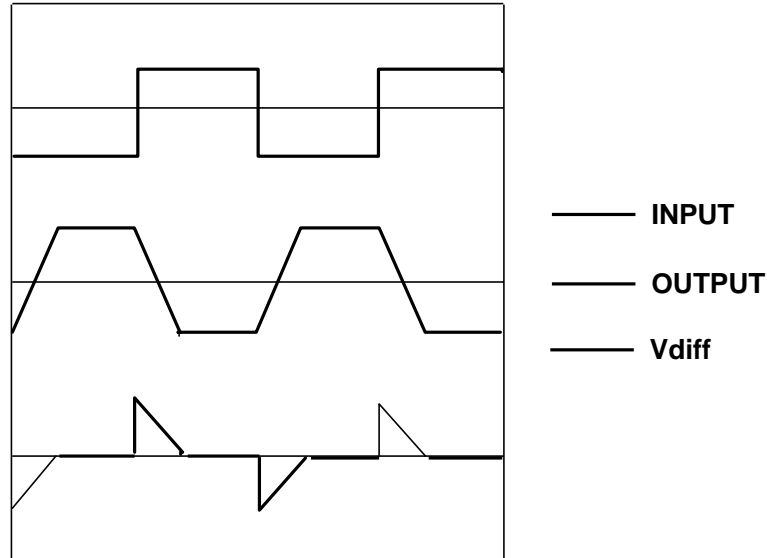


The effect of operating the amplifier in the slew limited region can be seen most dramatically by applying a step voltage to the input. Since the output of the amplifier cannot keep up with an infinite dV/dt , it goes into slew limited mode and begins changing its output voltage. At the point the amplifier goes into slew limit, we can use our "disappearing op amp" model to visualize what happens at the inverting input node of A1. In the example above, at $t=0+$, the input voltage has changed from +10 volts to -10 volts, but the output voltage has not yet changed from -10 volts. Therefore, -10 volts will be on both sides of the divider comprised of R_F and R_I . Since there is no voltage difference, the full -10 volts will appear as V_{DIFF} . As the output tries to "catch up", the right side of the divider will be changing linearly to +10 volts, therefore the differential voltage will drop linearly until the output catches up with the input. When the output catches up, the loop is closed and the differential voltage is zero.

 

Output saturation and current limit exhibit similar behavior — clipping on the amplifier output. This clipping produces differential input voltages.

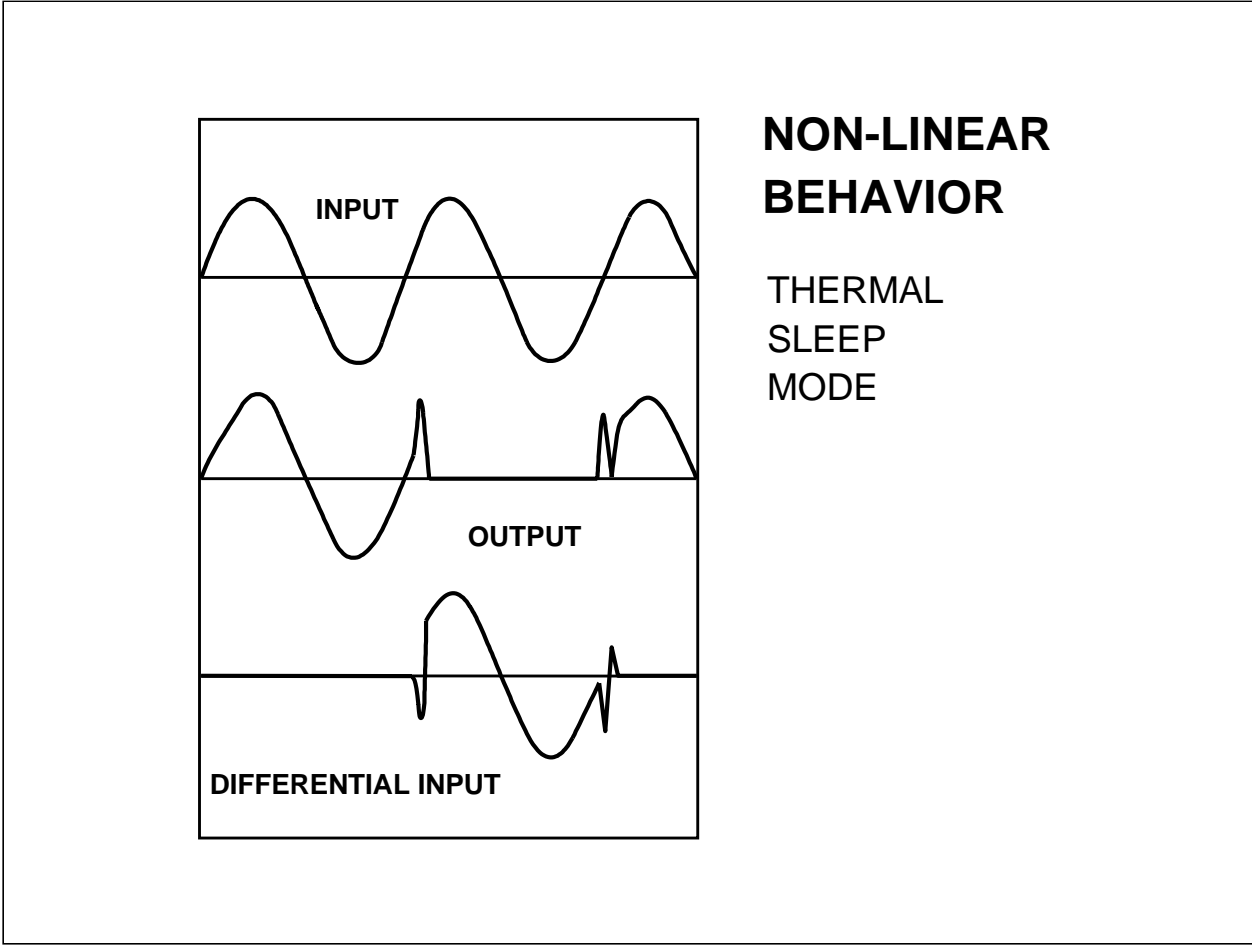
Any type of clipping can result in an overdriven condition internal to the amplifier. This can lead to recovery problems ranging from simple long recovery to ringing during recovery.



The situation with sleep mode is similar to thermal shutdown. In both cases, the amplifier is disabled by some circuitry which results in the output going into a high impedance state. One additional caution is that when coming out of sleep mode, an amplifier may saturate to one of the rails before recovering.

NON-LINEAR OPERATION

DETECTING PROBLEMS

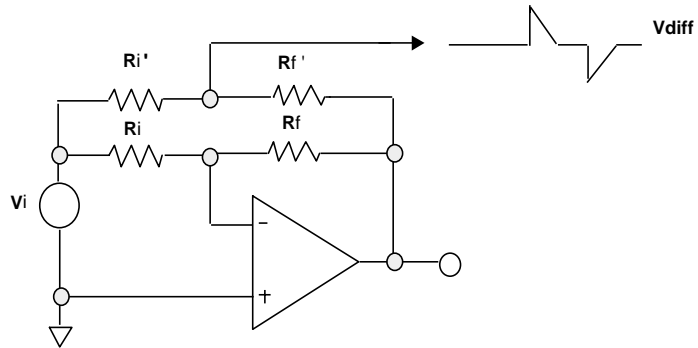

FALSE SUMMING NODE TECHNIQUE

The common denominator of all non-linear modes of operation is the appearance of differential input voltages. One method of sensing when an amplifier is in a non-linear region is to use this false summing node technique.

If $R_f'/R_i' = R_f/R_i$, then v_{diff} equals the voltage at the inverting node of the amplifier. This buffered error voltage signal can be used as an error flag possibly to drive a logical latch that could shut down the system.


ABS Maximums vs. the Spec Table

- ABSOLUTE MAXIMUM RATINGS
 - Stress levels, applied one at a time, will not cause permanent damage.
 - Does NOT guarantee op amp performance
- SPECIFICATIONS
 - Linear operation ranges
 - Vos, Ib, drift, CMRR... guaranteed performance

Beware that one stress level may bring on a second, which calls off all bets on op amp survival. Consider a commercial part where the last line of the specification table called "TEMPERATURE RANGE,case" is listed as -25/+85°C. Even though the ABS MAX temperature is 125°C, the part may latch up (very large voltage offset) at 86°C. With loads such as DC coupled inductors this may also lead to violation of the SOA.

COMMON MODE VIOLATIONS

GIVEN: V_{cm} RANGE = $\pm |V_s - 6|$

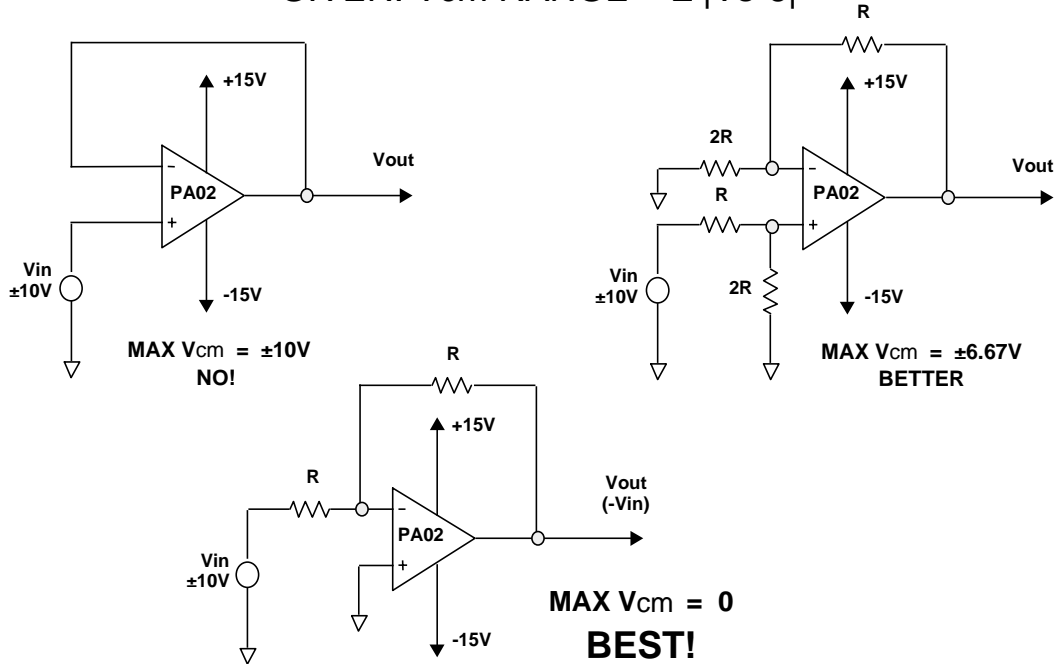

In an inverting configuration, the op amp's non-inverting terminal is usually tied to ground, making the inverting terminal a "virtual ground." This results in zero common mode voltage: a desirable benefit. However, operating the amplifier in a non-inverting mode results in the common mode voltage being equal to the voltage at the non-inverting terminal.

The schematics above illustrate the problem. The amplifier used in this example cannot have any common mode voltage that approaches within 6 volts of either supply rail. The first example shows a unity gain follower. This is the configuration where common mode violations are most common. Note that the input voltage is equal to the common mode voltage. In our example the input voltage exceeds the common mode range.

In the second example the input signal is first attenuated and then gained back up to result in a lower common mode voltage but a unity gain non-inverting transfer function. That is:

$$V_o = V_i \left(\frac{2R}{2R+R} \right) \left(1 + \frac{R_f}{R_i} \right)$$


where $R_f = R$ and $R_i = 2R$

The third example shows the best approach to eliminating common mode violations: use inverting configurations. In this case the input voltage is still 10 volts, the output voltage is 10 volts, but the common mode voltage is zero, eliminating the problem. Of course this does invert the phase of the output signal.

AMPLIFIER PROTECTION ELECTRICAL

- Input Transients
- Output Transients
- Over-voltage

WHY DIFFERENTIAL INPUT PROTECTION?

 


WHY DIFFERENTIAL INPUT PROTECTION?

Simple, to avoid damaging input stages due to differential overstress. Any input stage has maximum differential limits that can be exceeded any number of ways, with the most subtle occurring during non-linear operation.


In amplifiers with bipolar inputs, such as a PA12, differential overload has the additional hazard of causing degradation without catastrophic failure. Exceeding the reverse-bias zener voltage of a base-emitter junction of a transistor used in a differential amplifier can permanently degrade the noise, offset, and drift characteristics of that junction.

INPUT PROTECTION

DIFFERENTIAL

 

SIMPLE

 


ALLOWS OVERDRIVE


The protection scheme on the left uses parallel diodes to limit the differential voltage and uses series resistors to limit the current that flows through the diodes. The slightly more complicated scheme on the right accomplishes the same thing, but by using stacked diodes, allows a higher differential voltage to be developed. This allows a greater slew rate overdrive. The capacitors perform a similar function by allowing high frequency information to be passed directly to the input terminals.

GAIN SWITCHING

DON'T GET BURNED!

 

BAD

 


BETTER...


Often it is a requirement that the gain of an amplifier be switchable. This is very common in ATE applications. One method of doing this is shown on the left. This is a very poor way to accomplish gain switching. The problem is that the amplifier is usually much faster than the relay used to switch between the two resistors. **WHEN THE RELAY OPENS, THE AMPLIFIER HAS NO FEEDBACK.** Since the amplifier is now open loop, the amplifier will immediately slew toward one of the supply rails. By the time the relay closes, the amplifier will be saturated and the output voltage will appear directly at the inverting terminal of the amplifier.

The method on the right does not solve the problem, but it does provide amplifier protection. The parallel diodes clamp the differential input voltage while R_{ie} limits the amount of current that can flow during transient conditions. The value of R_{ie} should be chosen to limit the current to approximately 15mA with one full supply voltage across the resistor.

GAIN SWITCHING

 

GOOD

 


BEST

The "good" approach above represents a vast improvement over the previous technique. In this approach, gain is switched by switching the value of the input resistors rather than the feedback resistor. The major advantage to this approach is that the feedback loop is kept closed at all times. When the relay opens, the amplifier is now a unity gain follower with a zero volt input. The most voltage that will appear at the output is the offset of the amplifier. Input protection is still shown in this configuration to protect against possible switching transients.

The "best" approach above shows a configuration that prevents switching inside the feedback loop or opening up the input loop. R_{i1} and R_{f1} are in place at all times. The gain of the circuit is switched by EITHER switching in R_{i2} to parallel R_{i1} OR by switching in R_{f2} to parallel R_{f1} . This approach eliminates any transient voltages due to relay switching. At the time of contact closure, only the gain changes. Although input protection is still shown in this schematic, its only function is to protect the input in cases of non-linear operation, such as slew rate or current limit.

INPUT PROTECTION


OVERVOLTAGE

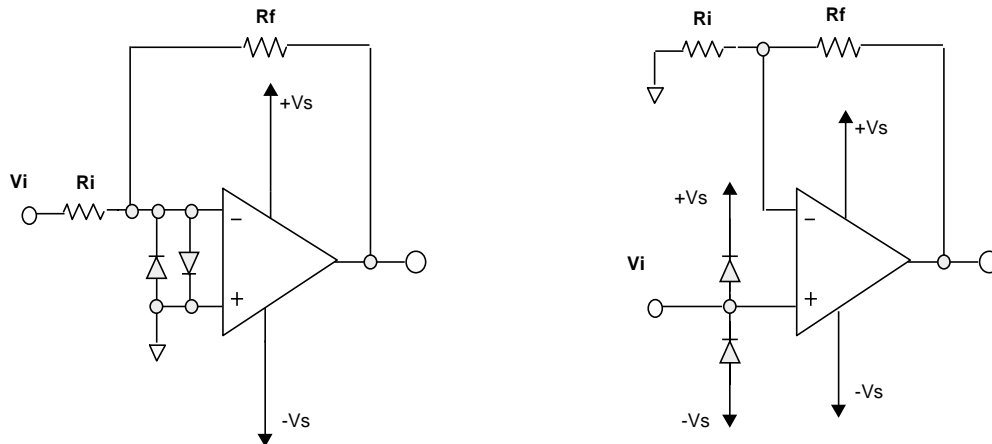

In multiple power supply systems, power supply sequencing is often a problem. If the power supplies for the "driving stage" come up before the "driven stage", the maximum input common mode specification may be violated. The diodes shown in the two circuits above serve to clamp the driven input to the amplifier supply pin so that the input cannot be raised above the supply voltage. Note, however, that if the supplies are in a high impedance state when the power supply is turned off, this approach will not protect the amplifier. Under those conditions however, the inverting amplifier configuration could be protected by running parallel diodes from the inverting node to ground. These would clamp the inverting input to ground under any circumstances. Since the inverting terminal is normally at virtual ground, these diodes would not interfere with signal in any way. However, on the non-inverting amplifier this approach will not work because the non-inverting input sustains a common mode voltage.

OUTPUT PROTECTION

KICKBACK / FLYBACK

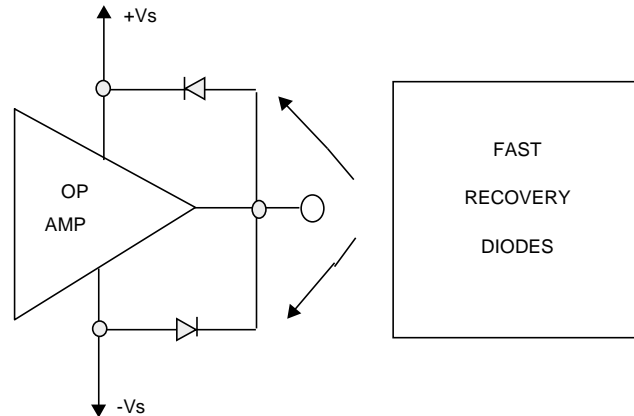

NOTE: SUPPLIES MUST BE ABLE TO ABSORB
TRANSIENT ENERGY, i.e.: LOW IMPEDANCE


Attempting to make a sudden change in current flow in an inductive load will cause large voltage flyback spikes. These flyback spikes appearing on the output of the op amp can destroy the output stage of the amplifier. DC motors can produce continuous trains of high voltage, high frequency kickback spikes. In addition, piezo-electric transducers not only generate mechanical energy from electrical energy but also vice versa. This means that mechanical shocks to a piezo-electric transducer can make it appear as a voltage generator. Again, this can destroy the output stage of an amplifier.

Although most power amplifiers have some kind of internal flyback protection diodes, these internal diodes **SHOULD NOT** be counted on to protect the amplifier against sustained high frequency kickback pulses. Under these conditions, high speed, fast recovery diodes should be used from the output of the op amps to the supplies to augment the internal diodes. These fast recovery diodes should be under 100 nanoseconds recovery time; and for very high frequency energy, should be under 20 nanoseconds.

One other point to note is that the power supply must look like a true low impedance source or the flyback energy coupled back into the supply pin will merely result in a voltage spike at the supply pin of the op amp again leading to an over voltage condition and possible destruction of the amplifier.

AMPLIFIER PROTECTION

OVERVOLTAGE

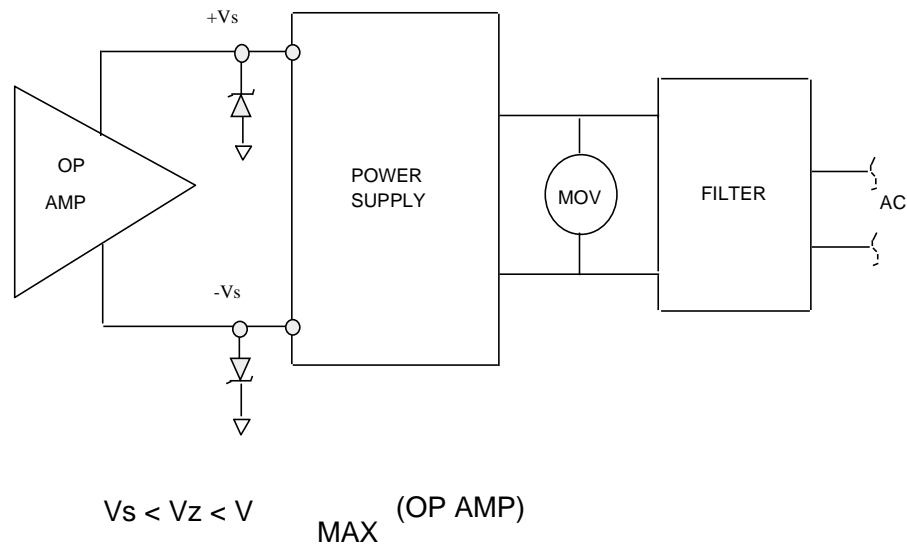


The amplifier should not be stressed beyond its maximum supply rating voltage. This means that any condition that may lead to this voltage stress level should be protected against. Two possible sources are the high energy pulses from an inductive load coupled back through flyback diodes into a high impedance supply or AC main transients passing through a power supply to appear at the op amp supply pins. These over voltage conditions can be protected against by using zeners or transorbs direct from the amplifier supply pins to ground. The rating of these zeners should be greater than the maximum supply voltage expected, but less than the breakdown voltage of the operation amplifier. Note also that MOS's can be included across the input to the power supply to reduce transients before they reach the power supply. Low pass filtering can be done between the AC main and the power supply to cut down on as much of the high frequency energy as possible. Note that inductors using power supplies will pass all high frequency energy and capacitors used in power supply are usually large electrolytics which have a very high ESR. Because of this high ESR, high frequency energy will not be attenuated fully and therefore will pass on through the capacitor largely unscathed.

SAFE OPERATING AREA OUTPUT STAGE DANGER!

- Current Handling Limitations
- Thermal (Power) Limitations
 - Steady State
 - Transient/Pulse Operation
- Second Breakdown
 - Bipolar Devices
 - MOSFETs: Not Applicable

USING THE SOA CURVE

 


Safe operating area curves show the limitations on the power handling capability of power op amps. There are three basic limitations.

The first limitation is total current handling capability. A horizontal line or the top of the SOA curve and represents the limit imposed by conductor current handling capability die junction area and other current density constraints. The second limitation is total power handling capability or power dissipation capability of the complete amplifier. This includes both of the power die and the package the amplifier is contained in. Note that the product of output current on the vertical axis and $V_s - V_o$ on the horizontal axis is constant over this line. For $T_C = 25^\circ\text{C}$, this line represents the maximum power dissipation capability of the amplifier with an infinite heat sink.

The third portion of the curve is the secondary breakdown areas. This phenomenon is limited to bipolar devices. MOSFET devices do not have this third limitation. Secondary breakdown is a combined voltage and current stress across the device.

Although the constant current boundary and the secondary breakdown boundary remain constant, the constant power/thermal line moves toward the origin as case temperature increases. This new constant power line can be determined from the de-rating curves on the data sheet. The case temperature is primarily a function of the heat sink used.

SOA STRESS CONDITIONS

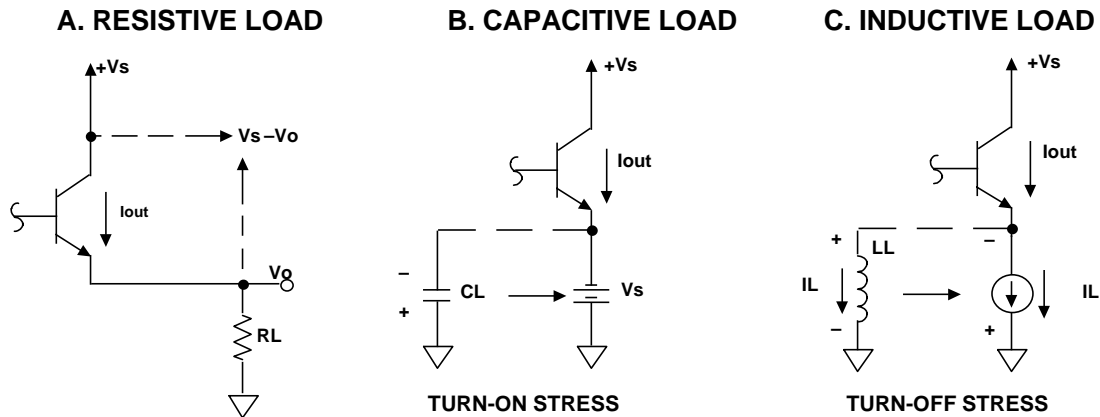


On the SOA graph, the horizontal axis, $V_s - V_o$ does not define a supply voltage or total supply voltage or the output voltage. IT DEFINES THE VOLTAGE STRESS ACROSS THE CONDUCTING DEVICE. Thus $V_s - V_o$ is the difference from the supply to the output across the transistor that is conducting current to the load. The vertical axis is simply the current being delivered to the load.

For resistive loads maximum power dissipation in the amplifier occurs when the output is 1/2 the supply voltage. This is because when the output is at 0 volts, no current flows from the amplifier whereas at maximum load current very little voltage is across the conducting transistor since the output voltage is near the supply voltage.

For reactive loads this is not the case. Voltage/current phase differences can result in higher than anticipated powers being dissipated in the amplifier.

An example of an excessive stress condition created by a capacitive load is shown in Figure B. In this case the capacitive load has been charged to $-V_s$. Now the amplifier is given a "go positive" signal. Immediately the amplifier will deliver its maximum rated output current into the capacitor which can be modeled at $t = 0$ as a voltage source. This leads to a stress across the conducting device of $I_{max} \times \text{total supply voltage}(2V_s)$.

Figure C shows a similar condition for an inductive load. For this situation we imagine the output is near the positive supply and current through the conductor has built up to some value I_L . Now the amplifier is given a "go negative" signal which causes the output voltage to swing to down near the negative supply. However the inductor at time $t = 0$ can be modeled as a current source still drawing I_L . This leads to the same situation as before, that is total supply voltage across a device conducting high current.

 

Current limit can be used to protect the amplifier against fault conditions. If, for instance, it is desired to protect the amplifier against a short-to-ground fault condition the $V_s - V_o$ number on the horizontal axis is equal to V_s since V_o is zero. Following this value up to the power dissipation limit and then across to the output current gives the value of current limit necessary to protect the amplifier at that case temperature. Note that better heat sinking allows higher values of current limit.

For more aggressive fault protection it may be desired to protect the amplifier against short to either supply. This requires a significant lowering of current limit. For this type of protection, add the magnitudes of the two supplies used, find that value on the $V_s - V_o$ axis, follow up to the SOA limit for the case temperature anticipated, then follow across to find the correct value of current limit.

It is often the case that requirements for fault protection and maximum output current may conflict at times. Under these conditions there are only four options. The first is simply to go the an amplifier with a higher power rating. The second is to trim some of the requirements for fault protection. The third is to reduce the requirement for maximum output current. The fourth option is a special type of current limit called “foldover” or “foldback.” This is available on some amplifiers such as the PA10 and PA12.

Current Limit Definition



A way to force output voltage where ever needed to maintain constant output current.

- **A non-linear mode of operation**
- **$V_{out} = f(I_{limit} \text{ and } Z_{load})$**
- **I_{limit} is only one term of the power equation**

Current limit circuits do what their name implies but they are not magic cures for all load fault conditions. The non-linear operation (the op amp is unable to satisfy input signal/feedback demands) means monitoring the inputs for the presence of a differential voltage will signal this mode of operation.

Usually the current limit mode will reduce the output voltage but this is not always true. To determine circuit survival the worst case voltage stress across the conducting transistor must be determined.


CURRENT LIMIT TWO RESISTOR AND FOLDOVER

  

The current limit is the first line of defense against SOA violations. Several different types of current limits are used. The first and most common type of current limit is the two resistor scheme shown above. In this scheme the current limit resistors perform a dual function. The first and primary function is to provide current limit but a secondary function is to provide local degeneration for the emitter followers in the output stage. In this scheme load current flowing from positive supply through Q2 and CL+ to the load will develop a voltage drop across RCL+. When this voltage drop reaches the base emitter turn on voltage of Q1 which is approximately .65 volts Q1 will turn on robbing base current drive through Q2.

The second type of current limit is called foldover or foldback current limit. It's available on the Apex PA04, PA05, PA10 and PA12. The circuit above shows only the positive half of a foldover current limit scheme. This type of current limit scheme works identically to the type just discussed for output voltages near zero. However, for high output voltages the dividing action of R1 and R2 requires that the voltage drop across RCL be slightly higher than before in order to turn on Q3. When energy is stored or produced in the load (reactive loads, motors, short to supply, active load circuits, et al) there will be times Q2 is conducting but output voltage is negative. In this case the divider action lower the current limit.

 Calculating current limit for Apex power op amps




The Ilimit sheet of Power Design.xls really shows the temperature variation. It's a good thing most of us don't have to cover -55° to 125°C. Not all op amps have this slope, but the spreadsheet knows the details of each model. Also enter your limit on junction temperature.

In the upper right, enter your maximum case temperature for the design then drop down and enter the desired current limit at high temperature to see the required resistor. Enter this as Rcl to see the graph. Note that the steady-state SOA curve has been adjusted to your max case and junction temperatures.


When analyzing an existing circuit, simply enter Rcl to see the graph. If the model you are using does not feature foldover current limit, don't worry about Rfo, any entry has no effect.

 Calculating current limit for Apex power op amps



Models featuring foldover current limit may be used in the fixed limit mode by entering ~100Mohms for Rfo. To use foldover enter the desired current limit at 0V output in the RCL calculator and then the desired current limit and voltage when swinging a signal below. If it is possible to meet this slope requirement, a value will be displayed for Rfo. Enter the two resistor values at the top to see the graph. Note that a new Rcl wattage for foldover operation has been calculated.

 This graph assumes dual supplies of maximum rating and charts voltage across the conducting transistor. In this graph, the 50V label corresponds to 0V output; the 10V label to 40V output.



Foldover current limit takes a fraction of the dynamic output voltage (relative to ground where the foldover resistor is connected) and combines it with the static V_{be} reference voltage setting current limit. While we often speak of THE current limit, there are actually two, one for the power transistor connected to the positive supply pin and another for the negative side.


The left half of this graph (labeled positive output) shows current limit when the output voltage and the power supply conducting the current are both on the same side of ground. This must be the case when the load is purely resistive and referenced to ground.

The right half of this graph (labeled negative output) shows current limit when the output voltage and the power supply conducting the current are on opposite sides of ground. This may be the case with reactive or EMF producing loads or if the load is referred to something other than ground.

The dynamic modification of current limit affects BOTH current limits. While one limit is increasing, the other is decreasing. This is a function of output voltage ONLY. If the decreasing side is allowed to reach zero, the amplifier may latch up. This means this graph should be checked for current limit crossing zero anywhere between plus and minus the maximum output voltage of the circuit.

With the graph extending to the full supply voltage spec in each direction, it can be used for any circuit from symmetric supplies to true single supply.

THERMO-ELECTRIC MODEL

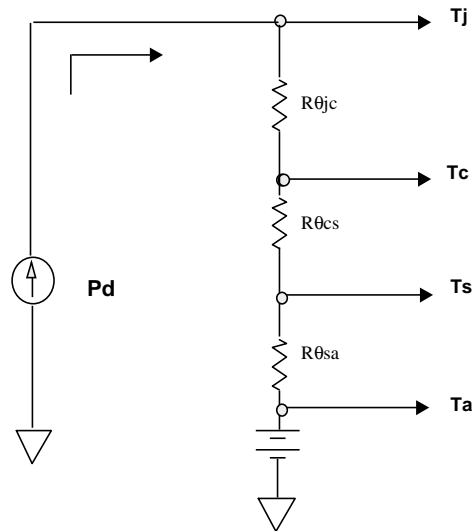

$$T_j = P_d (R_{\theta jc} + R_{\theta cs} + R_{\theta sa}) + T_a$$

The thermo-electric model translates power terms into their electrical equivalent. In this model, power is modeled as current, temperature is modeled as voltage, and thermal resistance is modeled as electrical resistance.

The real "name of the game" for power amplifiers is to keep T_j as low as possible. As you can see from the model, there are two approaches to doing this. The first is to reduce the current, ie; the power dissipation. The second is to reduce the thermal resistance.


Reducing power dissipation can be accomplished by reducing the supply voltage to no more than what is required to obtain the voltage swing desired. This reduces the $V_s - V_o$ quantity to as low a value as possible.

The thermal resistance problem should be attacked on all three fronts. R_{jc} , the thermal path resistance from the semiconductor junction to the case of the amplifier, is characteristic of the amplifier itself. The way to obtain maximum reliability and cool junction temperatures is to buy an amplifier with as low a R_{jc} as affordable.

R_{cs} is the thermal resistance from the case to a heat sink. This resistance is minimized by good mounting techniques such as using thermally conductive grease or an approved thermal washer, properly torqueing the package, and by not using insulation washers.

The last piece of the thermal budget is R_{sa} , the thermal resistance of the heat sink to ambient air. This is a very crucial piece of the puzzle and should not be skimmed on. A quick glance at an SOA curve that shows the difference between the power limitations of an amplifier with a 25° C case and an 85° C case shows the benefit of using the maximum heat sink allowable.

What is Tjmax?

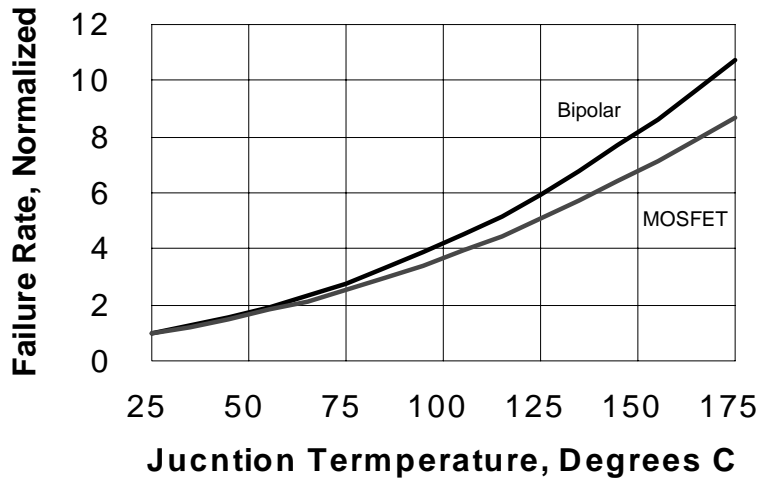

While this author would be the first to agree MIL-HDBK-217 has a few quirks and is very often misused, it does have the curves sloping in the right direction. Electronics is similar to your car, toaster- -almost anything: Run it too hot and it dies an early death. Apex suggests a maximum of 150°C for normal commercial applications. If the equipment is remotely located or down time is extremely expensive a lower temperature is appropriate.

This graph represents the temperature acceleration factors from revision F, Notice 2.

HEATSINK SELECTION

GIVEN: PA02 POWER OP AMP

$$P_d = 14 \text{ Watts}$$

$$T_a = 35^\circ \text{ C}$$

$$R_{jc} = 2.6^\circ \text{ C/W}$$

$$R_{cs} = .2^\circ \text{ C/W}$$

FIND: APEX HEATSINK TO KEEP $T_j = 100^\circ \text{ C}$

$$T_j = P_d (R_{jc} + R_{cs} + R_{sa}) + T_a$$

$$100^\circ \text{ C} = 14\text{W}(2.6^\circ \text{ C/W} + .2^\circ \text{ C/W} + R_{sa}) + 35^\circ \text{ C}$$


$$R_{sa} = 1.8^\circ \text{ C/W}$$

SELECT APEX HS03: $R_{sa} = 1.7^\circ \text{ C/W}$


This calculation illustrates the heat sink selection procedure using the thermal electric model discussed. First we calculate the power dissipation within the amplifier under worst case conditions. In this example, that number came out to 14 watts. Next we pick a desired value of T_j . In this example, we picked a very conservative value of 100° C . This value of T_j will result in a very large mean time to failure, spelling reliability for this application. Consulting the data sheet for the PA02, we find that the maximum DC thermal resistance from junction to case is $2.6^\circ \text{ C per watt}$. Next, we consult the APEX Data Book to determine that the typical case to heatsink resistance is between $.1$ and $.2^\circ \text{ C per watt}$, when thermal grease is used. Solving the given formula for the unknown, R_{sa} , we find that the required thermal resistance is less than or equal to $1.8^\circ \text{ C per watt}$. This can easily be achieved by using the Apex HSO3 Heatsink which has an RSA of $1.7^\circ \text{ C per watt}$.

If a system has forced air or a liquid cooling system available, physical size of the heatsink can be decreased. Heatsink data sheets often graph thermal resistance vs. air velocity. Fan data sheets usually speak of volume moved. At the very least a conversion is needed which takes in account the square area of the air path as it passes the heatsink.

POWER OP AMP “DC POWER DISSIPATION”

 

$$P_{dq} = [+V_s - (-V_s)][I_q]$$

 

$$P_{dout} = (+V_s - V_o)I_o$$

$$P_{dout(max)} = [1/2 V_s][I_o]$$

$$P_{dout(max)} = \frac{V_s^2}{4R_L}$$

$$P_{dtotal} = P_{dq} + P_{dout}$$


When calculating power dissipation in an amplifier, you **MUST NOT FORGET THAT POWER DISSIPATION IN THE AMPLIFIER IS NOT EQUAL TO POWER DISSIPATION IN THE LOAD.** That is, most of the time. One exception is when the output voltage is half of the supply voltage and the load is resistive. In this particular case the power dissipations are equal.

Calculating power dissipation in an amplifier under DC conditions with a resistive load is very simple.

The first portion of power dissipation is due to the quiescent power that the amplifier dissipates simply by sitting there with +Vs and -Vs applied. Multiplying total supply voltage by quiescent current gives the value of this power dissipation.

The maximum power dissipation in the amplifier under DC conditions with a resistive load is when the output voltage is 1/2 of the supply voltage. Therefore, whatever current is delivered to the load at 1/2 supply voltage multiplied by 1/2 supply voltage gives maximum power dissipation in the amplifier. The total dissipation is the sum of these two.

POWER OP AMP “AC POWER DISSIPATION”

 

$$Z_L = |Z_L|$$

$$P_{\text{dout(max)}} = \frac{2V_s^2}{\pi^2 Z_L \cos \theta}, \theta < 40^\circ$$

$$P_{\text{dout(max)}} = \frac{V_s^2}{2Z_L} \left[\frac{4}{\pi} - \cos \theta \right], \theta > 40^\circ$$


$$P_{\text{total}} = P_{\text{dout(max)}} + P_{\text{dq}}$$

With an AC output and/or reactive loads, output power dissipation calculations can get a bit stickier. Several simplifying assumptions keep the problem reasonable for analysis. The actual internal dissipation can be determined analytically or through thermal or electrical bench measurements. Both Application Note 22 and Application Note 1 General Operating Considerations give details on measuring AC power dissipation.

Worst case AC power dissipation formulae are given above for any reactive load range. With these worst case formulae one can calculate worst case power dissipation in the output stage for AC drive conditions and reactive loads. For most power op amps output stage power dissipation is the dominant component of total power dissipation so adding worst case AC output power dissipation with DC quiescent power dissipation and using AC $R_{\theta jc}$ thermal impedance for junction to case, will be sufficient for heatsink calculations.

More is not Always More

 - DC W.C.=50% of V_s
- R AC W.C.=63.7% of V_s
- Z AC W.C.>63.7% of V_s



Cranking the volume or the output up to maximum is not necessarily the worst case internal power dissipation for a linear output stage. We saw earlier that under DC and resistive load conditions, 50% of supply voltage was worst case.

As we progress to AC signals but the load remains resistive, worst case is when peak output is 63% of supply voltage. As we start adding reactive elements to the load the 63% figure starts increasing.

Is this chart saying reactive loads are the least demanding on the linear output stage?

No Way!

There are hidden scale changes in this chart. Assume the power scale is in actual watts and supply voltage is 1V. A resistor of 0.25Ω will generate the DC curve and maximum output power is 4W. Note that the heatsink calculation will use DC thermal resistance which is larger than AC thermal resistance. A resistor of 0.2027Ω will generate the AC resistive curve with a maximum output power of $\approx 2.47W$. A reactance of 0.637Ω will generate the AC reactive curve with a maximum output VA of only 0.785W.

Power Dissipation-the Easy Way

Power Design.xls

| Calculating Power Dissipation for Apex power op amps | | | | | | | | | |
|------------------------------------------------------|--------------|------------------------|----------|-----------|--|----------------|-----|---------|-----|
| Model | PA12A | Ta max = | 25 | | | Tj max= | 150 | Tc max= | 125 |
| Power for Sine Wave Outputs | | | | Note/PA46 | | | | | |
| Vs | 50 Volts | Note/PA21,5,6 | | | | | | | |
| Fmin | 0.005 KHz | Note/PA04,05 | | | | | | | |
| Fmax | 0.9 KHz | Bridge ckt? | | | | | | | |
| Sig | 45 Units | No | | | | | | | |
| Sig as ? | V peak | Note/W | | | | | | | |
| Res | 12.5 Ohms | # of Amps in parallel? | | | | | | | |
| Cap | 1E+11 uF | 1 | | | | | | | |
| Ind | 689 mH | | | | | | | | |
| Rcap | 0 Ohms | Unipolar or Bipolar? | | | | | | | |
| Rind | 0 Ohms | Bipolar | | | | | | | |
| Piq | 2.5 Watts | | | | | | | | |
| Read Me | | | | | | | | | |
| Resonant Frequency = | 6.06E-07 KHz | | | | | Max delta Tj = | 125 | | |
| At Fmax: | | At Fmin: | | | | Max delta Tc = | 100 | | |
| Xc hi = | 1.77E-09 | Xc = | 3.18E-07 | | | | | | |
| Xl hi = | 3896.203 | Xl = | 21.64557 | | | | | | |
| Notes: | Power Trial | | | | | | | | |

If your application can be modeled as a sine wave of any frequency, this sheet will tell you a lot. Entering a model pulls up a sizable portion of the data sheet for calculation and flag raising. Enter the three temperatures: ambient from the application, case per data sheet max or lower, and junction per contract or philosophy on reliability. If you need DC response, anything below 60Hz is OK. Define your output signal in terms of volts, amps or watts. If your load can be modeled by one of the first four diagrams, enter the values below. If you need diagram 5, use the Define Load command button.

Be sure to check these three cells!

If the Bridge circuit cell is “Yes”, the signal and load values specified will be treated as total but internal power will be for a single op amp.

Internal power will be divided by the # of parallel amplifiers.

“Unipolar” forces only one power supply and the use of DC thermal resistance.


A few useful pieces of information show up on this screen along with a red flag if your specified supply voltage is out of bounds. For more answers use the command button below the desired load diagram.

| | At Fmin: | At Fmax: | | At Fmin: | At Fmax: | |
|------------------------------|-----------|-----------|--------------------|------------------------|--------------|-----------|
| Z in Ohms | 15915.50 | 21.87 | | Maximum AC Pint | | |
| Phase angle | -89.95 | -46.70 | | 39.6 | 37.8 | Vpk |
| RMS Amperes | 0.0012218 | 0.8891318 | | 28.001429 | 26.728636 | Vrms |
| Peak Amperes | 0.0017279 | 1.2574223 | | 0.0017594 | 1.2221521 | Arms |
| RMS Volts | 19.445436 | 19.445436 | | 0.0492652 | 32.66646 | Wrms |
| Peak Volts | 27.5 | 27.5 | | 4.643E-05 | 22.404837 | Wtrue |
| RMS Power | 0.0237583 | 17.289557 | | 0.0633588 | 44.012142 | Pin |
| Peak Power | 0.0475166 | 34.579113 | | Minimum HS: | | 2.61 °C/W |
| Power factor | 0.001 | 0.686 | | Actual HS: | | 10 °C/W |
| Input power | 0.04 | 32.02 | | Results in Tjmax = | | 268.77 °C |
| True power | 0.00 | 11.86 | Results in Tcmax = | | 248.82695 °C | |
| Percent Efficiency = | 1.16 | 50.82 | TOO *@&# HOT!!!! | | | |
| Vpk capability = | 35.00 | 34.87 | | | | |
| Op amp internal dissipation: | | | | | | |
| Input power | 0.04 | 32.02 | | | | |
| Dissipation RMS | 0.04 | 20.16 | | | | |
| Dissipation Peak | 0.08 | 37.14 | | | | |
| Total in heatsink | 2.08 | 22.16 | | | | |
| WC watts & Rth | 22.161084 | 0.9 | 2.6074487 | 4.6405182 | 2.6074487 | |

If you're in a hurry, go to the right side just above the yellow box to find the smallest heatsink usable. Enter data sheet rating for selected heatsink to see maximum case and junction temperatures.

Since the low frequency load is so light we'll look at the high frequency numbers only. Below impedance & angle are the operating points of the load; amps, volts, watts and power factor. Next we find power being drawn from the supplies due to driving the load and true power dissipated by the load. This leads to efficiency (at your specified signal level). If the peak output capability based on the supply and output current is more than a few volts above required output, lowering supplies will reduce internal dissipation.

In the upper right, the worst case amplitude for your load is estimated (this amplitude varies with phase angle). Op amp RMS dissipation is calculated by subtracting true power from input power at worst case amplitude or your maximum level. Peak op amp dissipation is taken from the graph below. "Total in heatsink" uses peak if the frequency is below 60Hz (else RMS), then adds quiescent power. The last line picks worst case frequency and gives you power and thermal resistance for heatsink sizing. The three cells in the lower right are heatsink needed to keep the case cool, to keep the junctions cool without regard to the case, and the smaller of the two.

 

Remember transistor load lines from school? This is it and there should be no major surprises. At least none that we can't explain or fix.


The lack of an F_{min} curve in this example is because our load is completely off scale with peak current of only 1.7mA.

If one of the load lines peaks over the SOA curve remember we are looking at $\frac{1}{2}$ of a sine wave while the heatsink may have been sized on RMS values. If it looks like you have a lot of wasted power handling capability, go back and enter maximum case and junction temperatures calculated for the actual heatsink to be used.

Resistive Load Line Calculations

PA07
100Vs
37.3Ω
1.34A @ 50V
67W max

But.....

 


So, you've checked the maximum power dissipation at $\frac{1}{2}$ the single supply voltage and all is well (discounting the fact this example requires an infinite heatsink). The job is not over! At frequencies below 60Hz you do not to cross the second breakdown curve at all. At higher frequencies, keeping the duty cycle of these excursions down to 5% will keep you out of trouble.

When using dual symmetric supplies and pure resistive loads, all Apex power op amps are immune to this problem. For all other cases use Power Design.xls to plot sine wave load lines for you. This graph is from the power sheet but a trick had to be pulled to get a plot where output voltage is over 50% of the total supply voltage. In the Vs cell enter 100 volts and ignore the supply voltage warning. This is an illegal mode of operation as far as calculating power dissipation and heatsink size! **Do not use power & heatsink #s.** The graph and the load related data will be accurate.

Typical Load Line Calculation

PA12
±50Vs
45Vpk @ 5A
9Ω @ 60°
112VA → Load

But.....

 


Can a 125W, 10A device drive this 5A load? It's a large coil (250mH and 4.5Ω) and the frequency is only 5Hz. If efficiency were only 50%, delivering this 112VA to the load should be OK, shouldn't it? No. And no.

Phase shift is the killer here. You can see right away the load line exceeds the second breakdown curve. Look at current at the 56.2V stress level; its almost 4A (3.93 actually) giving peak dissipation of about 220W. Indeed, the data above this graph says the number is 223.5W (including I_q). We are in big trouble even though a 9Ω pure resistive load would have been fine with dissipation of only 72W and no hint of second breakdown problems.

It is time to look for a bigger amplifier or negotiate the load specifications.

Typical Load Line Calculation

 
PA12
±50Vs
45Vpk @ 1.8A
25Ω @ 60°
40VA → Load



Reducing the load requirements all the way to 25Ω produces a load line not in violation of the second breakdown curve and power dissipation in the amplifier is down to a manageable 82W.

The probability of negotiating load specs this far is rather dim. Its time to look at a bigger amplifier such as the PA05.

Multiple Reactive Elements

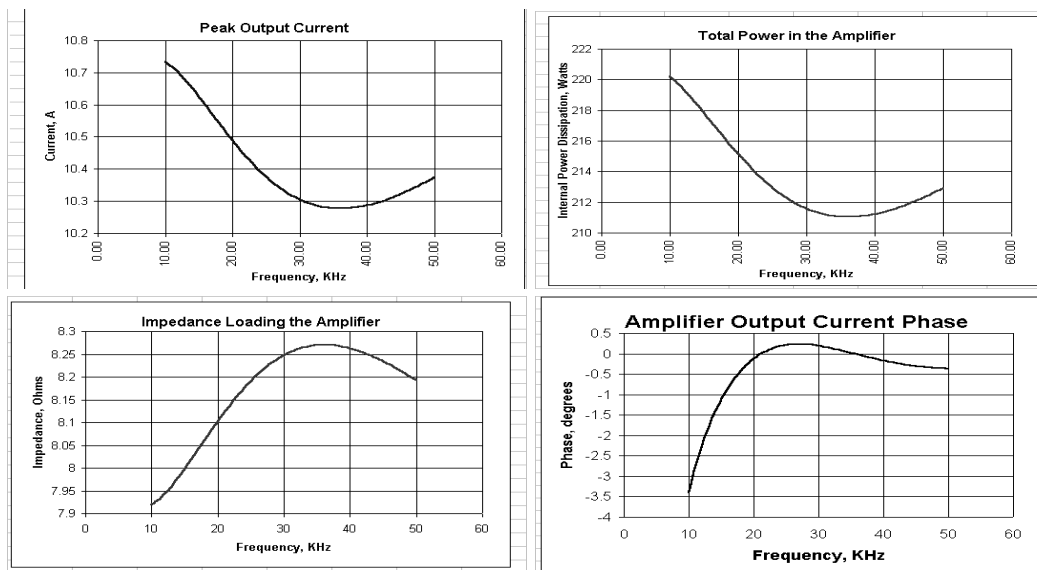

Any time an application has more than one reactive element, peak values of voltage, current, phase shift and power dissipation may not be at the minimum or maximum frequencies. It would be a good idea to run a frequency sweep to locate worst case operating points.

These graphs model operation of a tuned piezo load and the transmission line. In this case we find worst case power dissipation in the amplifier is at minimum frequency. Don't get caught by surprise with a complex load producing a power peak instead of a dip.

Thermal Capacity can be a Big Friend


- For pulse mode operation
- When pulses > 8ms
- Ap Note 11 Thermal Techniques
- Thermal response \cong to R-C response

$$\Delta V = V_s * (1 - e^{-t / RC})$$

$$\Delta \text{temp} = W * \text{Øhs} * (1 - e^{-t / \text{TAU}})$$

If the drive signal is pulse mode, internal power between pulses is zero and individual pulses are less than 8ms, size the heatsink by dividing the pulse power by the duty cycle and adding the quiescent power.

 For other pulse mode operations Application Note 11, Thermal Techniques, is the reference. It will explain how to calculate thermal capacity, thermal time constants and plot the charge/discharge curve. It also lists some common unit conversions and constants.



Key areas to check for proper mounting techniques:

- 1) Heatsink flatness.
- 2) Individual heatsink thru-holes for each pin.
- 3) Thermal interface between case and heatsink.
- 4) Mounting torque.
- 5) Sleeving on pins-thickness of heatsink

A detailed discussion of these areas follows.

MOUNTING CONSIDERATIONS

Heatsink surface smoothness is important to avoiding substrate cracking. While flatness in terms of total indicator runout (TIR) of 4 MIL/in. is adequate, and 1 MIL/in. preferred, any indentations, bumps or ridges, that protrude more than 0.5 mil can be a problem.

Once a proper heatsink selection is made it is essential to properly mount the amplifier. First, if you are drilling your own heatsink, drill 8 individual holes for each pin and deburr. Since the power die are located in the center of the pin circle, and this primary heat path is the shortest one, there must be plenty of heatsink mass in the center of the pin circle.


Next, the amplifier must have some media between it and the heatsink to insure maximum heat transfer. Thermally conductive grease is the oldest method to improve heat transfer, and continues to be among the best methods to reliably mount APEX power amplifiers and provide heat transfer along with avoiding problems with cracking the internal ceramic substrate.

Many customers prefer to avoid grease however. Thermally conductive washers must be approached with caution when used with APEX amplifiers. They must simultaneously provide the following attributes: 1. Good thermal conductivity. 2. Non-compressible. 3. As thin as possible and never over 5 mils thick. Power Devices Thermstrates easily meet these requirements and are available in the 8 pin TO-3 configuration. APEX stocks and sells them as our TW03 for TO-3 and TW05 for power dip packages. Power Devices Isostrates are thermally conductive washers suitable for those rare applications where electrical isolation is required (keep in mind that most APEX amplifiers have electrically isolated cases). Use of any other make/model of thermal washers voids any amplifier warranty.

Although not especially an issue during engineering bench testing, when mounting significant quantities of amplifiers in a production environment, use of a torque wrench is important. Proper torque ensures proper thermal conductivity without running the risk of cracking substrates..

Proper torque is defined as 4-7 in-lb for 8-pin TO-3 packages and 8-10 in-lb for power dip packages. This torque should be applied in 2 in-lb increments alternating between the two mounting bolts similar to when tightening lug nuts on a car tire.

Unless you can guarantee by mechanical design that shorts between pins and heatsinks are impossible, then it is wise to sleeve at least two amplifier pins. This will insure adequate alignment to prevent any possible shorting. Use 18 ga. tubing on TO-3 and 16 ga. tubing on power dip packages. Teflon covers all needs but other materials may work if they meet the mechanical, thermal and electrical breakdown requirements.

 


Properly applied grease results in good thermal performance. The operator variable shown above leaves the central area (where the heat is developed) with a high thermal path which led to amplifier destruction. Another variable to watch for is separation of the liquid from the solids in the grease. Too high a percentage of either can result in amplifier destruction due to thermal or mechanical stress. Buying thermal grease in a can or jar rather than a tube allows stirring to avoid the separation problem.

This slide also introduces the Apex failure analysis service. If you have an elusive problem, call us. We'll attempt to solve it over the phone. It's always good to have a schematic handy you can fax. If appropriate, we'll give you an RMA (return material authorization) to start a failure analysis. We will:

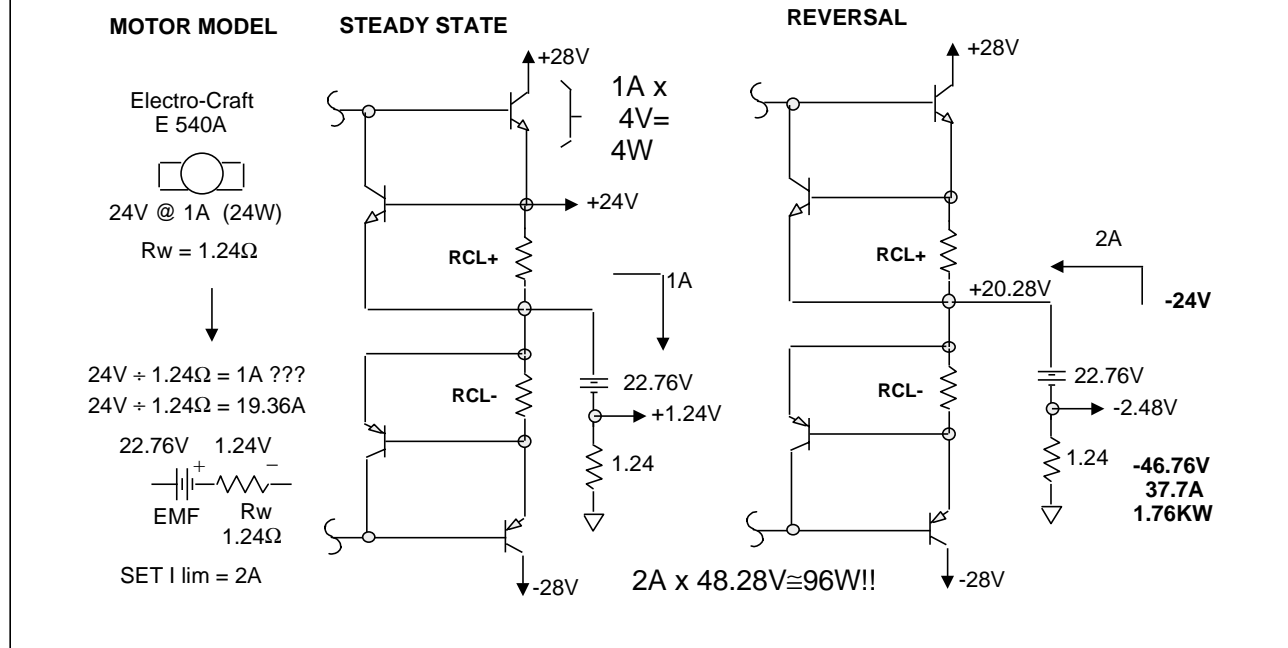1. Perform an external visual examination.
2. Test the part to all room temperature electrical specifications.
3. Delid and perform an internal visual.
4. Trouble shoot the circuit.

Many times the physical evidence helps pinpoint the problem. The location and nature of damage usually yields a suggestion on how to eliminate the problem.

MOTOR REVERSAL IS THE MOST DEMANDING LOAD CONDITION



A DC motor driven at 24V with 1A steady state current flow and a winding resistance specified at 1.24Ω can be modeled as a resistor in series with an EMF. In this example since the 1A drops 1.24V across the 1.24Ω, the remaining 22.76V is back EMF.

Under steady state conditions the motor voltage of 24V subtracted from the supply voltage of 28V leaves a 4V drop across the conducting transistor and a power dissipation of 4W.

When the amplifier is told to reverse the motor, the output of the amplifier attempts to go to -24V. If it could do so this -24V would add to the EMF of 22.76V to give -46.76V across the 1.24Ω resistor, resulting in a current flow of 37.71A. No way! Current limit is set at 2A.

When the current limit value of 2A flows across the winding resistance it drops 2.48V. The positive 22.76V of EMF is added to this negative 2.48V to give an output voltage of 20.28V. The difference between the output and the negative supply is now 28 - (-20.28) or 48.28V. That stress voltage on the conducting transistor means that the internal dissipation in the amplifier immediately after reversal is 48.28 volts * 2 amps or 96.56 watts!

This shows that a simple reversal can increase instantaneous power dissipation in the amplifier by over an order of magnitude. Judicious setting of current limiting and slowing the electrical response time will optimize reliability and mechanical response time.

Single Supply Operation


Advantages

Limitations

Special Considerations

The basic operational amplifier has no ground pin. It assumes ground is the mid-point of the voltages applied to the +Vs and -Vs pins. If voltages on the input pins deviate from the assumed ground, it labels this deviation as common mode voltage. If this common mode voltage is within the op amp's range and we don't ask the output to go out of range, the op amp is happy.

Head Room Required

 


Notice that as the input pins approach the negative rail, the voltage across Q15 decreases. Minimum operating voltages for Q12 and Q15 along with the zener voltage place a limit on how close common mode voltage can get to the negative rail.

With inputs going positive Q5, Q8, Q9 and D1 place a similar limit on how close common mode voltage can get to the positive rail.

On the output side look at a fraction of the D2 zener voltage plus Q16 operating requirements and the V_{be} of Q17 as all contributing to a limit of how close the output can approach the negative rail. This is the output voltage swing spec of the op amp. While this spec moves with output current, it never gets to zero even if current does. This means getting to zero output on a true single supply power op amp circuit is NOT going to happen.

While the actual voltages vary a lot, these type limitations are typical of all linear power amplifier output stages and most input stages. The Apex PA21, PA25 and PA26 family is an exception on the input side; common mode input goes below the negative supply rail making them ideal for some moderate power single supply applications.

Basic Single Supply Circuits

 


Circuit A is only suitable for unipolar and non-zero inclusive drives. These type applications might include Programmable Power Supply (PPS), heater controls and unidirectional speed controls.

Circuit B is practical only when the power supply has a mid-point capable of bi-directional current flow such as a stack of batteries. Even this is can be a problem due to battery impedance being in series with the load.

Circuit C is reasonably common in the audio world. Circuit D is sometimes used to reduce turn-on pops but must be matched to input signal circuits to be of much use.

 SINGLE SUPPLY NON-INVERTING CONFIGURATION



$$V_o = \frac{R_f}{R_i}$$

For $V_{in} = 0$

$$V_{cm} = \frac{V_s (R_i // R_f)}{R_b + (R_i // R_f)}$$

$$V_{cm\Delta} = \frac{V_{in} (R_b // R_f)}{R_i + (R_b // R_f)}$$

For $V_{in} > 0$


$$V_{cm} = V_{cm} @ V_{in} = 0 + V_{cm\Delta}$$

This configuration can easiest be viewed as a differential amplifier with an offset voltage summed in on both + and - input nodes. With this arrangement of resistors the transfer function is: $V_{out} = R_f/R_i V_{in}$.

R_b acts as a summation resistor to force the common mode voltage on the power op amp input to be within the common mode voltage specification. When $V_{in} = 0$, $V_{cm} = f(V_s, R_i, R_f \text{ \& } R_b)$. As V_{in} becomes greater than zero, one can easily calculate the change in common mode voltage using superposition. $V_{cm\Delta} = f(V_{in}, R_b, R_i \text{ \& } R_f)$. Adding these two functions produces V_{cm} for $V_{in} > 0$. Always check V_{cm} for entire range of V_{in} to guarantee common mode range compliance and thereby linear operation of the power op amp.


Inverting operation is actually easier. Simply move the signal source to the -side and ground the +side R_i . V_{cm} is set up in the same manner as above but there is no $V_{cm\Delta}$ to worry about at all. Since R_i and R_f will both go to ground, they could be replaced with a single resistor. For best accuracy keep two individual resistors; your are likely to get better ratios and tracking from +side to -side. Speaking of accuracy, model any current mismatch through the two R_b resistors as flowing through R_f producing an output error. Realize also that most current through R_b flows through the signal source producing an input error if the signal source is not zero impedance.

AIRCRAFT LIGHT DIMMER CONTROL

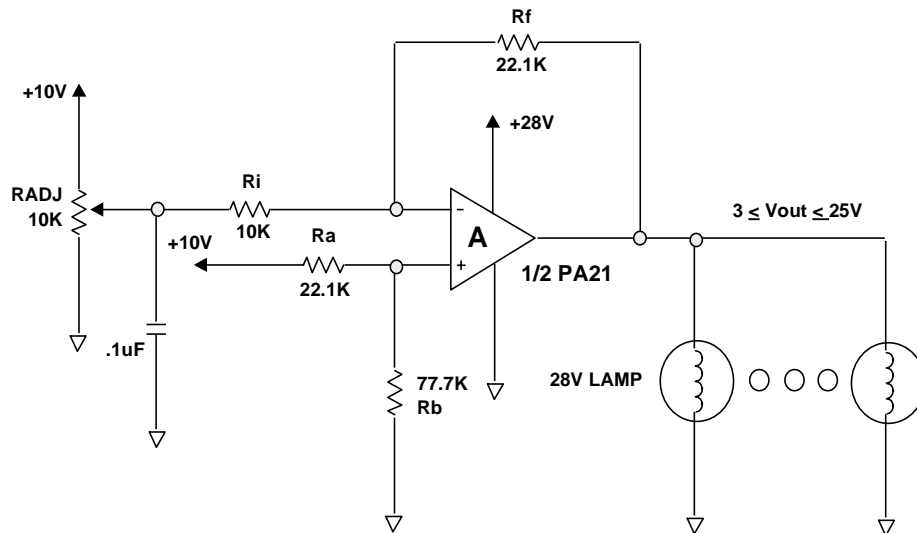

Accurate brightness control is provided in this aircraft panel light control circuit. A bank of several parallel connected lamps is driven by the PA21 which operates in a closed loop with a command voltage from a low power 10-turn pot. Offset is summed into the noninverting input of the PA21 to allow a zero to 10V input command on the inverting input to be translated into a 3 to 25V output voltage across the lamps. The 3V allowance for saturation voltage on the output of the PA21 assures an accurate low impedance output at 2.5 amps. The advantage of two power op amps in one package provided by the PA21 allows the design engineer to control two independent dimmer channels from one TO-3 power op amp package. The open loop gain of the PA21, along with its power supply rejection, force a constant commanded voltage across the lamps and thus a constant brilliance regardless of power supply line fluctuations, typical in an aircraft from 16 to 32 volts.

SINGLE SUPPLY— INVERTING

 

GIVEN: $V_s = 28V$
 $V_{in} = \pm 10V$
 $V_o = 6V \rightarrow 22V$

STEP 3: Offset: Set $V_{in} = 0, V_o = 14V$

$$V_o = -V_{in} \frac{R_f}{R_i} + \left\{ \frac{V_s R_B}{R_A + R_B} \right\} \left\{ 1 + \frac{R_f}{R_i} \right\}$$

FIND: Scaling resistor values

$$14V = 0 + \frac{R_f}{R_i} \left\{ \frac{28 R_B}{R_A + R_B} \right\} \left\{ 1 + \frac{R_f}{R_i} \right\}$$

SOLUTION:

$$\frac{R_B}{R_A + R_B} = .278 \rightarrow R_A = 2.6 R_B$$

STEP 1:

$$\text{Gain} = \frac{R_f}{R_i} \quad \text{Offset} = \left\{ \frac{V_s R_B}{R_A + R_B} \right\} \left\{ 1 + \frac{R_f}{R_i} \right\}$$

STEP 2:

$$\text{Gain} = \frac{V_o \text{ p-p}}{V_{in} \text{ p-p}} = \frac{16V}{20V} = .8$$

STEP 4: For minimum offset set

$$R_A || R_B = R_i || R_f$$


Choose $R_A = 16.2K, R_B = 6.19K$

$$\frac{R_f}{R_i} = .8 \quad \text{Choose } R_i = 10K \rightarrow R_f = 8.06K$$

STEP 5: Check for common mode:

$$V_{cm} = \frac{28 R_B}{2.6 R_B + R_B} = 7.78V (> 6V \rightarrow OK)$$

Ideal Single Supply Amplifier

 




The PA21 series amplifiers feature a common mode voltage range from 0.3V below the negative supply rail (ground in this case) to within 2V of the positive rail. These amplifiers also swing to about 0.5V of the rail with very light loads making the diode level shifter above quite practical as long as the load is resistive. With the diode inside the feedback loop it contributes essentially no errors at the load.

The non-inverting circuit shown is the most common but grounding the +input and using the -input in the normal summing junction fashion will work just as well.

PROTECTION ALTERNATIVES

CURRENT LIMITING PA21, PA25, PA26

NOTE:  → INVERTING GAIN
 → NO MOTORS

 

This handy circuit can be used with the PA21 series amplifiers in a single supply application to provide external current limit with minimum components.

By lowering the PA21 current limit one can keep the operating conditions of the PA21 within its SOA.

Q1 is the series pass element providing voltage to the PA21. During current limit we will limit the current to the load by reducing the supply rail. Ra provides a constant biasing current to the base of Q1. When the current through Q1 is sufficient enough to develop a .7V drop across Rcl Q2 turns on and starts to turn off Q1 until current into the PA21 drops below $I_{lim} = .7V/R_{cl}$. Rb and Cc insure the stability of the current limit circuit.


To avoid common mode violations on the input to op amp A and op amp B, as the supply rail is lowered during current limit, it is important to configure both op amp A and op amp B in an inverting gain configuration.

The maximum additional drop through the current limit circuit is 1.7V at up to 3A. This will reduce the maximum output voltage swing available from the PA21.

In a split supply application the negative current limit circuit would replace Q1 with a 2N6045 and Q2 with a 2N2222.

Asymmetrical Supplies

 - More common than true single supply
- Less accuracy hassles



There's something very appealing about a circuit with only two gain setting resistors. Many times there is already a low voltage supply in the system just waiting to be used. This supply need only provide quiescent current of the op amp unless the op amp swings negative or in the case of reactive loads where current and voltage are not in phase.

There is nothing magic about having a high positive supply and a low negative supply. As long as the lower voltage supply satisfies the common mode voltage requirement it makes no difference if you turn things over using high negative and low positive. If you are allowed to reverse the load terminals, this could work to significant advantage. Say that the small signal portion of the system runs on +12V or +15V and you need to buy a high power supply to drive the load anyway. If you set up a negative high power rail, the existing low power supply will work fine.

STABILITY AND COMPENSATION

- Ground Loops
- Supply Loops
- Local Internal Loops
- Coupling: Internal and External
- Aol Loop Stability

ELIMINATE COUPLING INTERNAL AND EXTERNAL

- Ground the Case
- Reduce Impedances
- Eliminate I_b Compensation Resistor on +IN
- Don't Run Output Traces Near Input Traces
- Run Iout Traces Adjacent to Iout Return Traces

1. Grounding the case forms a Faraday shield around the internal circuitry of the power amplifier which prevents unwanted coupling from external noise sources.

2. Reducing impedances keeps node impedances low to prevent pick-up of stray noise signals which have sufficient energy only to drive high impedance nodes.


3. Elimination of the I_b compensation resistor on the +input will prevent a high impedance node on the +input which can act as an antenna, receiving unwanted noise or positive feedback, which would result in oscillations. This famous I_b compensation resistor is the one from the +input to ground when running an amplifier in an inverting gain. The purpose of this resistor is to reduce input offset voltage errors due to bias current drops across the equivalent impedance as seen by the inverting and non-inverting input nodes. Modern op amps feature compensated input stages and benefit very little from this technique.

Calculate your DC errors without the resistor. Some op amps have input bias current cancellation negating the effect of this resistor. Some op amps have such low input bias currents that the error is insignificant when compared with the initial input offset voltage. Leave this +input bias resistor out and ground the +input if possible. If the resistor is required, bypass it with a $.1\mu\text{F}$ capacitor to ground.


4. Don't route input traces near output traces. This will eliminate positive feedback through capacitive coupling of the output back to the input.

5. Run Iout traces adjacent to Iout return traces. If a printed circuit board has both a high current output trace and a return trace for that high current, then these traces should be routed adjacent to each other (on top of each other on a multi-layer printed circuit board) so they form an equivalent twisted pair by virtue of their layout. This will help cancel EMI generated from outside from feeding back into the amplifier circuit.

GROUND LOOPS

 

PROBLEM

 


SOLUTION

$$f(\text{osc}) = \sim f(\text{unity})$$

Ground loops come about from load current flowing through parasitic layout resistances, causing part of the output signal to be fed back to the input stage. If the phase of the signal is in phase with the signal at the node it is fed back to, it will result in positive feedback and oscillation. Although these parasitic resistances (R_r) in the load current return line cannot be eliminated, they can be made to appear as a common mode signal to the amplifier. This is done by the use of a star ground point approach. The star point is merely a point that all grounds are referred to, it is a common point for load ground, amplifier ground, and signal ground.

The star ground point need to be a singular mechanical feature. Run each connection to it such that current from no other part of the circuit can mingle until reaching the star point. Don't forget your star point when making circuit measurements. Moving the ground lead around may change the indication leading to false assumptions about circuit operation.


SUPPLY LINE MODULATION

 

Supply loops are another source of oscillation. In one form of power supply related oscillations the load current flowing through supply source resistance and parasitic trace resistance modulates the supply voltage seen at the power supply pin of the op amp. This signal voltage is then coupled back into a gain stage via the compensation capacitor which is usually referred to one of the supply lines as an AC ground.

Another form of oscillatory circuit that can occur is due to parasitic power supply lead inductance reacting with load capacitance to form a high Q tank circuit.

BYPASSING SUPPLY LINES

 


C1 = 0.1 to 0.47 μ F, Ceramic
C2 = 10 μ F/Amp out (peak), Electrolytic

All supply line related oscillation and coupling problems can be avoided with proper bypassing.

The "must do" in all bypassing is a good high frequency capacitor right at each amplifier or socket power supply pin to ground. Not just any ground but the star point ground. This will most often be a multilayer ceramic, at least 1000pF, and as large as possible up to about 0.47 μ F. Above that capacitance high frequency characteristics shouldn't be taken for granted. Polyesterene, polypropylene, and mylar are possible alternatives when ceramics cannot be used for any reason. Check the manufacturer's data sheet for low ESR at least two times the unity gain bandwidth of the op amp being used.

Once high frequency bypassing is addressed, additional low frequency decoupling is advisable. In general use about 10 μ F/amp of peak output current, either electrolytic or tantalum type capacitors.

BIPOLAR OUTPUT STAGES

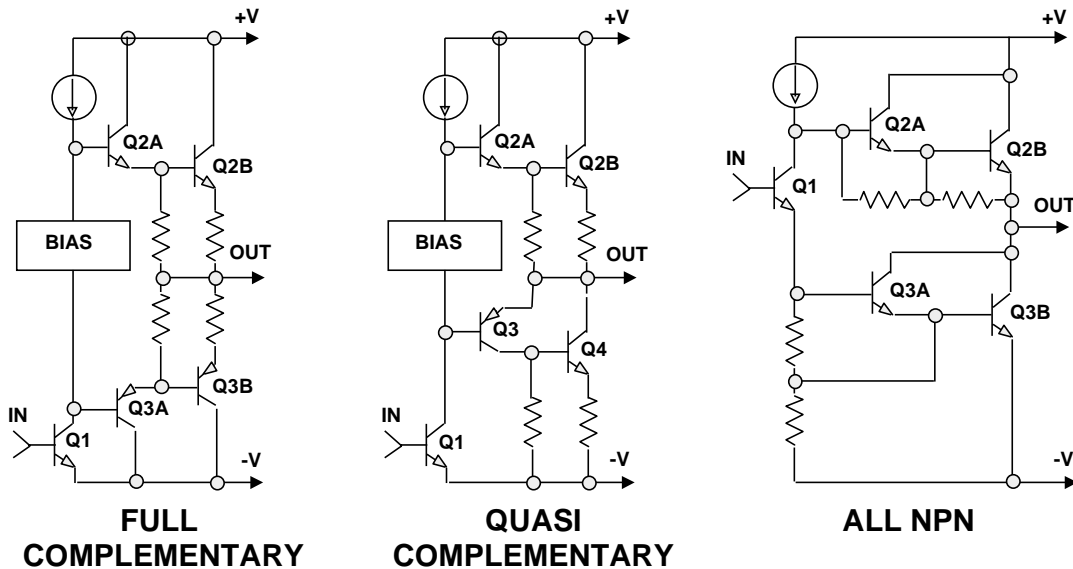


The full complementary output stage is a very easy to use stage. It exhibits symmetric output impedance and low crossover distortion. It is also easy to bias and is inherently stable under most load conditions. Q1 acts as a class A, high voltage gain, common emitter amplifier. Its collector voltage drives the output darlington. The bias circuitry provides class AB operation for the output darlington, minimizing crossover distortion. Both Q2 and Q3 are only called upon to provide impedance buffering. This is a unity voltage gain, high current gain stage. Both devices are operated as followers and thus provide very low output impedance for either sinking or sourcing current. Monolithic designers are constrained to work with NPN's for handling high currents. For this reason, the "all-NPN" output stage, followed by the "quasi-complementary" output stage were developed.

The quasi-complementary is similar to the full complementary in that Q1 again acts as a class A, common emitter, high gain amplifier and the output devices provide impedance buffering only. Q2 provides the same function as Q2 in a full complementary approach. Q3 and Q4 form a "composite PNP". The inherent problem with this approach is that there is heavy local feedback in the Q3, Q4 loop and this can lead to oscillations driving inductive loads.

The "all-NPN" output stage was an early approach to delivering power in a monolithic. During current source this stage operates much the same as the previous two. The major difference comes about during current sink. During the current sink cycle Q1 changes from a common emitter to an emitter follower. It now provides base voltage drive for Q3. Q3 is operated as a common emitter amplifier. The major disadvantage to this approach is the large changes in both output impedance and open loop gain between source and sink cycles. A problem common to both the quasi-complementary and the all NPN stage is the difficulty of biasing properly over extended temperature range.

FIXING OUTPUT STAGE OSCILLATIONS

 


$$F(\text{osc}) > f(\text{unity})$$


Any time you encounter an oscillation above the unity gain bandwidth of the amplifier it is bound to be one of the output stage problems discussed previously. These can be fixed through the use of a simple “snubber” network from the output pin to ground. This network is comprised of a resistance of from 1 to 100 ohms in series with a .1 to 1 uF capacitor. This network passes high frequencies to ground, thus preventing it from being fed back to the input.

Some manufacturers who use all NPN output stages in their monolithic power amplifiers suggest the use of this type of network to reduce output stage oscillations. Other manufacturers, while having a similar problem, never suggest that this type of network is necessary for proper use. Apex either takes care of the problem internally or specifies specific values for the external network.

LOOP STABILITY

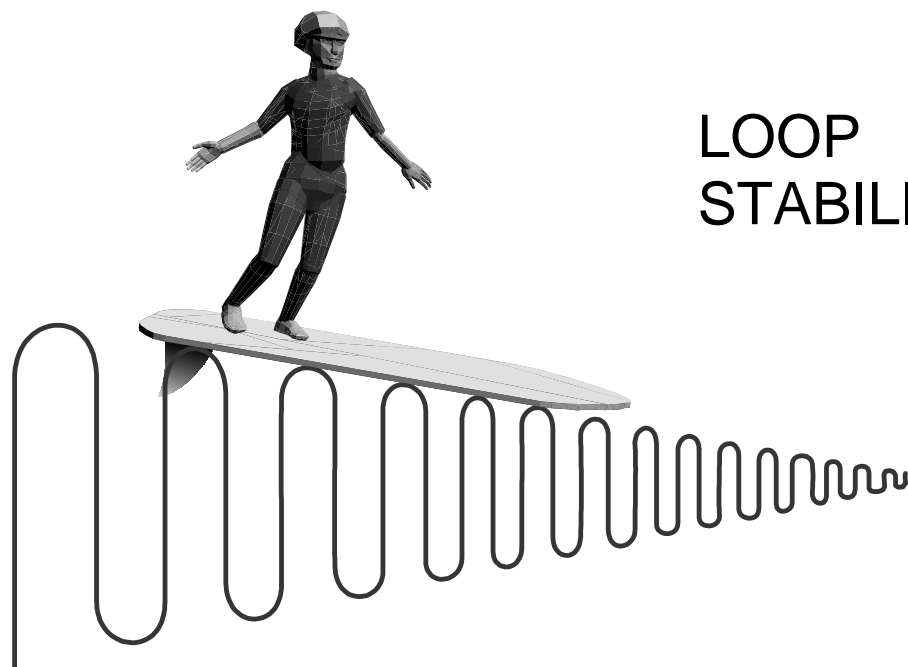


BETA (β) - FEEDBACK FACTOR

 

$$\beta = \frac{R_i}{R_i + R_f}$$

$$V_{fb} = \beta V_{out}$$

 

$$\frac{V_{out}}{V_{in}} = \frac{A_{ol}}{1 + A_{ol} \beta} = 1/\beta$$

(For $A_{ol} \beta \gg 1$)

$$V_{fb} = \frac{V_{out} R_i}{R_i + R_f}$$

$$V_{out} = V_{in} A_{ol} - A_{ol} \beta V_{out}$$

$$V_{fb} = \beta V_{out}$$

$$\frac{V_{out} + A_{ol} \beta V_{out}}{V_{in}} = A_{ol}$$

$$\beta = \frac{R_i}{R_i + R_f}$$


$$\frac{V_{out}}{V_{in}} \frac{A_{ol}}{1 + A_{ol} \beta} = \frac{1}{\beta}$$

(For $A_{ol} \beta \gg 1$)

Control theory is applicable to closing the loop around a power op amp. The block diagram above in the right consists of a circle with an X, which represents a voltage differencing circuit. The rectangle with A_{ol} represents the amplifier open loop gain. The rectangle with the β represents the feedback network. The value of β is defined to be the fraction of the output voltage that is fed back to the input. Therefore, β can range from 0 (no feedback) to 1 (100% feedback).

The term $A_{ol}\beta$ that appears in the V_{out}/V_{in} equation above has been called loop gain because this can be thought of as a signal propagating around the loop that consists of the A_{ol} and β networks. If $A_{ol}\beta$ is large there is lots of feedback. If $A_{ol}\beta$ is small there is not much feedback (for a detailed discussion of this and other useful topics related to op amps refer to: Intuitive IC Op Amps, Thomas M. Frederiksen, National's Semiconductor Technology Series, R.R. Donnelley & Sons).

RATE OF CLOSURE & STABILITY

 

* 20 db/ decade Rate of Closure → “Stability”


** 40 db /decade Rate of Closure → “Marginal Stability”

Aol is the amplifier’s open loop gain curve. $1/\beta$ is the closed loop AC small signal gain in which the amplifier is operating. The difference between the Aol curve and the $1/\beta$ curve is the loop gain. Loop gain is the amount of signal available to be used as feedback to reduce errors and non-linearities.

A first order check for stability is to ensure that when loop gain goes to zero, that is where the $1/\beta$ curve intersects the Aol curve, open loop phase shift must be less than 180 at the intersection of the $1/\beta$ curve and the Aol curve the difference in the slopes of the two curves, or RATE OF CLOSURE is less than or equal to 20 dB per decade. This is a powerful first check for stability. It is, however, not a complete check. For a complete check we will need to check the open loop phase shift of the amplifier throughout its loop gain bandwidth.


A 40 dB per decade RATE-OF-CLOSURE indicates marginal stability with a high probability of destructive oscillations in your circuit. Above examples indicate several different cases for both stable (20 dB per decade) and marginally stable (40 dB per decade) rates of closure.

EXTERNAL PHASE COMPENSATION

 

- ① Stable for any C_c
- ② Unstable for $C_c = 0\text{pF}$

——— Aol
 - - - - $1/\beta$
 AVcl

 


External phase compensation is often available on an op amp as a method of tailoring the op amp's performance for a given application. The lower the value of compensation capacitor used the higher the slew rate of the amplifier. This is due to fixed current sources inside the front end stages of the op amp. Since current is fixed, we see from the relationship of $I=CdV/dt$ that a lower value of capacitance will yield a faster voltage slew rate.

However, the advantage of a faster slew rate has to be weighed against AC small signal stability. In the figure above we see the Aol curve for an op amp with external phase compensation. If we use no compensation capacitor, the Aol curve changes from a single pole response with $C_c=33\text{pF}$ to a two pole response with $C_c=0\text{pF}$. Curve 1 illustrates that for $1/\beta$ of 40 dB the op amp is stable for any value of external compensation capacitor (20 dB/decade rate of closure for either Aol curve, $C_c=33\text{pF}$ or $C_c = 0\text{pF}$).


Curve 2 illustrates that for $1/\beta$ of 20 dB and $C_c=0\text{pF}$, there is a 40 dB/decade rate of closure or marginal stability. To have stability with $C_c=0\text{pF}$ minimum gain must be set at 40dB. This requires a designer to not only look at slew rate advantages of decompensating the op amp, but also at the gain necessary for stability and the resultant small signal bandwidth.

STABILITY – RATE OF CLOSURE

 

$$f_p = \frac{1}{2\pi R_f C_f}$$
 
$$f_z = \frac{R_i + R_f}{2\pi R_i R_f C_f}$$




The example above shows a typical single pole op amp configuration in the inverting gain configuration. Notice the additional Vnoise voltage source shown at the + input of the op amp. This is shown to aid in conceptually viewing the $1/\beta$ plot.

An inverting amplifier, with its + input grounded, will always have potential for a noise source to be present on the + input. Therefore, when one computes the $1/\beta$ plot, the amplifier will appear to run in a gain of $1 + R_f/R_i$ for small signal AC. The V_{out}/V_{in} relationship will still be $-R_f/R_i$.

The plot above shows the open loop poles from the amplifier's Aol curve as well as the poles and zeroes from the $1/\beta$ curve. The locations of f_p and f_z are important to note as when we look at the open loop stability check we will see that poles in the $1/\beta$ plot will become zeroes and zeroes in the $1/\beta$ plot will become poles in the open loop stability check.


Notice that at f_{cl} the RATE-OF-CLOSURE is 40 dB per decade indicating a marginal stability condition. The difference between the Aol curve and $1/\beta$ curve is labelled $A_{ol}\beta$ which is also known as loop gain.

STABILITY – OPEN LOOP

 

$$f_z = \frac{1}{2\pi R_f C_f}$$
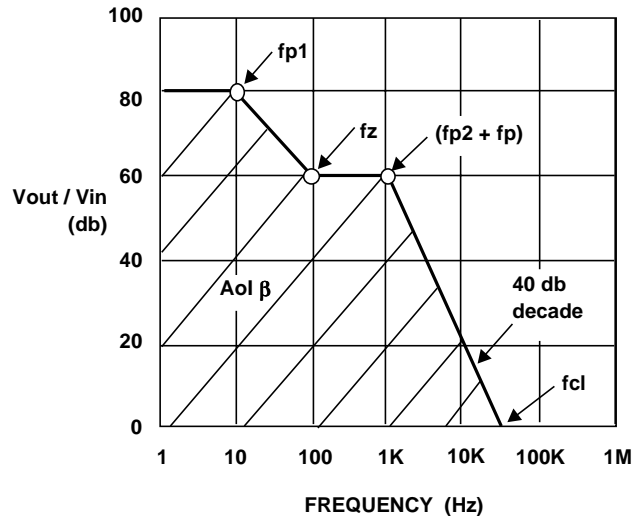
$$f_p = \frac{R_i + R_f}{2\pi R_i R_f C_f}$$




Stability checks are easily performed by breaking the feedback path around the amplifier and plotting the open loop magnitude and phase response. This open loop stability check has the first order criteria that the slope of the magnitude plot as it crosses 0 dB must be 20 dB per decade for guaranteed stability.

The 20 dB per decade is to ensure that the open loop phase does not dip to -180 degrees before the amplifier circuit runs out of loop gain. If the phase did reach -180 the output voltage would now be fed back in phase with the input voltage (-180 degrees phase shift from negative feedback plus -180 degrees phase shift from feedback network components would yield -360 degrees phase shift). This condition would continue to feed upon itself causing the amplifier circuit to break into uncontrollable oscillations.

Notice that this open loop plot is a plot of $A_{ol} \beta$. The slope of the open loop curve at f_{cl} is 40 dB per decade indicating a marginally stable circuit. As shown, the zero from the $1/\beta$ plot became a pole in the open loop plot and the pole from the $1/\beta$ plot became a zero. We will use this knowledge to plot the open loop phase plot to check for stability. This plotting of the open loop phase will provide a complete stability check for the amplifier circuit. All the information we need will be available from the $1/\beta$ curve and the A_{ol} curve.

V-I CIRCUIT & STABILITY

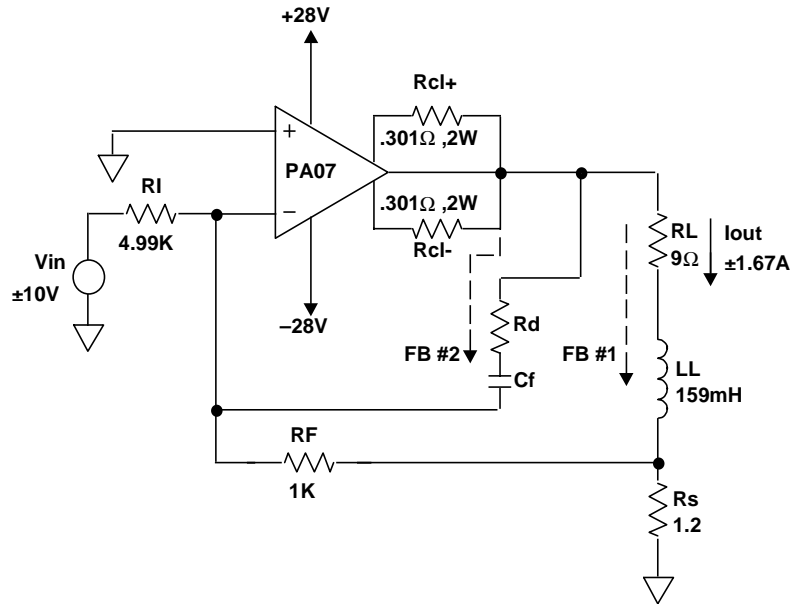

This V-I (Voltage to Current) topology is a floating load drive. Neither end of the load, series RL and LL, is connected to ground.

The easiest way to view the voltage feedback for load current control in this circuit is to look at the point of feedback which is the top of R_s . The voltage gain V_{R_s}/V_{in} is simply $-R_F/R_I$ which translates to $(-1K/4.99K = -.2004)$. The I_{out}/V_{in} relationship is then V_{R_s}/R_s or $I_{out} = -V_{in}(R_F/R_I)/R_s$ which for this circuit is $I_{out} = -.167V_{in}$.

We will use our knowledge of $1/\beta$, Rate of Closure, and open loop stability phase plots, to design this V-I circuit for stable operation. There are two voltage feedback paths around the amplifier, FB#1 and FB#2. We will analyze FB#1 first and then see why FB#2 is necessary for guaranteed stability.

PA07 Inductive Load Problem Entry



STABILITY FOR INDUCTIVE LOADS

| | | | | | | |
|-------|------|----------------------|-----|----------------|-------------------------------|----------------|
| MODEL | PA07 | Note/PBs | Rin | 4.99 Kohms | Estimated Closure Frequency = | 1 KHz |
| Rs | | 1.2 Ohms | Rf | 1 Kohms | Suggested maximum bandwidth | 316.2278 Hz |
| Load | | 159 mH | Cf | 9999 nF | Estimated Closure Rate = | 40.0 db/decade |
| Rload | | 9 Ohms | Rd | 99999999 Kohms | Estimated Phase Margin = | 0.41 Degrees |
| | | Is this a Composite? | No | | | |

Notes:

R-C Pole Calculator +:


| | | | | | | |
|--------------------|----------|-------------|------------|----------|-----------------------------|------------------------------------|
| 82 Kohms | Rd Kohms | 82.47245 | AC gain db | 40 | 28 Print Data, Bode & Phase | 29 Print Data, Bode, Phase & Parts |
| 32 Hz | Rd Kohms | 84.18197 | Rd Kohms | 82.47245 | | |
| 60.654 nF | Cf nF | 1.11E-06 | | | | |
| Ri/(Ri+Rf) | | 0.833055092 | | | | |
| Equiv Z @ Rs | | 1.199759647 | Ohms | | | |
| Requiv/(Ri+Requiv) | | 0.117626267 | | | | |
| DC Beta | | 0.09798916 | | | | |
| DC Gain | | 20.17643928 | db | | | |
| Zero R/L | | 10.20969916 | Hz | | | |
| Rin Rf | | 0.833055092 | Kohms | | | |
| Zero Rd/Cf | | 1.59171E-08 | Hz | | | |
| AC Gain | | 181.5865255 | db | | | |
| Zero Cross | | 1000 | Hz | | | |

  

The Load sheet of Power Design.xls will handle inverting or non-inverting circuits. In this example we can enter our component values in a straight forward manner. For non-inverting circuits you probably want to enter $\cong 100M$ for Rin. To illustrate the basic problem with inductors inside the feedback loop we enter high values for the R-C stabilizing network.

Notice first on the right, rate of closure and phase margin are both not acceptable. Back to the right and down a little is a handy calculator for analyzing and selecting component values. To the right are two suggestions for the value of Rd and one for Cf. More to the right we find a yellow entry cell for setting Rd for a specific AC gain. Below this are listed several operating points of the circuit. The liberal scattering of red triangles are notes of explanation (brought up by cursor placement). Application Note 19, Stability for Power Amplifiers is the reference to consult for detailed information.

Aol & FB#1 Magnitude Plot for Stability

 


As frequency increases, impedance of the inductor increases and being inside the feedback loop it is causing closed loop gain to increase. Another way to view it: The amplifier's job is to drive constant current but as frequency goes up it needs more voltage to maintain that constant current, so voltage gain is increasing with frequency.

Open loop gain is decreasing 20db per decade and closed loop gain is increasing 20db per decade. This intersection rate of 40db per decade is the problem.

What if we could invent a circuit to make the open loop gain stop increasing? The precise function of feedback path #2! As soon as we enter this in the data entry screen, we see 20db per decade and phase margin of 45°.


Aol & FB#2 Magnitude Plot for Stability

 


Here's a way to start:

1. Select R_d for an AC gain either 20db below gain at the intersection or 20db above the DC gain of the current feedback (Path 1). These two points are the two suggested R_d values on the data entry screen. We can also read 40db from the graph and enter it as AC gain. An 82K should work well.
2. Select C_f for a corner frequency $\frac{1}{2}$ to 1 decade below the intersection frequency. Giving the calculator pad 82K and 30Hz allows it to suggest a standard value of 68nF (with a little help from you). After entering 82K for R_d , the data entry screen will suggest a capacitor based on 1 decade below the intersection frequency.
3. Play "what if" with the circuit.
4. If trying to achieve higher bandwidth, try increasing the value of R_s .

Phase Plot for Stability

 


Phase Shift Components

 

Here are all the pieces going into the previous phase plot. Again, Application Note 19 is the reference.


CAPACITIVE LOADING

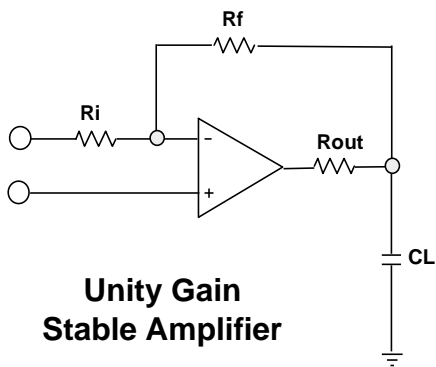

**Unity Gain
Stable Amplifier**

**Unstable
40db/decade
with CL**



 
- Aol
- Aol with CL
- 1/β
- Acl
- Stable
- Unstable



Even when using a unity gain stable amplifier, capacitive loads react with amplifier output impedance, which has the effect of introducing a second pole into the amplifier response which occurs below the unity gain crossover frequency.

If the amplifier is used at a low enough loop gain, this will result in the unstable condition shown in this graph. One simple solution is to increase the closed loop gain again.

CAPACITIVE LOAD COMPENSATION

  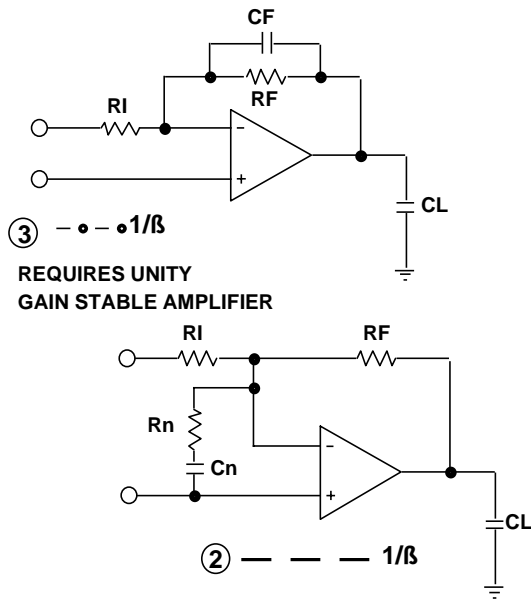



If it's necessary to use low gains with capacitive loads, or in the unlikely event they are a problem at higher gain, these techniques can help solve stability problems caused by capacitive loads.

Method 1 uses a parallel inductor-resistor combination in series with amplifier output to isolate or cancel the capacitive load. Feedback should be taken directly from the amplifier's A_{ol} output. In the graph, this has the effect of restoring the amplifier response to 20db/decade. This method has the advantage that with proper component selection, it can produce an overdamped or critically damped response to a square wave. The inductor is typically 3 to 10 μ H, and the resistor from 1 to 10 ohms; although a higher voltage, lower current amplifier like PB58 needs about 35 μ H and 20 Ω .

Method 2 uses "noise gain compensation" to enhance stability. This method will work in virtually all cases. The idea is to set the ratio of RF/Rn for a gain high enough to insure crossing the A_{ol} line at a stable point. The capacitor, Cn , is selected for a corner frequency one-tenth the A_{ol} crossover.

Method 3 uses a capacitor in the feedback path to cause a phase lead in the feedback which cancels the phase lag due to capacitive loading. This technique requires careful selection of capacitor value to ensure $1/\beta$ crosses the modified A_{ol} before unity gain, unless a unity gain stable amplifier which has a good phase margin is used.

NOISE-GAIN COMPENSATION

  

This plot illustrates how Noise Gain Compensation works. One way to view noise gain circuits is to treat the amplifier as a summing amplifier. There are two input signals into this inverting summing amplifier. One is V_{in} and the other is a noise source summed in via ground through the series combination of R_n and C_n . Since this is a summing amplifier, V_o/V_{in} will be unaffected if we sum zero into the R_n - C_n network. However, in the small signal AC domain, we will be changing the $1/\beta$ plot of the feedback as when C_n becomes a short and if $R_n \ll R_i$ the gain will be set by R_f/R_n . The figure above shows the equivalent circuits for AC small signal analysis at low and high frequencies.

Notice in the plot above that the V_o/V_{in} relationship is flat until the Noise Gain forces the loop gain to zero. At that point, f_{cl} , the V_o/V_{in} curve follows the A_{ol} curve since loop gain is gone to zero. Since noise gain introduces a pole and a zero in the $1/\beta$ plot, here are a few tips to keep phase under control for guaranteed stability. Keep the high frequency, flat part of the noise gain no higher in magnitude than 20dB greater than the low frequency gain. This will force f_p and f_z in the above plot to be no more than a decade apart. This will also keep the open loop phase from dipping below -135 since there is usually an additional low frequency pole due to the amplifier's A_{ol} already contributing an additional -90 degrees in the open loop phase plot. Keep f_p one-half to one decade below f_{cl} to prevent a rate of closure of 40dB per decade and prevent instability if the A_{ol} curve shifts to the left which can happen in the real world.

Usually one selects the high frequency gain and sets f_p . f_z can be gotten graphically from the $1/\beta$ plot. For completeness here are the formulae for noisegain poles and zeroes:

$$f_p = \frac{1}{2\pi R_n C_n} \qquad f_z = \frac{R_f + R_i}{2\pi (C_n) (R_f R_i + R_f R_n + R_i R_n)}$$


PA07 with a BIG Load

| STABILITY FOR CAPACITIVE LOADS | | | | 45 Goto Composite | | |
|--------------------------------|------|---------------|------|-------------------|-------------------------------|------------------------------------|
| MODEL | PA07 | Note/PBs | Rn | 99999999 Kohms | Estimated Closure Frequency = | 36.51741 KHz |
| Rcl | | 0.4 Ohms | Cn | 0 nF | Suggested maximum bandwidth | 8.659643 KHz |
| Cload | | 4 uF | Cf | 0 pF | Estimated Closure Rate = | 40.0 db/decade |
| Rin | | 2 Kohms | Riso | 0 Ohms | Estimated Phase Margin = | 25.8688 Degrees |
| Rf | | 20 Kohms | | | | |
| Notes: | | | | | | |
| R-C Pole Calculator: | | | | | 28 Print Data, Bode & Phase | 29 Print Data, Bode, Phase & Parts |
| 20 Kohms | | 0.1 Kohms | | 30 KHz | | |
| 20 KHz | | 10 nF | | 4 uF | | |
| 0.3979 nF | | 159.15494 KHz | | 1.326291192 Ohms | | |
| Total Rout | | 2.9 Ohms | | | | |
| Pole Zout/Cloud | | 13.720253 KHz | | | | |
| 1/Beta (DC) | | 20.8 db | | | | |
| Noise Gain | | 0.0 db | | | | |
| Pole Noise Gain | | 15.915494 KHz | | | | |
| Zero Noise Gain | | 15.915487 KHz | | | | |
| Pole Cf/Rf | | 7.958E+09 KHz | | | | |
| Zero Rf/Cf | | 8.754E+10 KHz | | | | |
| Zero Riso/Cloud | | 3.979E+09 KHz | | | | |
| Page Down for Plots. | | | | | | |

This basic circuit will demonstrate how each of the capacitive load compensation techniques can work independently to solve the large C load stability problem.

This screen sets up the problem. Enter values describing the circuit being sure to assign *open* values to components not yet in the circuit. To the right we see a 40db closure rate and less than 30° phase margin. We don't need them yet but please note the three windows of the R-C Pole Calculator. The first window tells us 398pF will yield a pole at 20KHz when paralleled with 20K. The last window tells us 1.3Ω will place the corner frequency at 30KHz when in series with 4μF.

PA07/Cload Problem

 


This picture is the first part of the problem. The output impedance of the PA07, plus the current limit resistor along with the big capacitive load, have added an additional pole to the open loop response of the amplifier. This degrades closure rate to 40db per decade--a warning flag. Its too bad we can't use a gain of 100 (40db) where closure rate would have been OK.

Here's the beauty of this system: Visualize or hold anything with a straight edge up to the graph in the area where we just learned a roll-off capacitor fixes these problems. Hold the edge parallel to the original open loop response curve and move it around to achieve intersection with the modified response about 1/2 way between 0 & 20db. Read the frequency where the straight edge crosses 20db. Remember the 20KHz in the R-C Pole Calculator? This is the origin. The spreadsheet makes it very easy to play "what if".


For noise gain compensation, visualize the upper flat portion of the curve being 20db up from the DC gain. Setting $R_n = R_{in}/9$ will put you about where it should be. On the open loop gain curve, read frequency where the imaginary line crosses. Enter one tenth this frequency and the R_n value in the R-C Pole calculator to set C_n . Again, play what if to optimize the circuit.

For Riso pick a frequency a little lower than the intersection of DC gain and the modified open loop gain. It looks like 30KHz is about as high as we should go. Use the R-C Pole Calculator, plug in values and optimize.

PA07/Cload Cf Solution

 

PA07/Cload Noise Gain Solution

 


An important point one more time:

The closed loop curves here $1/\beta$ curves.

They are obviously related to signal gains but are stability analysis tools which always assume non-inverting gain. A signal gain of -1 will plot as 2 in $1/\beta$ format. The signal gain does not increase between 150Hz and 1.5KHz.


PA07/Cload Riso Solution

 

Notice the difference between the curve showing the Signal at Clload and the Acl curve. This is the voltage loss across Riso which is outside the feedback loop and therefore not corrected for amplitude loss. The picture says we really aren't losing much at usable frequencies. Lets look at another error between 10KHz and closure frequency.

Op amp theory says output impedance is reduced by the loop gain. Our data entry screen told us Zout for the PA07 was 5Ω. This graph tells us loop gain goes from 10 to zero in our band of interest. This means uncorrected output impedance goes from 0.5 to 5Ω in this band. The losses across the 1.2Ω Riso now seem even more trivial.


PA07/Cload Riso Phase

 

The first thing usually pulled from this graph is phase margin; 45° is good, 30° is pushing things. Here we see the open loop phase crossing Fcl (closure frequency) at $107\frac{1}{4}^\circ$ (Excel97 gives you the number if you place the cursor on the curve). Phase margin = 180° - open loop phase shift, or 72.75° in this case.


Sometimes we need to know the closed loop phase shift at a particular frequency. Suppose 1KHz is the point of interest. We can tell from the un-scaled curve this shift is not zero but resolution stinks. The curve with best resolution at 1KHz is the one scaled times 100. This curve crosses 1KHz at 158.66° for an open loop phase of about 1.6° .

PA07/Clod Riso Phase Components

 

Here are all the pieces making up the total open loop phase shift. Each segment is based on component values and the plotting rules detailed in Application Notes 19 and 25. P1 Phase (first pole in the bode plot) appears to be missing. Power Design shows only one curve when two or more coincide. Notice that P1 Phase does show up roughly between 1KHz and 100KHz. Open loop Phase is simply the sum of all the segments. Some segments show only partially or not at all because they are off scale, usually because of the *open* values entered.

Errors of Straight Lines

 

Straight line approximation is a great way to visualize location of corner frequencies but information is lost about attenuation near the corner. In db terms, the errors are small numbers and most circuits have enough frequency margin such that we see no problems.

In more exacting circuits, this graph indicates about 30% low amplitude right at the corner frequency, a 10.6% error at half the corner frequency, 3% at one-quarter, and so on.


These errors apply to both the use of an isolation resistor and to a roll-off capacitor in the feedback loop.

STABILITY TROUBLESHOOTING GUIDE

| fosc (Oscillation Frequency) | Oscillates unloaded? | | | Probable Cause (In order of probability) |
|---------------------------------|--------------------------------|-----|----|---------------------------------------------|
| | Oscillates with Vin = 0 | | | |
| | Loop check† fixes oscillation? | | | |
| $CLBW \leq fosc \leq UGBW$ | N | Y | N | A,C,D,B |
| $CLBW \leq fosc \leq UGBW$ | Y | Y | Y | K,E,F,J |
| $CLBW \leq fosc \leq UGBW$ | - | N | Y | G |
| $fosc \leq CLBW$ | N | Y | Y | D |
| $fosc = UGBW$ | Y | Y | N* | J,C |
| $fosc \ll UGBW$ | Y | Y | N | L,C |
| $fosc > UGBW$ | N | Y | N | B,A |
| $fosc \leq UGBW$ | N | N** | N | A,B,I,H |

Previous sections have covered the major stability issues for more details and further explanation to use the Stability Troubleshooting Guide, refer to Application Note 1 in “General Operating Considerations” in the APEX Data Book.

REAL WORLD STABILITY TESTS

 


We have devoted much text to discussing and learning how to design stable circuits. Once a circuit is designed and built it is often difficult to open the feedback path in the real world and measure open loop phase margin for stability.


The following Real World Stability tests offer methods to verify if predicted open loop phase margins actually make it to the real world implementation of the design. Although the curves shown for these tests are only exact for a second order system, they provide a good source of data since most power op amp circuits possess a dominant pair of poles that will be the controlling factor in system response.

When performing these tests, use actual production hardware. Supplies, harnesses, mechanical loads, fluid load and others all make a difference. The time spent here may save days of troubleshooting 6 months after the design is in production.


SQUARE WAVE TEST

 

SQUARE WAVE TEST

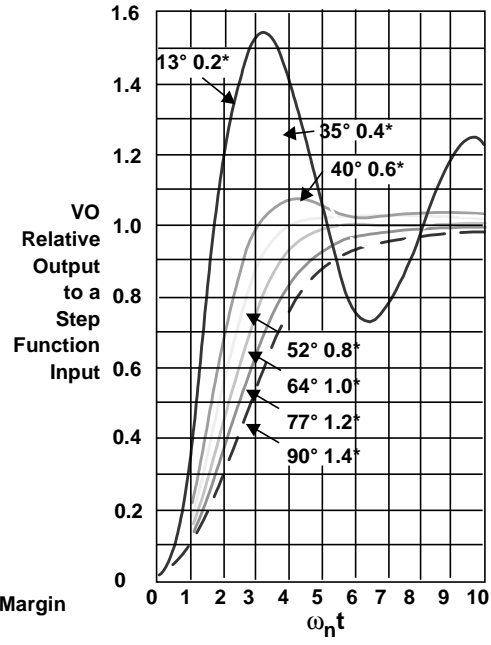


 * Open Loop Phase Margin & Damping Factor




* OPEN LOOP PHASE MARGIN AND DAMPING FACTOR

AVcl PEAKING TEST

 

PEAKING-MEASURED CLOSED LOOP

 

AVcl(dB) Peaking

We are often asked to generate data resembling this test. Why not look up the graph and translate to degrees of phase margin?


HIGH SPEED TECHNIQUES OPTIMIZING FOR SPEED

- Minimize Impedances
- Minimize Compensation Capacitance
- Minimize Integration Capacitance (Cf)
- Optimize Small Signal and Large Signal Bandwidths
- Trade-off:
 - Slew Rate
 - Settling Time

Maximum high speed performance with stability is achieved through the use of good high speed techniques and an understanding of the trade-offs involved between the various high speed requirements. For instance, small signal and large signal bandwidth requirements are not directly related and the designer must understand the trade-off between them.

Also, some high speed characteristics have conflicting requirements such as settling time and slew rate.

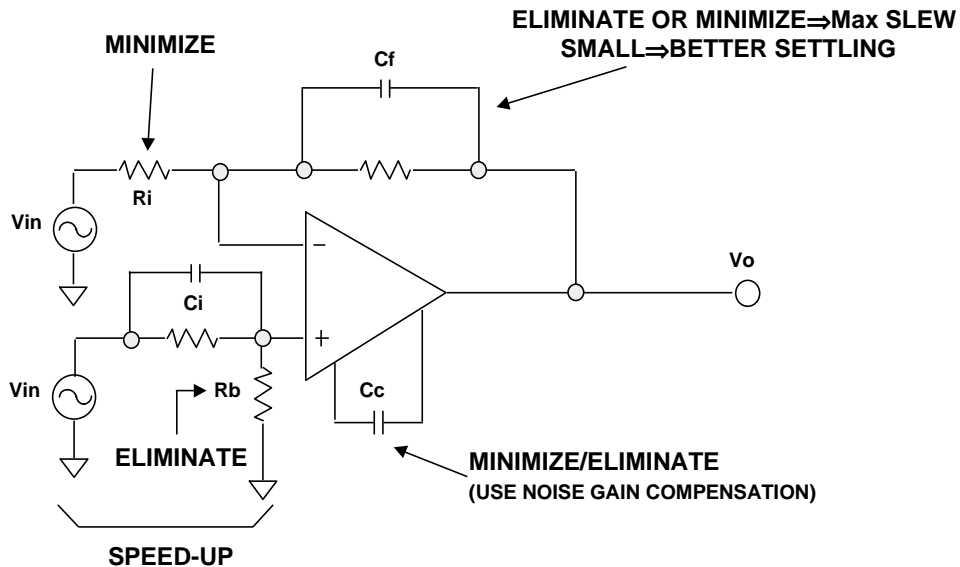HIGH SPEED TECHNIQUES GOOD GENERAL PRACTICES



Ever try to buy 100K Ω coax cable? 100K Ω could simply not drive the parasitics. So, don't use that impedance trying to deliver input signals to the op amp.

C_f is a roll-off or slow down element. To achieve maximum slew rate get rid of C_f . Small values can be used to reduce overshoot and improve settling time.

The basic idea of this "Input Speed-up Network" is to provide a path for the higher frequency components of a step input to overdrive the input of the amplifier to get high slew rate. At high frequencies, the capacitor C_i is a short and the input drives the +input unattenuated. At low frequencies, such as the flat part of a step input, the resistor divider attenuates the signal to achieve the desired final gain for V_o/V_{in} .

The use of R_b to compensate bias current errors makes this pin an antenna or a low pass filter. Ground it.

Other ways to maximize high speed performance are to decrease the compensation capacitor C_c to maximize slew rate and to provide large enough drive input signal to cause at least a 1V-2V differential signal at the op amp input. If the amplifier is decompensated for slew rate, Noise Gain Compensation may be needed for stability. Most amplifier slew rates are specified using a 1V-2V input differential drive voltage into the amplifier. Adequate input signal amplitude will maximize slewing of the output.

SLEW RATE AND PBW

$$\text{S.R.} = \left[\frac{\Delta V_{\text{out}}}{\Delta t} \right]_{\text{max}} \quad [\text{V}/\mu\text{s}]$$

FOR PBW, SET:

$$\text{S.R.} = \frac{dV}{dt} (V_p \sin 2\pi f t)_{\text{max}} \quad [\text{SINUSOIDS}]$$


$$\text{S.R.} = 2\pi (\text{PBW}) V_p \quad [\text{SINUSOIDS}]$$

$$\text{PBW} = \frac{\text{SR}}{2\pi V_p} \quad \text{SR} = \text{PBW} 2\pi V_p$$

Op amps have a maximum rate of change of output voltage that is directly related to the input stage current and the compensation capacitance. The maximum dV/dt of a sine wave occurs as the output passes through zero. Setting the dV/dt max of the amplifier equal to the dV/dt of a sine wave gives a relationship between slew rate and full power bandwidth. The simplicity of this relationship is often complicated by the common practice of specifying slew rates under conditions of extreme overdrive. This overdrive results in operation deep within the non-linear region with apparent slew rates up to several times higher than the slew rate derived from the full power bandwidth formula above.

Full power bandwidth is a "large signal" parameter. It is not directly related to small signal bandwidth. It's a good idea to also check loop gain for the specific application.

OPTIMIZE PBW AND SSBW

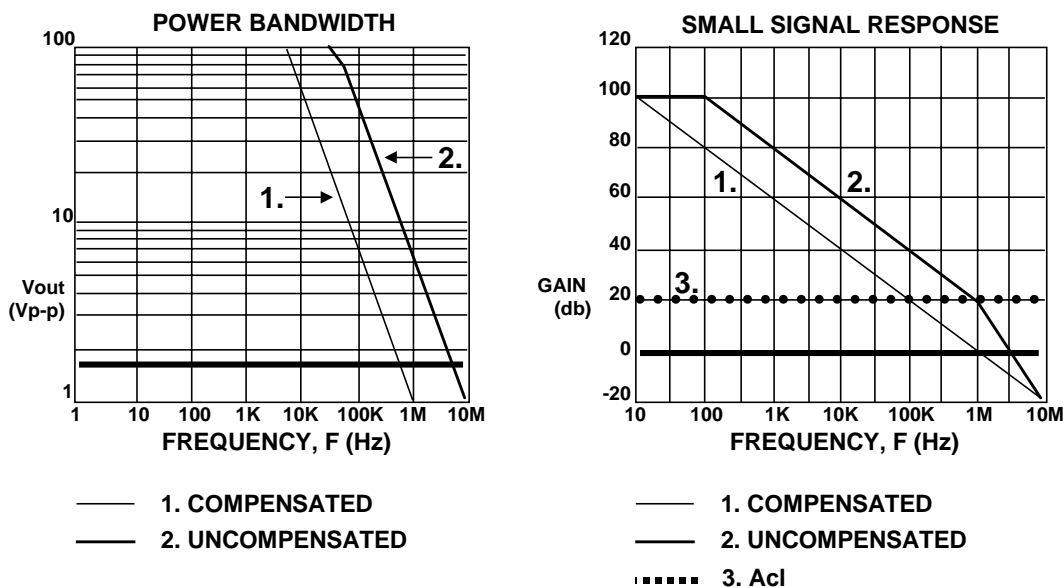

The trade offs between small signal performance and large signal performance are often misunderstood or misinterpreted. It helps to understand the differences between the two bandwidths.

On the right are the small signal response curves of a typical high speed amplifier with both uncompensated and compensated Aol curves shown. On the left is the large signal or "full power" response curve shown for both compensated and uncompensated conditions.


Note that the maximum useful small signal bandwidth of the amplifier is approximately 1MHz with or without compensation. The unity gain amplifier has a maximum bandwidth at unity gain of 1MHz, the uncompensated amplifier has more bandwidth but must be run at higher gains. Therefore its useful bandwidth is also limited to about 1MHz. The full power response curve may extend on up to 10MHz for low amplitude signals, however this power response is not achievable due to small signal bandwidth limits.

The best approach is to start with your maximum peak to peak output voltage requirements for sinusoids and find that peak to peak value on the Full Power Response Graph. Find the intersection of this line with the maximum output frequency required on the horizontal graph. The intersection of these two points will determine the maximum allowable compensation.

Consult the small signal response curve. For the compensation value chosen, find the minimum allowable closed loop gain. the intersection of Acl (min), with the AOL curve for that particular compensation value, gives the maximum useful small signal bandwidth.

Choosing the lowest possible compensation value combined with the lowest possible stable gain gives the maximum full power and small signal bandwidth combination. Keep in mind that larger loop gains give the best accuracy and lowest distortion.

CABLE LOADS

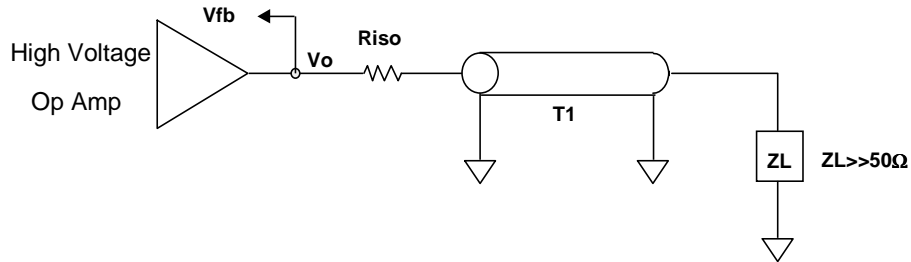

$$F \leq \frac{K(7.5 \times 10^6)}{L} \rightarrow T1 = CL$$

Where: L = length of cable

K = velocity factor

High voltage power op amps often drive their loads via coax and these are often not terminated in the characteristic impedance of the cable. This means the coax is primarily adding capacitive loading to the op amp unless the cable length is at least one-fortieth of wavelength at the frequency of interest.


In the formula above, K is typically around .66 for common coax, the constant is simply the speed of light/40 in meters/second and L is in meters. As a benchmark, 10KHz corresponds to 1624 feet or 495 meters.

A ballpark value for the capacitive loading is 30pF/foot or 100pF/meter. As higher voltage op amps tend to have higher output impedances, they are more likely to have trouble with additional load and need compensation.

HIGH POWER TECHNIQUES

But, Mom...

You should've seen the other guy!

 

The number is part of the FBI crime lab evidence labeling program. It seems some digital jock said, "Electrons are electrons. I'll show those analog folks I can design a high power circuit just as well as they can."

The slide is right. The widow now keeps this screwdriver on the mantel in the living room.

Dead Op Amps Don't Power Much

Who, me? Read the book?

- AN1 General Operating Considerations
- AN8 Optimizing Output Power
- AN9 Current Limiting
- AN19 Power Op Amp Stability
- AN25 Driving Capacitive Loads

- Subject Index

We've heard of the male stereotype character who reads directions only as a matter of last resort. This anonymous author isn't much of a reader but after a few explosions, I broke down and opened the book- -the Apex book of course.

Better than ¼ of the book is application notes, arranged mostly by type of application rather than amplifier model. This along with a comprehensive subject index make this book very valuable.

Here's my suggestion: Thumb through at least the Ap Notes above looking at pictures and paragraph titles. Then check out the index in the back.

Quiz for today: What is the Apex *Cage Code*?


The Bridge Circuit

- Double the voltage swing
- Double the slew rate
- Double the power

- Bipolar drive on a single supply
- More efficient use of supplies

There are two basic categories of motivation to use the bridge circuit. The most common is doubling the voltage capability of the whole line of power op amps. The second category solves some limited supply availability situations.

Bridge Basics

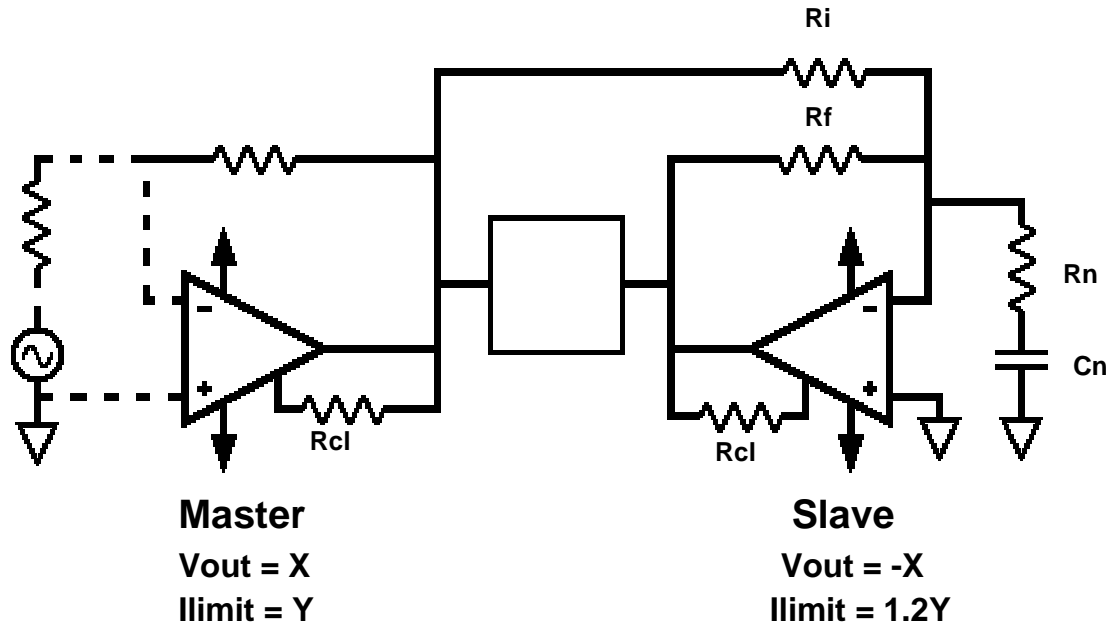


The master amplifier in the bridge may be configured in any manner suitable for a single version of the particular model. Set gain of the slave for $\frac{1}{2}$ the total required to drive the load. The slave provides the other half of the gain by inverting the output of the master and driving the opposite terminal of the load. Dual supply operation is the easiest but asymmetric or single supply versions are also common.

The R-C network is often used to fool the slave amplifier into believing it is running at the same gain as the master. This is important when using externally compensated amplifiers at other than their lowest bandwidth compensation. Set R_n for $R_{in} || R_n = R_f / \text{gain of the master}$. Set C_n for a corner frequency with R_n at least $1\frac{1}{2}$ decades below unity gain bandwidth.

Consider a shorted load. Tolerances make it impossible to set identical current limits on the master and the slave; one will go into current limit, the other will never reach the limiting level. Assume the master limits and the slave reduces its drive to the load also because it is still in a linear inverting mode. With both amplifier outputs going toward zero, power dissipations are equal and worst case is $I_{limit} * \frac{1}{2}$ total supply.

If the slave limits first, the master remains linear and capable of driving to either rail leaving a power stress on the slave of $I_{limit} * \text{total supply}$.

BRIDGE POWER CALCULATION

 

There are several formulae available for calculating worst case power dissipation in a power amplifier (refer to APEX catalog “General Operating Considerations” as well as previous seminar text). These formulae are based on a single power op amp using bipolar, symmetrical supplies. But what about this single supply bridge?


Instead of attempting algebraic manipulation of the formulas, try the using *circuit algebra*. Knowing the master and slave drive equally but in opposite directions tells us the ohmic center of the load does not move. This leads to an equivalent two resistor load where the center voltage can be calculated. When using dual symmetric supplies the center is almost always ground and we have an equivalent circuit right away.

For the single supply the center of the equivalent load is almost always the mid-point of the supply. Simply lowering all voltages by the load center voltage yields the same equivalent circuit. Simply calculate power dissipation of the equivalent and don't forget to double this figure.

If you are using Power Design you will need the voltage translation portion of this exercise, but not the equivalent load. Enter the total load, total signal level and “Yes” in the bridge question yellow cell.

A Weird & Dangerous Bridge

0/800V Unipolar Output

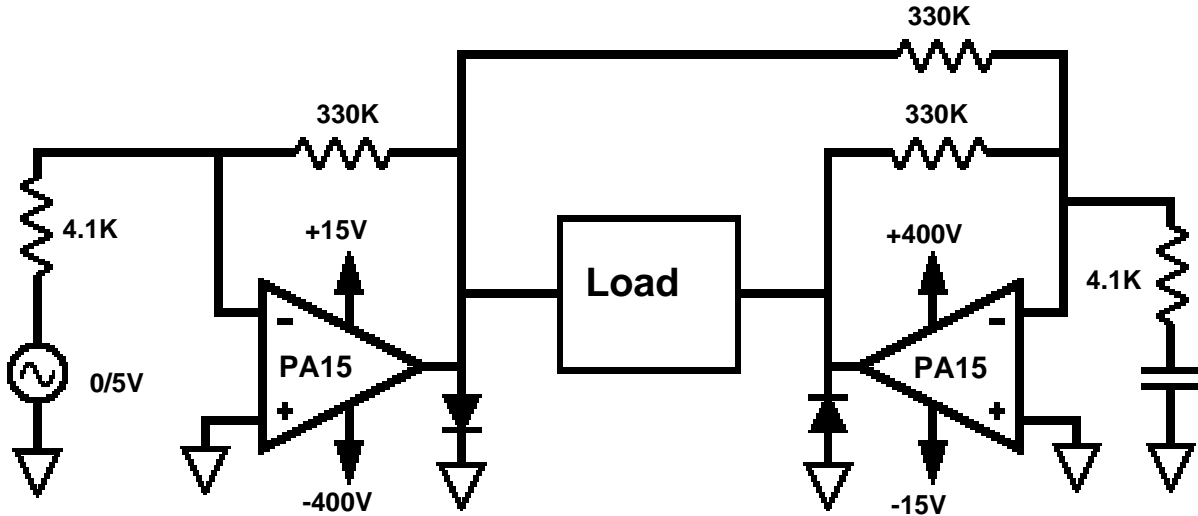

No, this is not the most common bridge circuit. But consider that the only other choice above 450V total supply is the PA89 which is quite slow and costs about \$200 more than two PA15 amplifiers (both @ 100 quantity).

Dangerous? Any 800V circuit qualifies for this description but from the op amp point of view this one is a little more so because there are voltages in the area greater than his supply rails.

The left hand op amp swings 0 to -400V; the right hand from 0 to +400V. With the load looking at these two voltages differentially it sees 0/800V.


Consider a shorted load causing the right hand amplifier to current limit. If the left amplifier ever goes below -15V, he can destroy his partner. The diodes prevent this.

Output Current Buffers

- Multiplies power & current capabilities
- Small loss of swing capability
- More prone to oscillate

Class C Current Buffer

Speed Limit Strictly Enforced

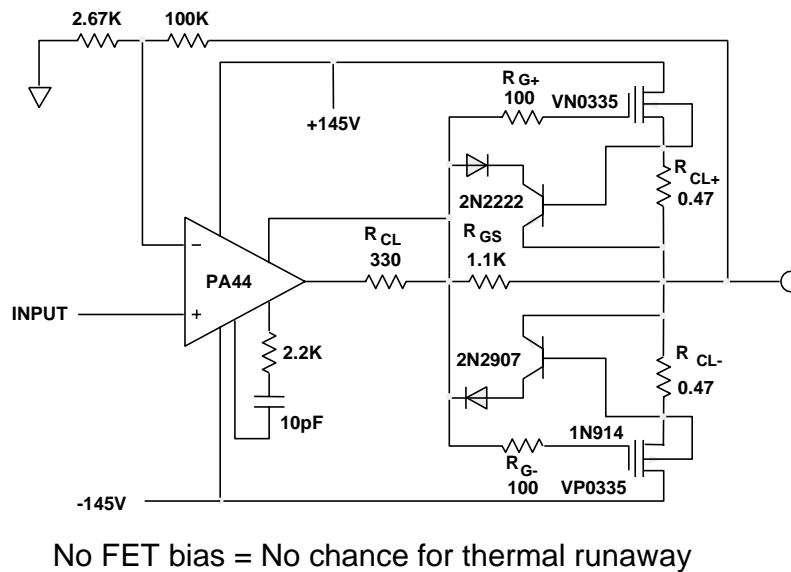


The choice of specific MOSFETs is determined entirely by current, voltage and power dissipation requirements. There are no radical differences among the different MOSFETs regarding threshold voltages of transconductance. Note that each MOSFET must be rated to handle the total supply voltage, 300V in this case.

Current limits work like the circuits we covered earlier. Power dissipation requirements for the MOSFETs can also be found methods we learned earlier, just remember the power is split between the two packages if the signal is AC only. Power Design will calculate the watts, plug in the driver amplifier, the real load and ignore the red flags.

The 330Ω current limit resistor sets the PA44 current limit to approximately 9mA. This current flowing across R_{GS} limits drive voltage on the MOSFETs to 10V. This current also lowers crossover distortion. Worst case (during output stage current limit) power dissipation in the PA44 will then be 1.3W due to output current plus 0.6W due to quiescent current totaling 1.9W. Unless you are willing to cut holes in the PC board to to contact the bottom of the surface mount package with an air or liquid cooling system, this is about the limit. Typical operation will generate less than 1W in the op amp. Replacing R_{gs} will a 10 to 12V bi-directional zener will allow a cooler running op amp at the cost of increased distortion.

If more power is required than a single pair of MOSFETs can handle, additional MOSFETs may be added in parallel. Each device needs its own source resistor and gate resistor but the small signal current limit transistor and diode need not be duplicated.

COMPLIMENTARY MOSFET BUFFERS

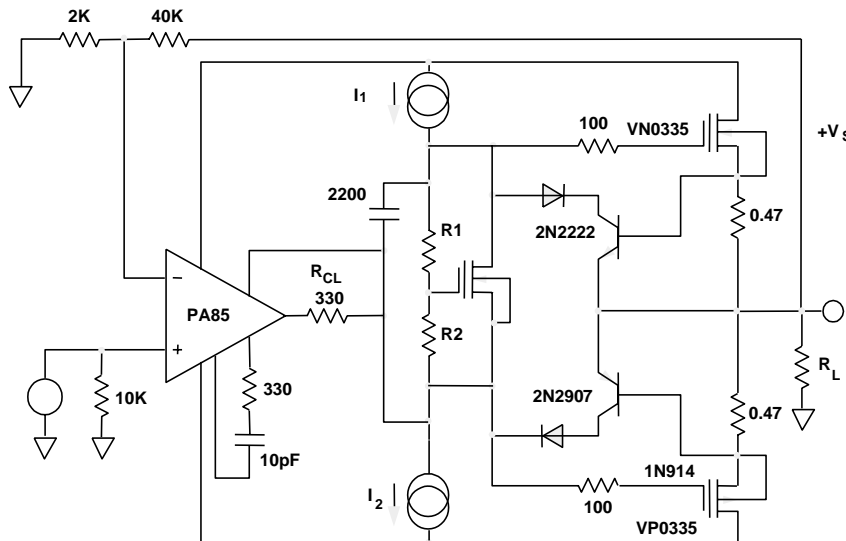


The class C circuit was able use a simplified version of this slide with no attempt to establish class A/B bias in the MOSFET output stage. In that circuit with no bias, the typical MOSFET threshold of 3V means the op amp must swing 6V during the crossover transition while the final output does not move. The additional circuitry used here will lower distortion and is increasingly important as frequency goes up. Distortion improvements better than an order of magnitude have been achieved.

As most power MOSFET data sheets provide little data on VGS variations at low currents over temperature, it facilitates the design process to have curve tracer data over the temperature range of interest. Design the VGS multiplier empirically. Current sources of 5mA and splitting the current equally between the resistors and the MOSFET area good starting points. Decreasing current in the MOSFET will increase the multiplier TC. Typical designs requiring low distortion will be set up to obtain 2mA or less bias in the output stage. The trade offs are more distortion with low current and danger of thermal runaway on the high end. Be absolutely sure to guardband your high end temperature. The circuit shown here is capable of distortion below .05% at 50KHz and is thermally stable (flat or negative TC of current in the output stage) over the range of -25° to 85°C.

Note that any multiplier voltage at all reduces distortion. Successful designs have even reduced the multiplier circuit to just a diode connected MOSFET. Do NOT use bipolar transistors or diodes for this biasing. Their TCs do not match those of the MOSFETs.

The 100Ω gate resistors prevent local output stage oscillations. It is important they be physically close to the MOSFETs.

QUASI-COMPLIMENTARY MOSFET BUFFERS

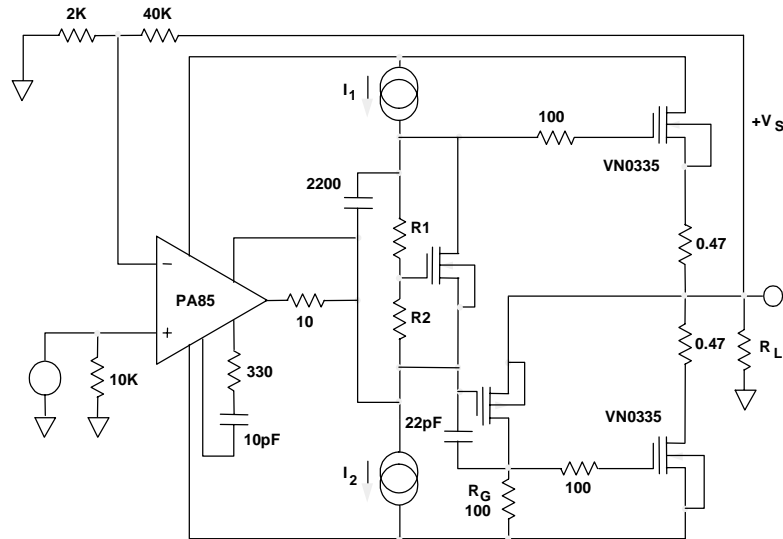


Above 300V p-channel high power MOSFETs can be difficult to find. An alternative is to use a quasi-complementary connection on the negative side. Since the required gate drive voltage of the output device appears across R_G , its value will set the maximum current through the p-channel MOSFET. Typical maximum gate drive requirements are 10V. This circuit has demonstrated a slew rate of 360V/ μ s. A second disadvantage of the quasi-complementary design is higher saturation voltage to the negative rail because two gate-source voltages are stacked between the rail and the output.

Connecting the op amp to the top side of the multiplier helps a little but both buffer design approaches can benefit from having the high voltage op amp operate on higher supply rails than the high power MOSFETs. This improves efficiency by allowing better saturation of the buffers.

Design criteria for the current sources, current limiters (not shown here) and multiplier are the same as with the complementary version. It is possible to omit one of the current sources in these circuits. However, this places an added heat burden on the high voltage op amp because the entire current of the remaining source must flow through it. When calculating this added dissipation, use the current and the total supply voltage. When both current sources are used the op amp need only make up the difference between them.

PARALLEL OPERATION

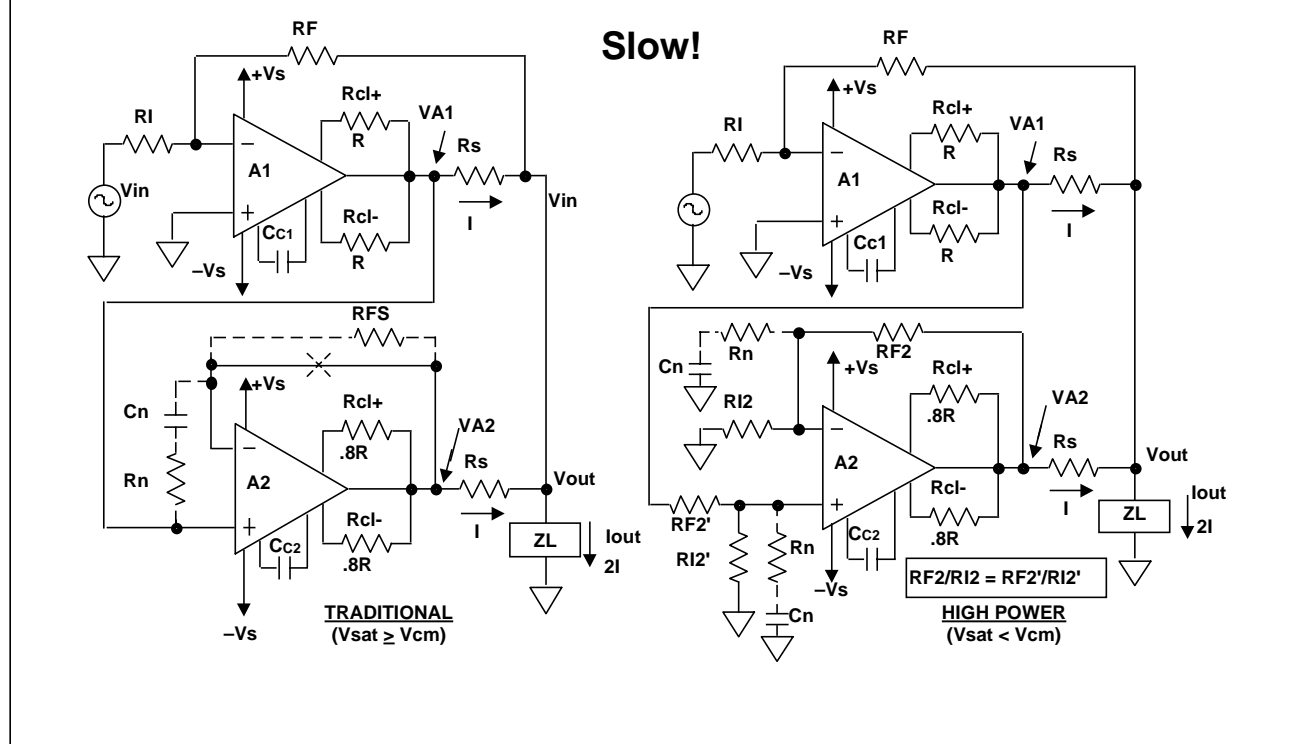

GENERAL COMMENTS:

Occasionally it is desired to extend the SOA of a power op amp or provide higher currents to a load than the amplifier is capable of delivering on its own. Sometimes it is more cost effective to use power op amps in parallel rather than to select a larger power op amp.

The parallel power op amp circuit will consist of a master amplifier, A1, which sets the V_{out}/V_{in} gain and slave amplifiers, A2 et al, which act as unity gain followers from the master amplifier. For simplicity we will review the case of two power op amps in parallel.

We will need to consider the following key areas when paralleling power op amps:

- 1) Input offset voltage
- 2) Slew rate
- 3) Phase compensation
- 4) Current limit resistors

If we attempt to hook the outputs of two power op amps directly together the difference in input offset voltages, divided by theoretically zero ohms (a connecting wire), will cause huge circulating currents between the amplifiers, which will lead to rapid destruction. To minimize circulating currents we will need to add ballast resistors, R_s , as shown. The worst case circulating currents now are $I_{circ} = V_{os}/2R_s$. To minimize circulating currents we want R_s to be as large as possible. However, large values of R_s will add an additional voltage drop from the power supply rails and thereby reduce output voltage swing. Large values of R_s will also result in higher power dissipations. A rule of thumb compromise is to set R_s for circulating currents of about 1% of the maximum output current from each amplifier, .011 in our example.

GENERAL COMMENTS (cont.):

Notice the particular arrangement of the master and slave amplifiers. $V_{A1} = I R_s + V_{out}$. However the point of feedback for A1 is at V_{out} causing A1 to control the gain for V_{out}/V_{in} . V_{A1} then becomes the input to A2. V_{A2} is then $V_{out} + I R_s$. But $V_{out} = V_{A1} - I R_s$. So each amplifier, A1 and A2, put out the same voltage across R_s and Z_L and currents are thereby added to force $2I$ through the load with each amplifier providing one-half of the total.

The slew rates of A1 and A2 must be selected to be the same or A1 must be compensated for a lower slew rate. If A1 slews faster than A2, large circulating currents will result since A1 could be close to $+V_s$ while A2 is still at zero output or worse near $-V_s$. C_{c1} and C_{c2} must then be selected to be the same or C_{c1} greater than C_{c2} . Even with these steps for slew rate matching it is recommended to control the slew rate of V_{in} such that the amplifiers are not commanded to slew any faster than 50% – 75% of the selected slew rates. This is because, even with identical compensation, no two amplifiers will have identical slew rates.

If it is decided to have A2 not compensated for unity gain, to utilize a higher slew rate, use Noise Gain Compensation, shown by the dashed RFS and R_n , C_n combination, to compensate the amplifier for AC small signal stability.

Current limit resistors, R_{cl+} and R_{cl-} for A2 should be 20% lower in value than current limit resistors for A1. This is to equalize SOA stresses during a fault condition. With the master amplifier, A1, going into current limit first it will lower its output voltage thereby commanding A2 to do the same for equal sharing of stresses during a current limit induced condition.

TRADITIONAL ($V_{sat} \geq V_{cm}$):


This parallel configuration is for op amps whose saturation voltage is greater than or equal to their common mode voltage ($V_{sat} \geq V_{cm}$). For example, a PA10 has a common mode voltage specification of $\pm V_s - 5$ and a saturation voltage of $\pm V_s - 5$. For the PA10 the output saturation voltage (5V) is equal to the common mode voltage (5V from either rail). We will not have any common mode voltage violation then if we drive the output of A1 into saturation as we will still be in compliance with the input common mode voltage specification for A2.

HIGH POWER ($V_{sat} < V_{cm}$):

This parallel configuration is for amplifiers whose currents are greater than 200mA and whose saturation voltage is less than their common mode voltage ($V_{sat} < V_{cm}$).

For example, a PA02 has a common mode voltage specification of $\pm V_s - 6$ and a saturation voltage of $\pm V_s - 2$. For the PA02 the output saturation voltage (2V) is less than the common mode voltage (6V from either rail). If we drive the output of A1 directly into A2 in a unity gain voltage follower configuration we will have a common mode voltage violation.

The only way around this is to use a matched resistor network where the ratio of $R_{F2}/R_{I2} = R_{F2}'/R_{I2}'$. The absolute value of each resistor is not as important as accurate ratio matching with temperature. If A1 and A2 are compensatable amplifiers and unity gain compensation is not desired, to use faster slew rates, then A1 can use noise gain compensation to guarantee AC small signal stability. R_n and C_n are our traditional Noise Gain Compensation components. R_n' and C_n' are essential to guarantee a flat V_{out}/V_{in} frequency response until we run out of loop gain.

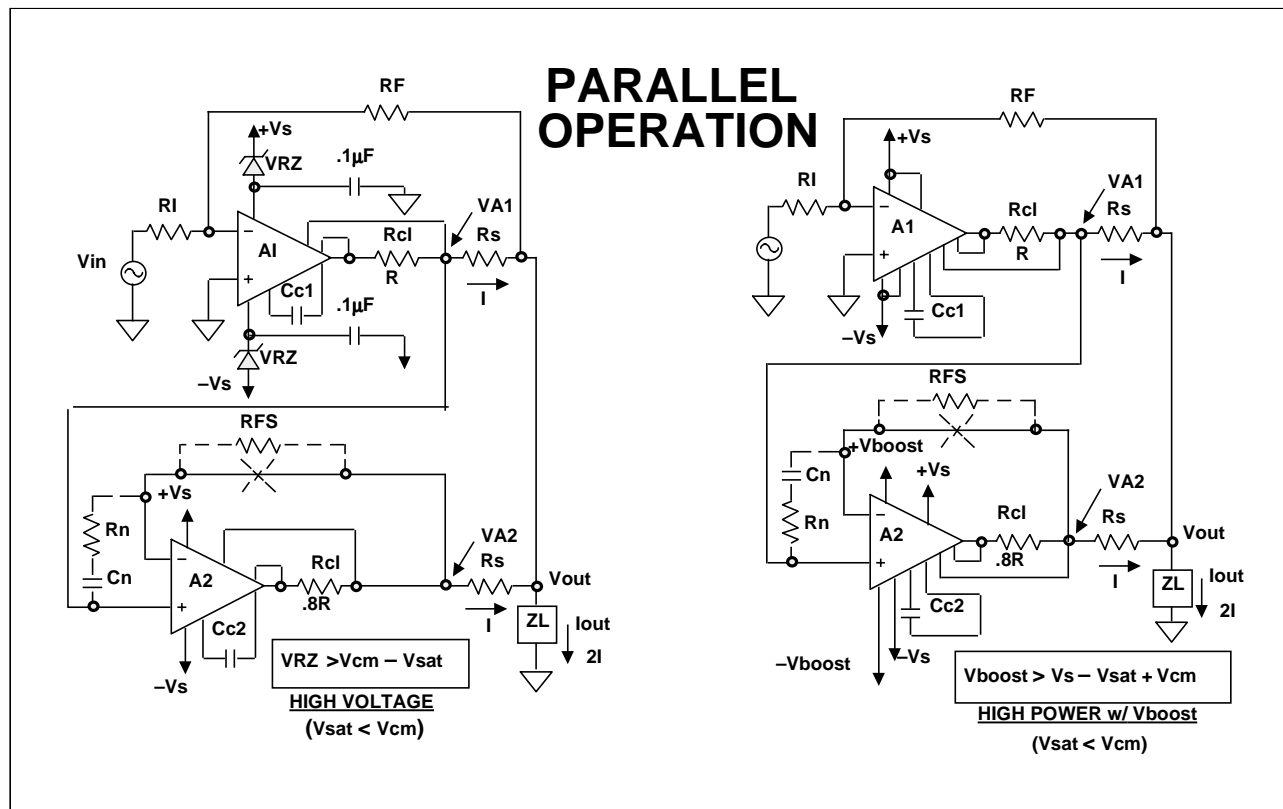

All our previous “GENERAL COMMENTS” on the use of parallel power op amp circuits still apply to these configurations. Additional specific comments on each follows.

HIGH VOLTAGE ($V_{sat} < V_{cm}$):

This parallel configuration is for amplifiers whose currents are less than 200mA and whose saturation voltage is less their common mode voltage ($V_{sat} < V_{cm}$). In the APEX amplifier line this will almost always be high voltage ($\pm V_s > 75V$).

For example a PA85 has a common mode voltage of $\pm V_s - 12$ and a saturation voltage of $\pm V_s - 5.5$ at light loads. For the PA85 the output saturation voltage (5.5V) is less than the common mode voltage (12V from either rail). If we try to drive A2 as a unity gain voltage follower directly from A1 we will have a common mode voltage violation. That is, unless we lower the supply voltage of A1 by about 6.5V, which we can do easily with a zener diode in each supply line of A1. For 200mA output current plus 25mA quiescent current would require at least a 2W, 6.8V zener in each supply rail. The obvious loss with this technique is output voltage swing from the rail, now limited to V_{sat} of 5.5 Volts plus VRZ drop of 6.8 volts for a total of 12.3V, at light loads.

HIGH POWER w/Vboost ($V_{sat} < V_{cm}$):

This parallel configuration is for amplifiers such as the PA04or PA05 that are high output current and whose saturation voltage is less than their common mode voltage ($V_{sat} < V_{cm}$.)

For example a PA05 has a common mode voltage of $\pm V_s - 8$ and a saturation voltage of $\pm V_s - 5.0$ at light load. If we try to drive A2 as a unity gain voltage follower directly from A1 we will have a common mode voltage violation. That is, unless we utilize the Vboost function of these power op amps on A2 to run the front end of A2 at a supply voltage which is at least 3 volts above its output voltage supply (V_s). This Vboost supply need only supply quiescent current for the device and can be generated by a switching floating regulator.

A less advantageous approach, which would reduce output voltage swing, is to utilize a zener diode in the Vboost supply of A1, similar to the “HIGH VOLTAGE ($V_{sat} < V_{cm}$)” example above.

Watch the Slave Phase Shift

- PA85 Power Response Curve = 500KHz@400Vp-p
- Power Design suggests 86Khz for accuracy
- Power Design tells us phase shift is 7° @ 87KHz
- $\text{Sin}(7^\circ) = 0.122 * 200\text{Vpk} = 24.3\text{V}$

- This voltage appears across the two Rs resistors


The power response graph says you can get to those points, however, you will usually need to increase the drive amplitude and you will probably just start seeing distortion. Another way to put it: these curves demand no loop gain and circuit accuracy is a function of the op amp rather than feedback components on the sloping portion of the power response curve (AC response limits rather than voltage saturation). The amplitude and distortion voltage errors of the slave appear across the two sharing resistors.

Phase phase shift grows as loop gain decreases. In the master of the parallel circuit this does no harm locally because the slave input includes the shift. However shift in the slave produces voltage applied across the sum of the two ballast resistors where circulating current becomes a concern.

The Cload sheet of Power Design will calculate closed loop phase shift. The sine of this angle times peak voltage yields the error we are looking for.

Parallel power op amps is not a high speed technique.

SINGLE SUPPLY PARALLEL BRIDGE

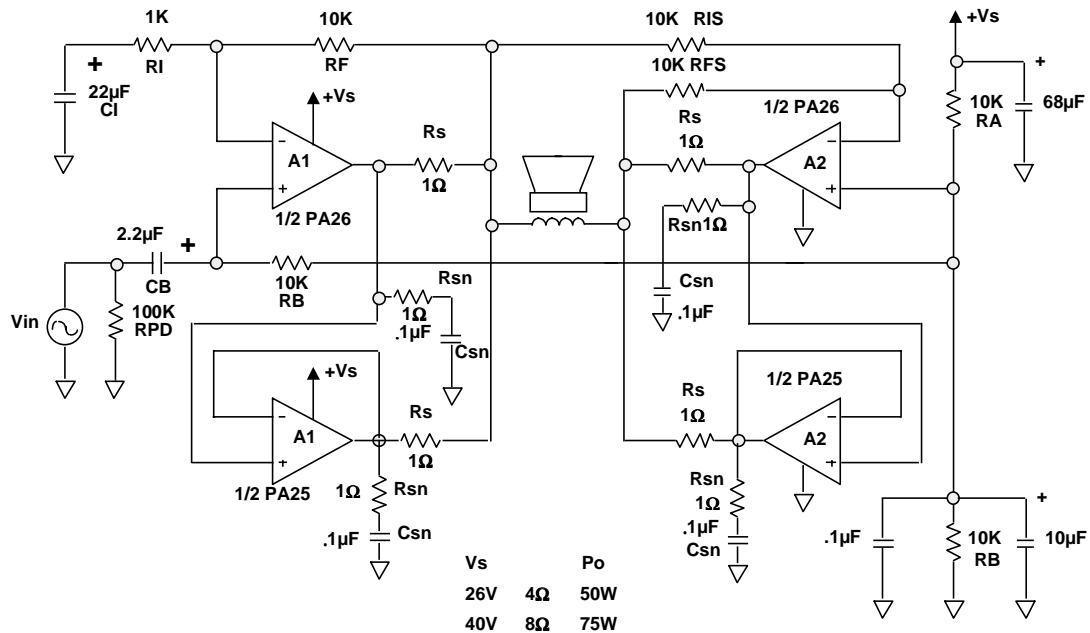

This application utilizes two power op amp circuit tricks—single supply bridge mode to increase output peak-to-peak voltage and parallel power op amps to increase output current.

The PA26 is optimized for single supply operation with its wide input common mode voltage range and low saturation voltage. The parallel combination provides a dual advantage in that we can deliver higher output currents as well as reduce the output saturation voltage since each op amp need only supply one-half the total load current.

AC coupling of V_{in} provides level shifting of the input signal to swing symmetrically about $1/2V_s$. AC coupling through C_I ensures the maximum DC offset across the load is only 20mV. R_B provides a +input DC bias path for the front end of the master amplifier half of A1. R_{sn} and C_{sn} networks are required on the output of each amplifier section of A1 and A2 to prevent oscillations on the output during negative swings. This is due to the type of output power stage inside the monolithic PA26. A2 is configured as a traditional inverting gain amplifier for single supply bridge mode and uses one half of itself for providing extra current as a slave amplifier in the parallel configuration.

With the PA26 at \$5US (1000) this is about 13 cents per watt. PA21 and PA25 offer hermetic packages at higher cost. Just imagine what you could do with PA03s in this circuit. Let's break the KW barrier!

Controlling Output Current

- Removes Zload from the Iout equation
- Adds Zload to the Vout equation

- Charge Rate control


**Batteries, capacitor plate forming
power supply active loads, CD welder**

- Magnetic field intensity


**Bearings, deflection, MRI, torque, linear
or angular displacement**

Controlling current rather than voltage is much more common with power op amps than with small signal op amps. The current control world brings interesting applications plus some new techniques with their own equations and special points to watch.

1 Volt, 1 Henry, 1 second, 1 Amp

 

I_L

 

$$di = \frac{V * dt}{L}$$

$$V = \frac{di * L}{dt}$$

OK, so you've seen this before. It is central to current control.


Changing current a lot, in a big inductor, in a hurry, takes lots of volts.

The corollary:

Stopping a big current, in a big inductor, in a hurry, generates lots of volts.

It may require more power than first glance says; opening a current carrying line may release all the stored energy in the form of fire.


Basic PWM Current Output

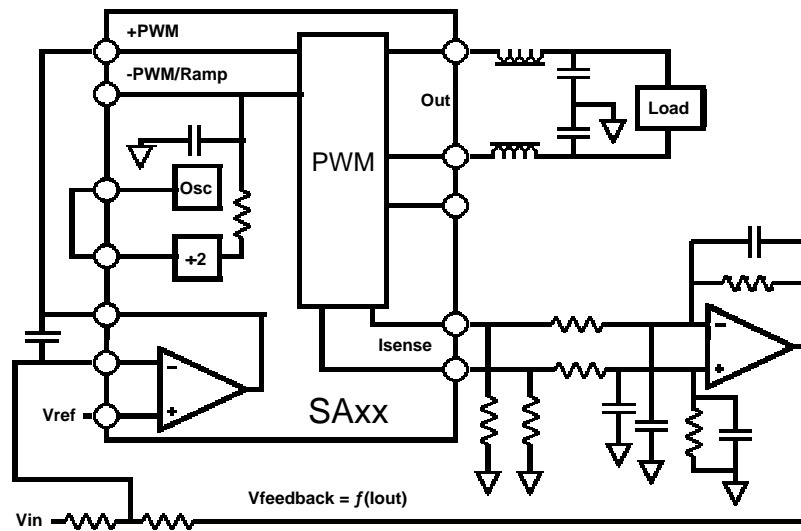

Most Apex PWM amplifiers offer two current sense pins. With the H-bridge output this means the current path changes sense pins each half cycle. Since alternating half cycles correspond to opposite directions of current flow in the load, a differential amplifier monitoring the two pins yields magnitude and direction data.

The integrator now compares the input and feedback voltages and moves its output as required to balance them. The two associated resistors allow easy magnitude scaling. Reference voltage is often used to elevate signals above ground to comply with op amp common mode voltage ranges. The reference voltage is also often used to level translation such as matching bipolar input signals to a single supply control system.

VOLTAGE-TO-CURRENT CONVERSION

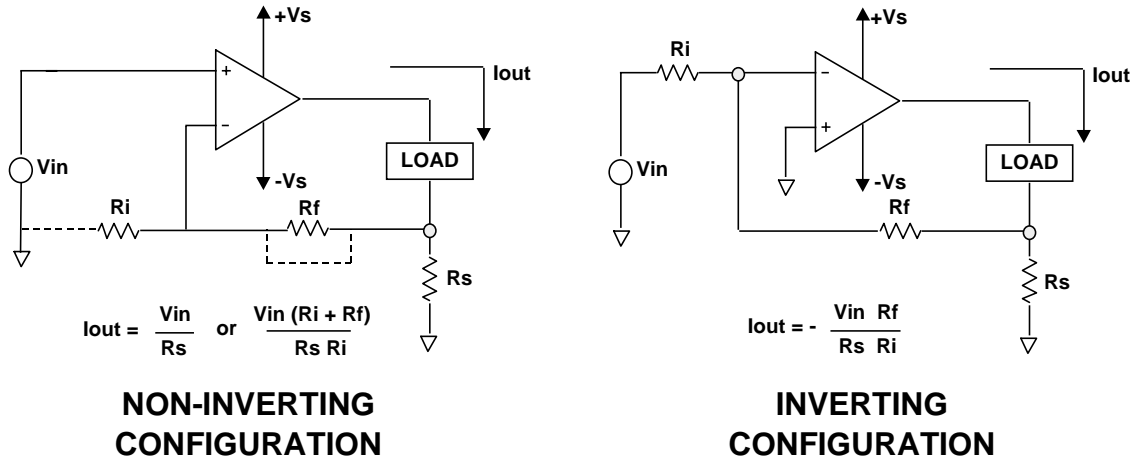


Two generic examples of voltage-to-current conversion for a floating load are shown here. The floating load circuit provides the best possible performance of any of the current output circuits with the tradeoff that the load must float.


In the basic non-inverting circuit R_i and R_f don't exist. Load current develops a proportional voltage in R_s which is fed back for comparison to applied input. As long as voltage across R_s is lower than the input voltage, the output voltage increases. In other words the op amp impresses the input voltage on the sense resistor. Adding the resistors allows increasing the transfer function. It is also common to have R_f without R_i providing an RC stabilizing network a reasonable impedance for its AC feedback signal.

The inverting circuit works in the same manner other than polarity but does have the advantage of being able scale the transfer function up or down. This mean it is possible to have less voltage on the sense resistor than the input signal has.

 VOLTAGE-TO-CURRENT CONVERSION IMPROVED HOWLAND CURRENT PUMP


 
$$I_{out} = -V_{in} \frac{R_F}{R_I R_S}$$



$$I_{out} = V_{in} \frac{R_F}{R_I R_S}$$

DOMINANT ERROR - MISMATCH OF R_Is AND R_Fs

When a load must have one end of it ground referenced, voltage to current conversion circuits are still a possibility. The Improved Howland Current Pump provides a topology for V-I circuits driving a grounded load.


One way to view this circuit is to think of it as a differential amplifier circuit with a differential input and a differential output. V_{in} is gained up by the ratio of R_F/R_I and differentially impressed across R_S . I_{out} then is the voltage across R_S divided by R_S . Since we have a differential input as well, moving V_{IN} to the opposite input reverse the relationship of I_{out} to V_{in} .

The dominant error in this topology is ratio matching of the R_F/R_I resistors. The ratio of R_F/R_I for the negative feedback path should closely match the ratio of R_F/R_I in the positive feedback path. Resistor networks with close ratio matching, where the absolute tolerance of the resistors may be as high as 10%, are required if high accuracy is desired.

The Improved Howland Current Pump offers a minimum component count ground referenced V-I circuit. In many systems accuracy of this V-I function is not critical. A typical circuit of this topology using 1% resistors may only have an overall I_{out}/V_{in} accuracy of 20% when output impedance, A_{ol} , offset voltage, and component accuracy are accounted for.

Our final consideration for the Improved Howland Current Pump will be AC stability analysis. The load itself is in the feedback path of the op amp for this circuit. Stability compensation will then be load dependent. We will look at stability in great detail in future pages.

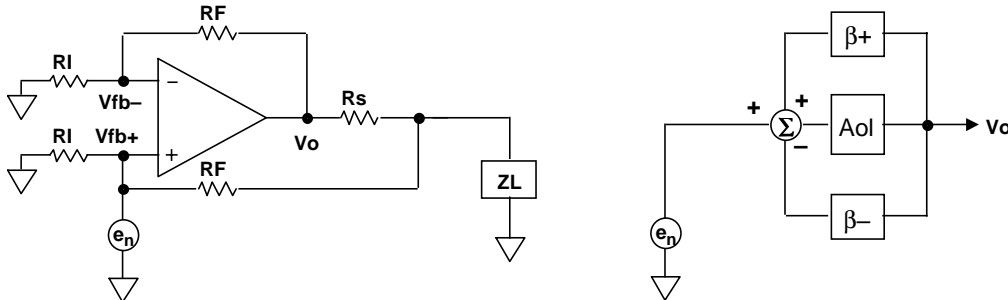IMPROVED HOWLAND CURRENT PUMP SMALL SIGNAL AC MODEL FOR STABILITY



$$\beta_+ = \frac{V_{fb}}{V_o}$$

$$\beta_- = \frac{R_i}{R_f + R_i}$$

$$\beta_+ = \frac{[Z_L] [(R_f + R_i)] R_i}{[R_s + Z_L] [(R_f + R_i)] [R_f + R_i]}$$

$$\beta = \beta_- - \beta_+$$

$$V_o = A_{ol} (e_n + V_o \beta_+ - V_o \beta_-)$$

$$V_o - A_{ol} V_o \beta_+ + A_{ol} V_o \beta_- = e_n A_{ol}$$

$$\frac{V_o}{e_n} = \frac{A_{ol}}{-A_{ol} \beta_+ + A_{ol} \beta_-}$$


$$\frac{V_o}{e_n} = \frac{1}{\beta_- - \beta_+}$$

$$\beta = \beta_- - \beta_+$$

The figure on the left above shows a typical Improved Howland Current Pump circuit. Notice the additional e_n voltage source on the non-inverting input node of the op amp. For AC small signal stability analysis we do not know where the input signal can be injected. We choose to inject the AC input signal at the +input since this will result in the worst case stability situation. $1/\beta$ plots then will be a representation of V_o/e_n .

The figure on the right above is the equivalent control system block diagram from which we derive the powerful equation for β which will enable us to stabilize the Improved Howland Current Pump with the stability analysis techniques we have previously covered.

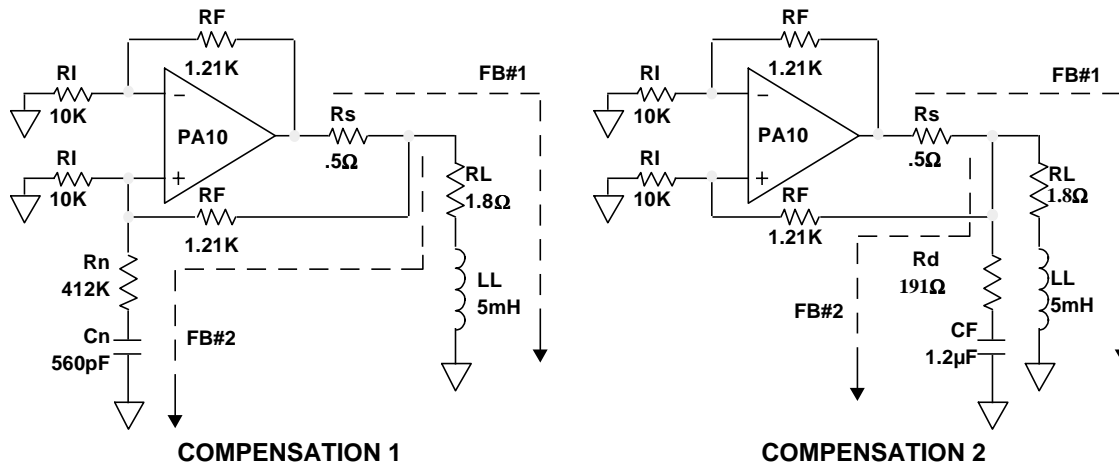IMPROVED HOWLAND CURRENT PUMP AC STABILITY




For any engineering problem there is usually more than one solution. This is true when reviewing AC stability compensation for the Improved Howland Current Pump and proposing a solution, or two!

Shown above are two compensation techniques, Compensation 1 and Compensation 2. FB#1 for both compensation techniques will be the same. Similar to V—I circuits for floating loads this $\beta +$ feedback path which will cause a zero in the net $1/\beta$ plot which will result in 40dB per decade rate of closure and instability without additional compensation provided by FB#2.

FB#2 has the function of reducing the voltage fed back to the +input at higher frequencies and thereby forming a pole in the net $1/\beta$ plot which guarantees stability and a 20dB per decade rate of closure.

COMPENSATING THE HOWLAND CURRENT PUMP

10 STEPS TO STABILITY

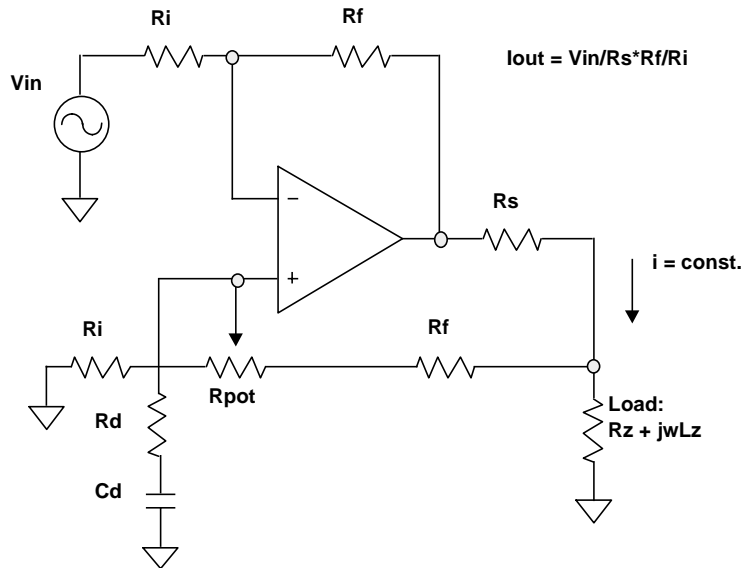

Inductive loads cause stability trouble with current source applications. Because current lags voltage in an inductor, current feedback is delayed and thus decreases the phase margin of the current amplifier. Consequently, ringing or oscillation occurs. This following procedure shows a proper compensation technique for inductive loads.

After choosing R_i , select an appropriate current sense resistor R_s . The voltage available to your load is the power supply voltage minus the voltage drop across R_s . Power dissipation of R_s calculates to $P_{rs} = I_{max}^2 * R_s$. Continue to calculate the following component values: Finally, adjust R_d and C_d values to standard values and insert a trim pot between the feedback resistor and the input resistor of the positive feedback network:

$$R_{pot} = .02 * \Delta R[\%] * (R_i + R_f)^1$$

The potentiometer compensates the resistance mismatch of the R_f/R_i network. Trim for maximum output impedance of the current source by observing the minimum output current variation at different load levels and maximum output current.

¹ $\Delta R[\%]$: resistor tolerance in percent

COMPENSATING THE HOWLAND CURRENT PUMP

10 STEPS TO STABILITY


| Step | Description | Symbol | Formula |
|------|----------------------------------------------|---------------|----------------------------------|
| 1 | feedback resistor | Rf | $I_{out}/V_{in} * R_i * R_s$ |
| 2 | negative feedback factor | β_- | $R_i / (R_i + R_f)$ |
| 3 | positive feedback (DC) factor | β_+ | $R_z / (R_z + R_s) * \beta_-$ |
| 4 | total feedback factor | β_{tot} | $(\beta_-) - (\beta_+)$ |
| 5 | corrected total feedback limit (AC) | β_{lim} | $\beta_{tot}/10$ |
| 6 | corrected positive feedback | β_{cor} | $(\beta_-) - (\beta_{lim})$ |
| 7 | parallel resistance of ground leg (Rd Ri) | Rp | $R_f / ((\beta_{cor}^{-1}) - 1)$ |
| 8 | compensation resistor | Rd | $(R_p^{-1} - R_i^{-1})^{-1}$ |
| 9 | zero feedback frequency | fz | $(R_s + R_z) / (2 * \pi * L_z)$ |
| 10 | compensation capacitor | Cd | $L_z / (10 * R_d * (R_s + R_z))$ |

For single supply operation, two pull-up resistors are required to bias the input stage up to the minimum specified common mode voltage. They are connected from both input terminals to the positive supply and must be closely matched, too. Voltage sources represent a zero impedance (ideally) and let those pull-up resistors appear in parallel to the input resistors. A trim pot allows offset current adjustment. Apex Application Note #21 expands on single supply operation.

Note, that the current control bandwidth (f-3dB) is much less than the small-signal bandwidth (fcl) shown in the Bode plot. As a rule of thumb, the compensation frequency is a decade above the zero frequency fz. Maximize current sense resistor Rs, as far as voltage swing headroom and power dissipation allow. This improves current control bandwidth. For a slope of 20dB/decade, the gain limit for high frequencies is 20dB above the DC voltage gain.

Refer to App Note #13 for details.


Stability for the Howland

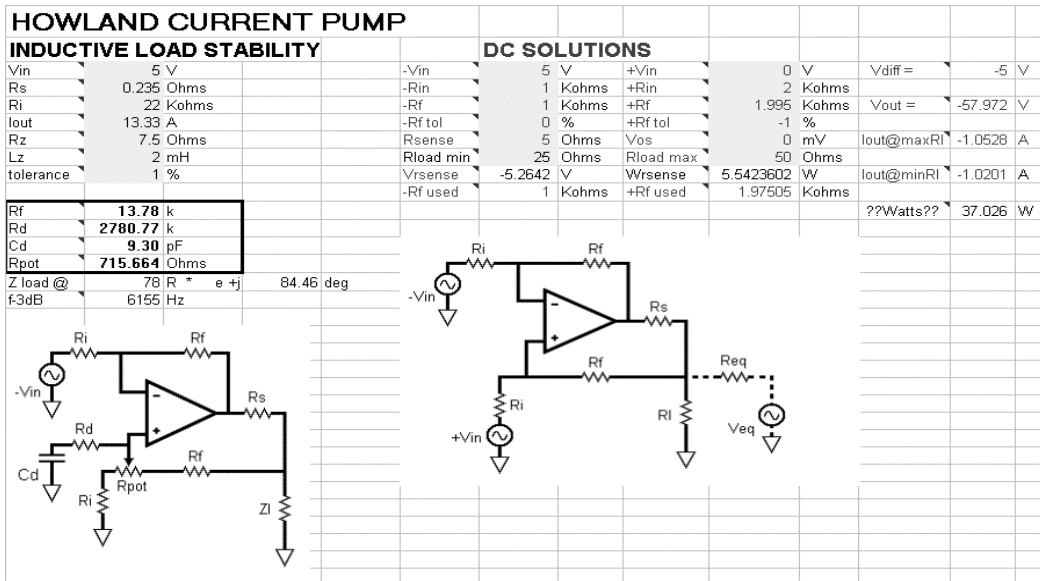

Again, Power Design eases the design burden. Cells to describe the circuit, both for stability analysis and error budget analysis. There are many other pieces of data lying outside this slide if you like to dig around. Application Note 13, Voltage to Current Conversion is the reference.

VOLTAGE-to-CURRENT CONVERSION

SINGLE SUPPLY, BRIDGE MODE

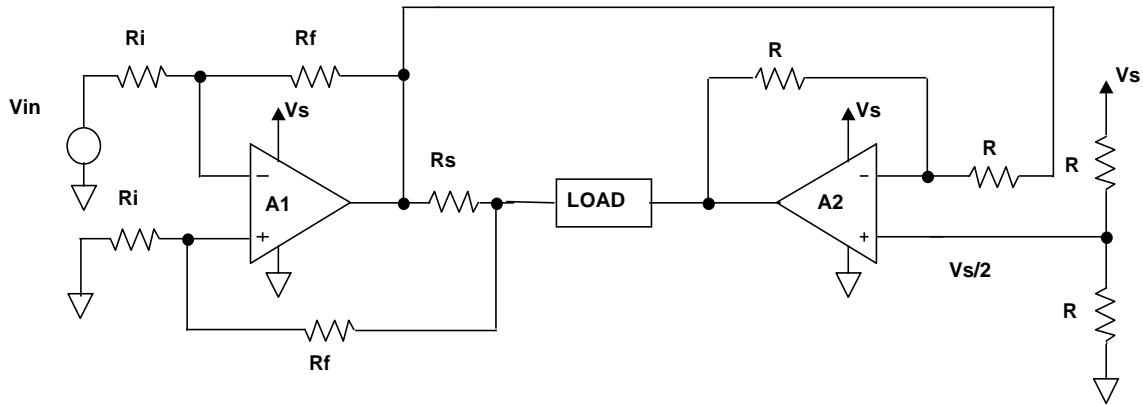

$\pm V_{load}$ LIMITED BY V_{cm} LIMITS OF A1

This configuration combines two previously covered techniques: single supply bridge configuration and V to I conversion using the improved Howland current pump. A2 is biased at the familiar $V_s/2$ mid-supply point. R_f and R_i must be ratioed such that during min and max output voltage swings of A1 the common mode input range of A1 is not violated. This imposes a max output voltage swing limit across the load. I_{out} through the load is given by: $I_{out} = (V_{in} * R_f) / (R_s * R_i)$. R_s is selected as large as possible to give as much voltage feedback as possible with acceptable power dissipation. V_{in} is set to its most positive value. V_{cm} for A1 (common mode input voltage for A1) is set to comply with data sheet specifications. Usually this will be about $V_s - 6$, which means V_{cm} must be at least 6.0 volts. R_i is selected to cause about .5 mA to flow through it when V_{in} is at its most negative voltage. This then dictates the value for R_f which is selected to complete the V_{in} to I_{out} equation given above. V_{cm} should then be rechecked for input common mode compliance at positive and negative swing out of A1. Recall that $V_{out}(A2) = V_s - V_{out}(A1)$ for the given circuit. $V_{out}(A1)$ must be at least V_{cm} to keep A1 operating in the linear region. Then $V_{load} = (V_s - V_{cm}) - V_{cm}$. In other words $V_{load} = V_{out}(A2) - V_{out}(A1)$. Therefore, the maximum output peak voltage across the load for this configuration is $V_s - (2 * V_{cm})$.


MOTION CONTROL

Position, Torque or Speed

- **Brush**
- **Micro-steppers**
- **Linear (voice coil)**
- **Multi-phase AC**
- **Galvanometers**

One of the largest applications for high power op amps is in motion control. High current high power op amps can be used for all components of motion control including speed control, position control and torque control. Their ease of use, rapid design ability and rugged hybrid construction lead to cost effective motion control systems.

Z-Axis Voice Coil Position

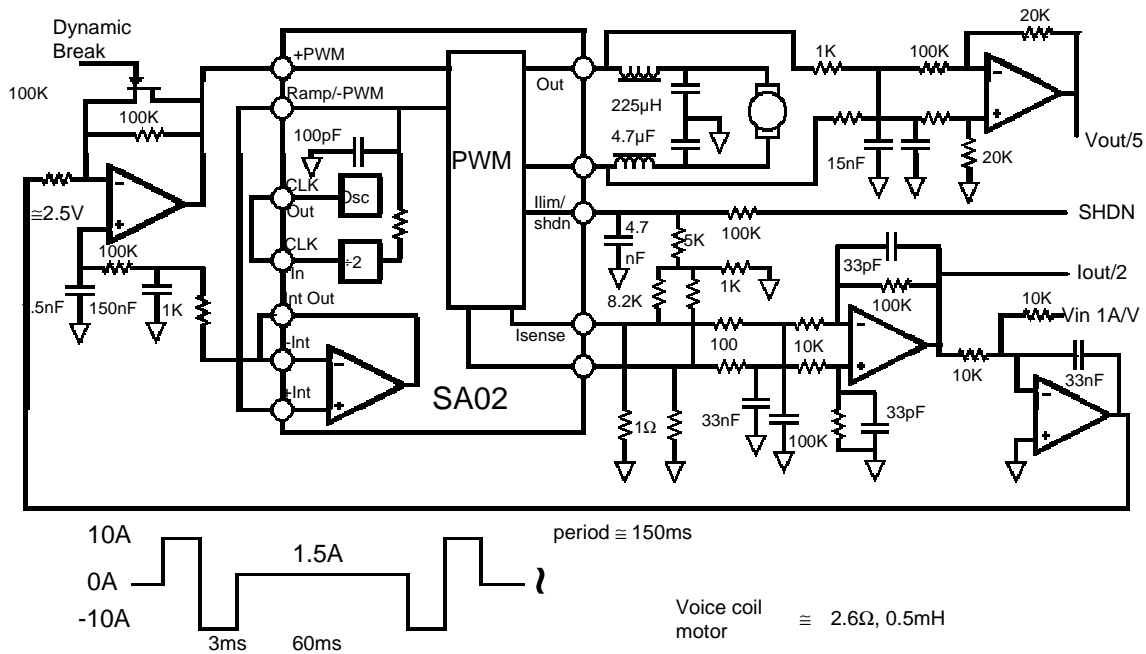

Slower versions of this machine used a PA12 linear op amp for Z-axis control. Even though currents were lower and motor impedance was higher, an exotic custom heat sink had to be designed to fit the small physical location of the amplifier. It was clear that this generation of the machine required higher efficiency in the drive circuit.

Current sense resistors of 0.1Ω develop 1V at the 10A current peaks giving very good resolution and accuracy for the differential current monitor which provides the ½V/A feedback signal. A divider network then feeds the Ilimit/Shutdown pin along with the shutdown signal added in. Filtering is per the data sheet recommendation. The external integrator now reacts to any magnitude difference between feedback and input command signals. Note that the output of the integrator is a function of ramp-to duty cycle transfer function of the PWM amplifier, V_s , internal losses and load impedance.

The internal integrator is used as only a buffer for the ramp driving a filter to derive the average DC level which is very close to the 50% duty cycle point. When the dynamic brake is applied the SA02 output is a low impedance, near zero voltage.

Even though the nominal motor inductance was adequate to keep ripple current in check, this inductance varied with position of the motor and a filter was used clean up the circuit. The voltage monitor is not part of the active control loop but aids in troubleshooting and calibration.

MOTOR RATINGS AND AMPLIFIER SELECTION

CAN PA21A BE USED?


MOTOR RATINGS:

Electro-Craft E 540A

Torque Constant: 10oz/in/A

Voltage Constant: 7.41V/KRPM

Winding Resistance: 1.24

 

APPLICATION REQUIREMENTS


10oz/in/torque

3240 RPM

24V @ 1A

Will the PA21A do? It is rated 3A peak. This application only needs 1A normally.

EVALUATION AGAINST SOA

 

$$4A \times 1.24\Omega = 4.96V \text{ ACROSS LOAD}$$

$$28 - 4.96 \cong 23.0V$$

23V WORST CASE STRESS ACROSS AMPLIFIER B

11.5V PER AMPLIFIER IF A CURRENT LIMITS FIRST


The above model provides us with a tool for analysis to examine worst case SOA stresses. This represents the condition for motor start-up or stall (not as demanding as instant motor reversal which is easily avoidable).

For this condition the motor is modeled as a 1.24 ohm resistance at stall. Assuming the PA21 current limit is at 4A results in a 4.96V drop across the load. Since it is not known which amplifier half will current limit first we must assume the worst case. If op amp B limits first all 23V of voltage stress will occur across it.

If op amp A were to current limit first or both op amp A and op amp B current limit at the same level then the voltage stresses would be equal at 11.5V across each.

For our SOA evaluation of the PA21 we will need to assume a 4A, 23V stress. In amplifiers with externally adjustable current limit we can guarantee op amp A current limits first by setting op amp B current limit 20% higher than that of op amp A and thereby equalizing voltage stresses across each op amp.

PA21 SAFE OPERATING AREA (SOA)

 

Plotted on the PA21 SOA graph are the four possible operating conditions for the PA21 when used with the Electro-Craft E540.

Point 1 is normal running condition which is well within the SOA boundaries.

Point 2 is the best case start-up condition where both op amp A and op amp B current limit at the same level or op amp A current limits first.

Point 3 is the worst case start-up condition where op amp B current limits first and bears the total voltage stress.

Point 4 is a worst case motor reversal condition with op amp B current limiting first.


It is readily apparent that with the PA21's non-adjustable internal current limit of 4A there is not sufficient SOA for driving this motor in start-up or stall conditions. Our alternatives will be either a complex soft-start circuit or power op amps with larger SOA.

PROTECTION ALTERNATIVES

PA61 — IMPROVED SOA

| START-UP | | |
|-----------------|--------------------------------|-----|
| I _{um} | V _s -V _o | |
| 10A | 8V | (1) |
| 7A | 10V | (2) |
| 4A | 12V | (3) |

| REVERSAL | | |
|-----------------|--------------------------------|-----|
| I _{um} | V _s -V _o | |
| 5A | 25V | (4) |
| 2.5A | 26V | (5) |
| 2A | 27V | (6) |

 

Often the only solution to the conflicting requirement of protection along with reasonable motor acceleration is simply an amplifier with a larger SOA. Not only does the PA61 provide a better SOA fit but the programmable current limit provides additional flexibility in meeting SOA requirements.

Points 1 thru 6 above on the PA61 SOA plot show a variety of operating choices depending upon what start-up current is desired, whether motor reversals are a possibility, and what heatsinking is available referenced to op amp case temperature.

The following handy formulae provide a quick way for estimating these points given a properly designed bridge circuit.


$$\text{START-UP: } V_s - V_o(\text{each op amp}) = V_s - (I_{\text{limit}} * \text{Motor resistance})/2$$

$$\text{REVERSAL: } V_s - V_o(\text{each op amp}) = 2 * V_s - (I_{\text{limit}} * \text{Motor resistance})/2$$

Where: V_s = total supply voltage.

If using a single amplifier rather than a bridge, delete the "/2" term. The reversal formula makes 2 assumptions: Prior to reversal, output voltage was saturated all the way to the rail and motor back EMF = V_s . This may not be true by virtue of input signal level, and cannot be true by virtue of the output voltage swing spec of the amplifier (saturation limit) and plus it requires a zero ohm motor. Despite all this it's a good first order approximation.

PA61 MOTOR DRIVE

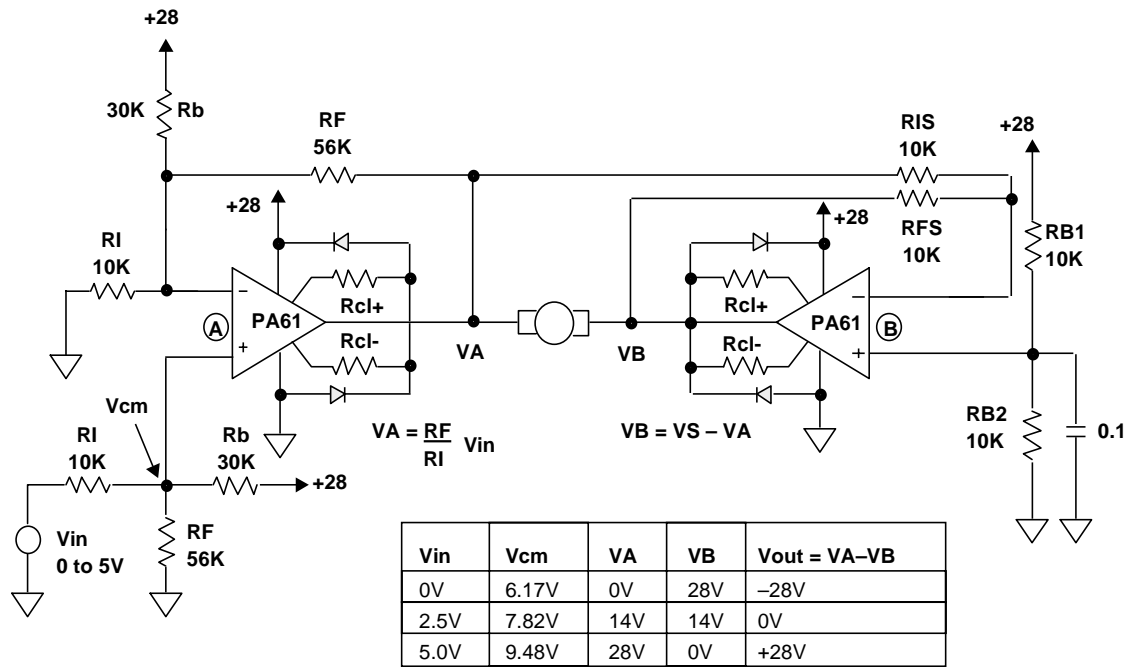


Ideal Outputs!!!

Our first alternate drive circuit for controlling the Electro-Craft motor utilizes a bridge of PA61 class “C” power op amps. Class “C” amplifiers are usually less expensive than similar class “AB” devices. While our PA61 implementation does require more components, than would our original PA21 circuit, it has the SOA to withstand start-up and even reversal conditions. Note that the PA61 has enough voltage range to handle this motor with a single amplifier. If the 28V supply is already part of the system, this may not be a good economic choice. PA73 is a 5A class “C” amplifier which would be a good candidate if high speed mechanical response is not of prime concern.

Amplifier A uses our Single Supply Non-Inverting Configuration seen previously to meet the common mode scaling requirements of the PA61. Gain scaling with this arrangement is set to try to drive the amplifier into saturation trying to achieve 0V or +28V out of the amplifier. This scaling needs to be cut back according to the saturation voltage of the specific amplifier at the specific output current level to be used. The specification is labeled Voltage Swing in the data sheet. This voltage is lost twice in a bridge circuit, once for each amplifier.

SIMPLE SPEED CONTROL

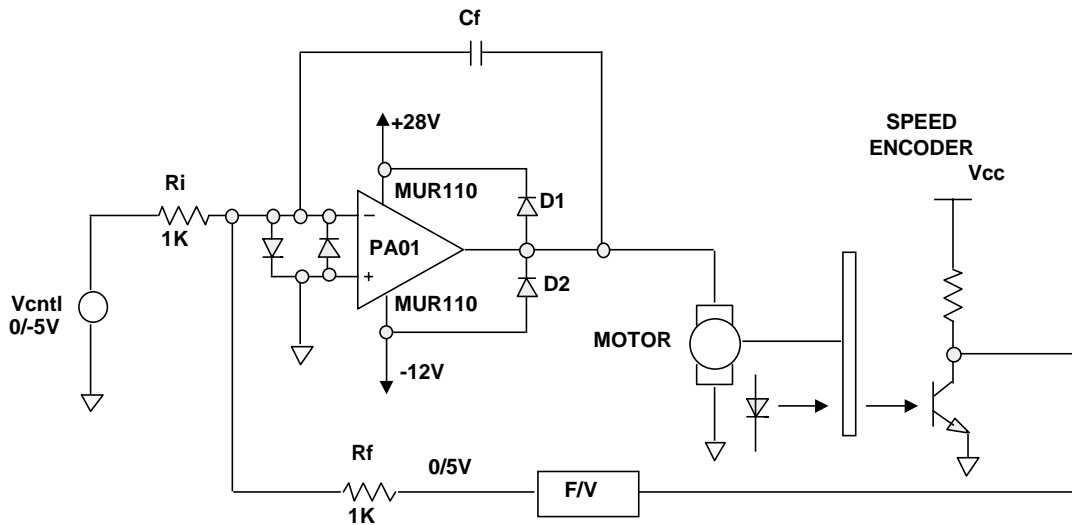


In speed control circuits the usual approach taken is to integrate the difference between an input voltage signal and a feedback signal that gives information about the speed of the motor being driven. In the application above a PA01 is being used to drive a DC motor with an integral speed encoder that outputs a pulse train whose frequency is proportional to the angular velocity of the motor. This signal is then fed to a VFC, or Voltage to Frequency Converter, that is operated in the frequency to voltage mode. The output voltage of the VFC appears across R_f to create a current into the summing node of the amplifier. Likewise, V_{cntl} appears across R_i to create a current out of the summing node. When: $V_o(VFC) = -V_{cntl}$, then no current is fed to C_f , the integrating capacitor. If there is a difference between the current fed into the summing node by the Vfc and the current removed out of the node by the control voltage the difference current is fed to the integrating capacitor resulting in a change in output voltage which acts to correct the error.

Note that since the PA01 is driving a DC motor which can generate a continuous train of high frequency kickback pulses external flyback protection diodes, MUR110's were added from the output to the supplies in order to protect the PA01's output stage.

Unless dynamic braking is used, the -12V supply needs to support amplifier quiescent current only; a maximum of 50mA for the PA01.

Multiple Antenna Elevation and Azimuth

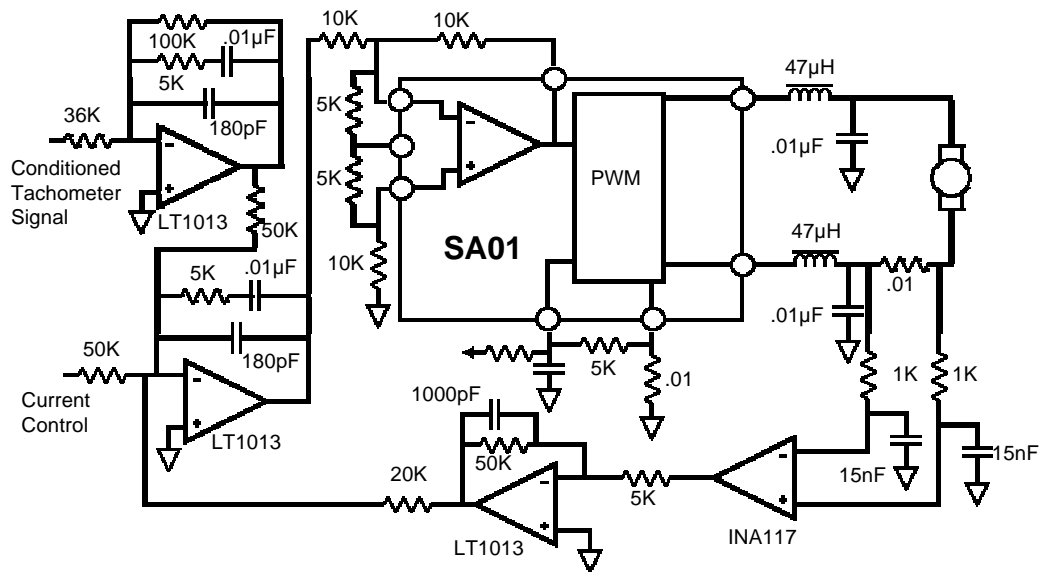


The real challenge of this application is what you don't see above; putting four of these circuits on one PC card. The motors have a minimum inductance of 300µH and have current ratings from 4.6A to 16.7A on 48V. The drive circuit needs to be universal with a current drive and a velocity loop to be used under some circumstances.

The SA01 was chosen for its size and cost even though its single current sense pin does not provide direction information. The fact that the current sense resistor in series with the motor is anywhere between zero and 48V is no problem for the unity gain INA117 instrumentation amplifier. The 1KΩ resistors of the filter networks have no appreciable affect on accuracy. The gain of 10 stage has more filtering.

The external integrator provides an accurate summing junction and easy scaling of the current command input, the velocity loop input and the current feedback signal. The internal error amplifier of the SA01 is configured as an inverting level shifter so the ±2.5V integrator output becomes the 2.5V to 7.5V needed to achieve plus and minus full scale drive to the motor.

The four SA01s share a common heatsink and fit in a single 19 inch rack along with some other power components.

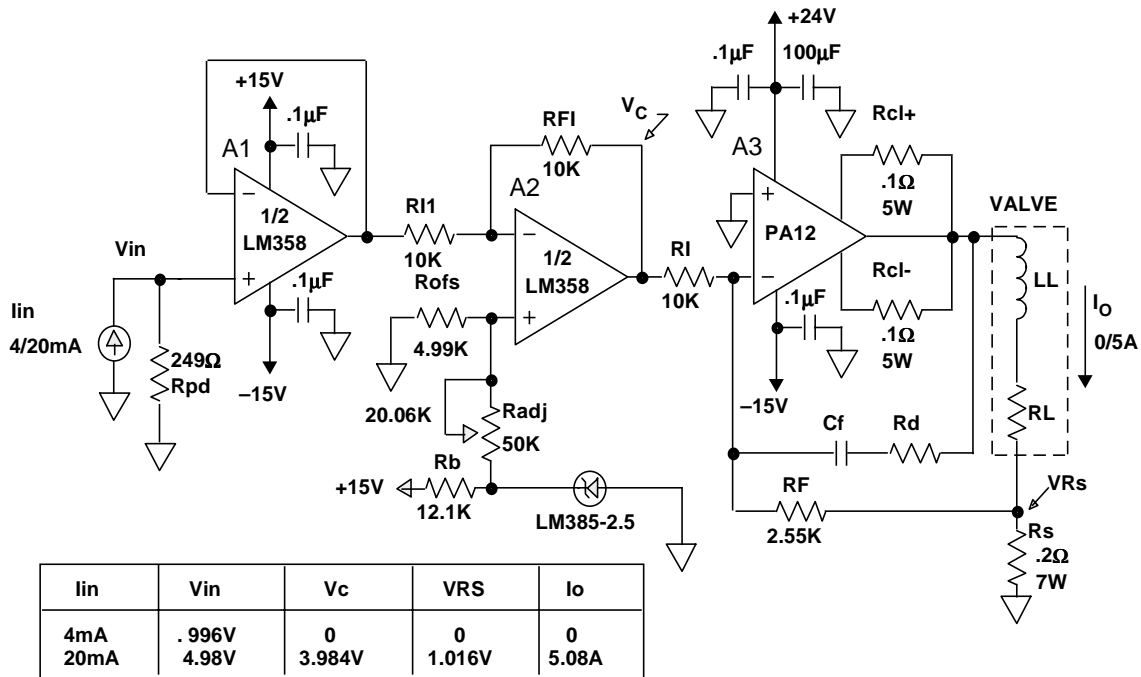VALVE CONTROL CURRENT-TO-CURRENT CONVERTER




This circuit provides a Current-to-Current converter function through translation of a 4-20mA current transmitter to 0-5A output for linear control of a valve.

The 4-20mA is converted to a voltage through the use of a 249 ohm pull down resistor and buffered by A1. This voltage, V_{IN} , is then offset to zero through the use of a precision voltage reference and a summing amplifier. Voltage V_C then becomes the input command for the Voltage-to-Current conversion output stage using the PA12.

To guarantee AC small signal stability, stability analysis needs to be done using the load resistance and inductance of the actual linear valve to be used. These stability techniques we have covered previously. Be aware that valve inductance is likely a dynamic parameter changing with position of the valve.

PROGRAMMABLE TORQUE CIRCUIT

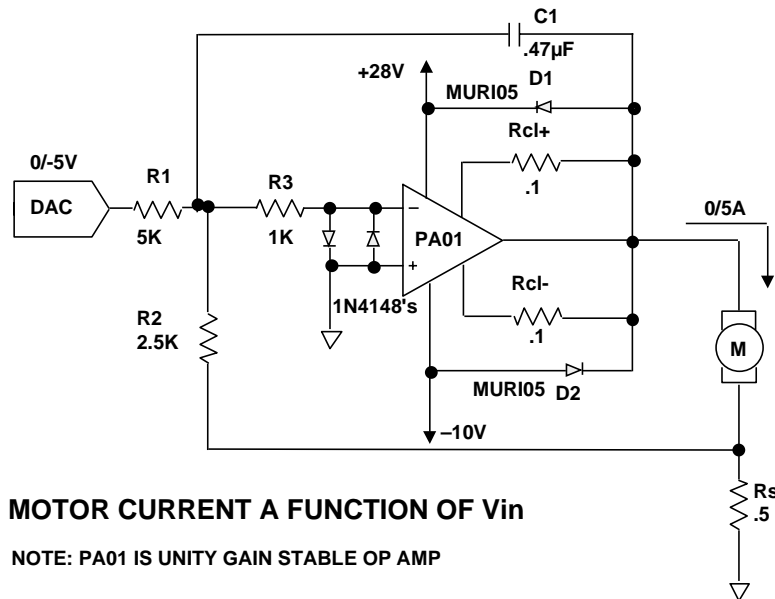


This schematic uses several tricks that we've learned. First of all, notice that the PA01 is operating from non-symmetrical supplies. The -10 volt supply is merely to provide input common mode bias. The 28 volt supply is used to supply the load current.

In a motor, torque is directly proportional to current, so this is another form of voltage to current conversion. The inverting node of the PA01 is used as a summing node. Into the summing node flow two currents, one is the input voltage from the DAC across R1, the second is the feedback voltage ($I_{load} * R_s$) across R2. These two currents are summed and the difference current is fed to C1 to be integrated. When the current through the motor is at the proper value the voltage across R_s will produce a current into the summing node that is equal to the current out of the summing node from the DAC. This results in no current flow to the integrating capacitor C1 resulting in a fixed output current.

Note that since the PA01 is driving a motor, high speed flyback diodes, MUR105s, are used to protect the amplifier's output stage against flyback voltage spikes. Also note that in integration type circuits the integration capacitor is connected directly from the output of the amplifier to the input. This means that high frequency pulses can be fed back directly to the input stage. Therefore we show 1N4148 input protection diodes and R3 in this application to prevent input stage damage to the PA01 caused by flyback coupling through C1.

LIMITED ANGLE TORQUE CONTROL

SINGLE SUPPLY

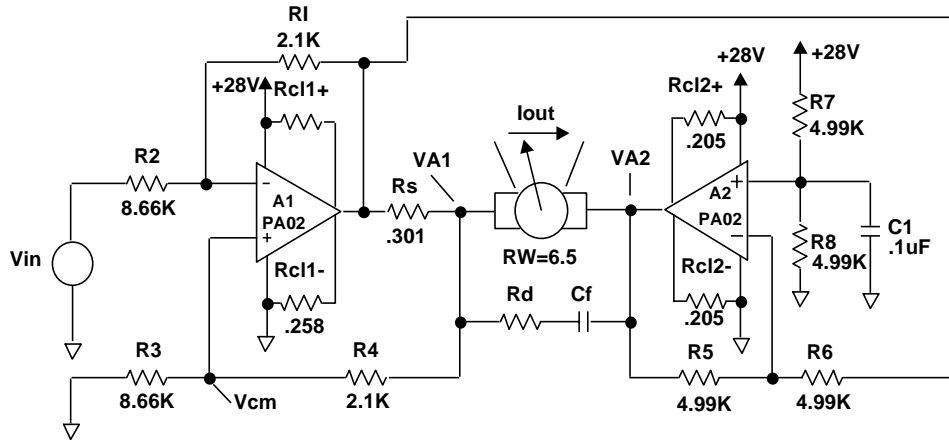

| Vin | Vcm | Va1 | Va2 | Iout |
|-------|-------|--------|--------|------|
| +2.5V | 6.0V | 7.45V | 20.55V | -2A |
| -2.5V | 16.5V | 20.55V | 7.45V | +2A |

This real world application shows implementation of the generic case of V to I single supply. It combines bridge mode operation with the improved Howland current pump. The limited angle torquer will see bipolar current changes for bipolar input voltages.

Note that the V_s –6 common mode voltage range is met under both conditions of output voltage swing on A1. Also note that the peak output voltage swing is limited to less than $V_s - (2 * V_{cm})$ as was mentioned in the generic case for this configuration.


Although we are driving an inductive load we need no external flyback diodes since the PA02 has internal fast reverse recovery diodes. A full plus and minus 2 Amps is available for position control of the limited angle torquer despite the availability of only a single supply.

ATE APPLICATIONS

- High Voltage PPS
- High Current PPS
- AC Power Supplies
- Pin Drivers
- Waveform Generators
- Active Loads

There are an extensive array of applications for high power, high voltage, and/or high speed linear amplifiers in almost any type of automatic test equipment. Some of the most popular applications include different types of programmable power supplies. There are also ample opportunities for them to be used for waveform generation for DUT excitation.

LOW DRIFT PB50 PZT TESTER

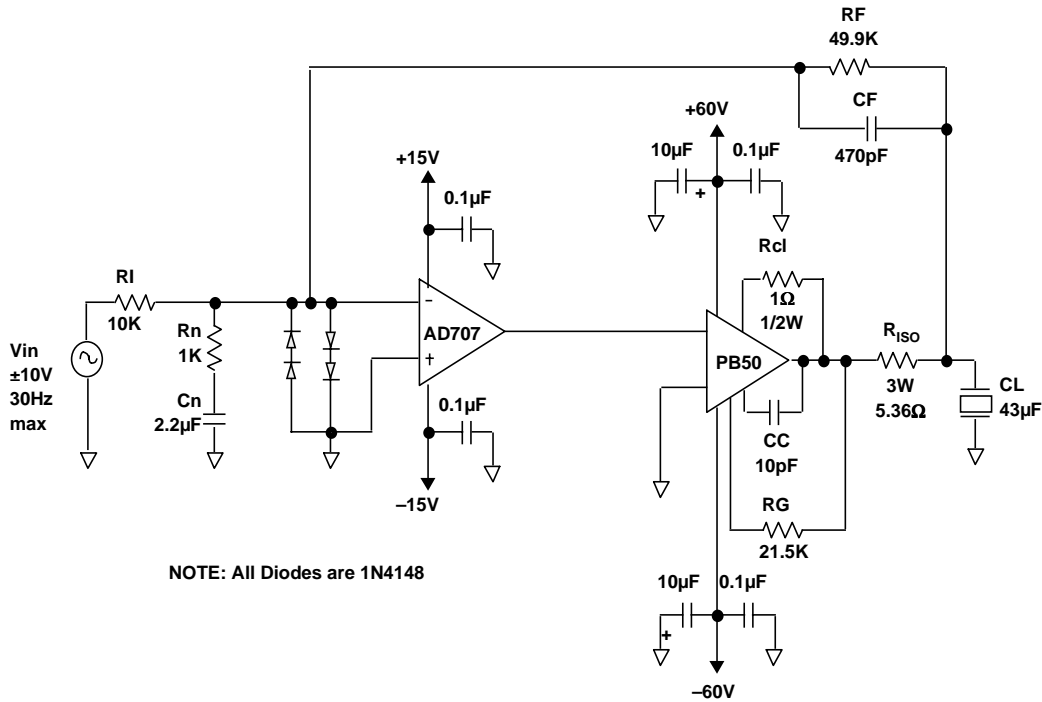


This Low Drift PB50 PZT Tester utilizes the flexibility of the PB58 power booster to provide low drift, high accuracy voltages to the PZT (Piezo Transducer) under test. The AD707 provides a composite amplifier input offset voltage of $90\mu\text{V}$, and a drift of $1\mu\text{V}/^\circ\text{C}$. Higher accuracy can be obtained with a different host amplifier or a better grade of AD707.

The PB50 is a versatile building block for ATE design that provides a low cost option for providing high voltages to devices under test. With supply voltages from $\pm 30\text{V}$ to $\pm 100\text{V}$, with a slew rate of $100\text{V}/\mu\text{S}$, and output current drive capability of 2A , The PB50 can provide up to 100KHz power bandwidth for high voltage test equipment. The composite amplifier approach for using this power booster allows the user to program the accuracy of the overall amplifier through selection of the front end host amplifier.


This particular implementation of the PB50 will present some stability challenges since we are driving a capacitive load with a composite amplifier. The approach to stabilizing this circuit will be to stabilize the power booster with its capacitive load and then stabilize the total composite amplifier. We don't stand a chance of stabilizing the composite amplifier if the output power booster is not stable first.

MAGNITUDE PLOT FOR PB50

 

Without the isolation resistor, the modified Aol curve would have changed to -40db per decade just under 1KHz giving an unacceptable intersection rate and about 2.5° phase margin rather than 90°.


COMPOSITE MAGNITUDE PLOT

 


Now that the power stage is stable we add its closed loop gain to the open loop gain of the host amplifier. Note that it is the poles of the power stage rather than the host producing the -40db per decade slope in the area of interest. A roll off capacitor gives us required slope for good intersection rate and noise gain allows good placement of the actual intersection.


In this circuit final value selection was a result of playing “what-if”, and the phase component graph was very useful. The first pole of the host amplifier is at 0.1Hz giving a 90° open loop phase shift by 1Hz. The first pole of the power stage at just under 1KHz produced 180° at less than 10KHz. Visualizing the phase components moving on the graphs and using the R-C calculator make fairly short work of the design.

COMPOSITE OPEN LOOP PHASE PLOT

 


COMPOSITE OPEN LOOP PHASE PLOT

 

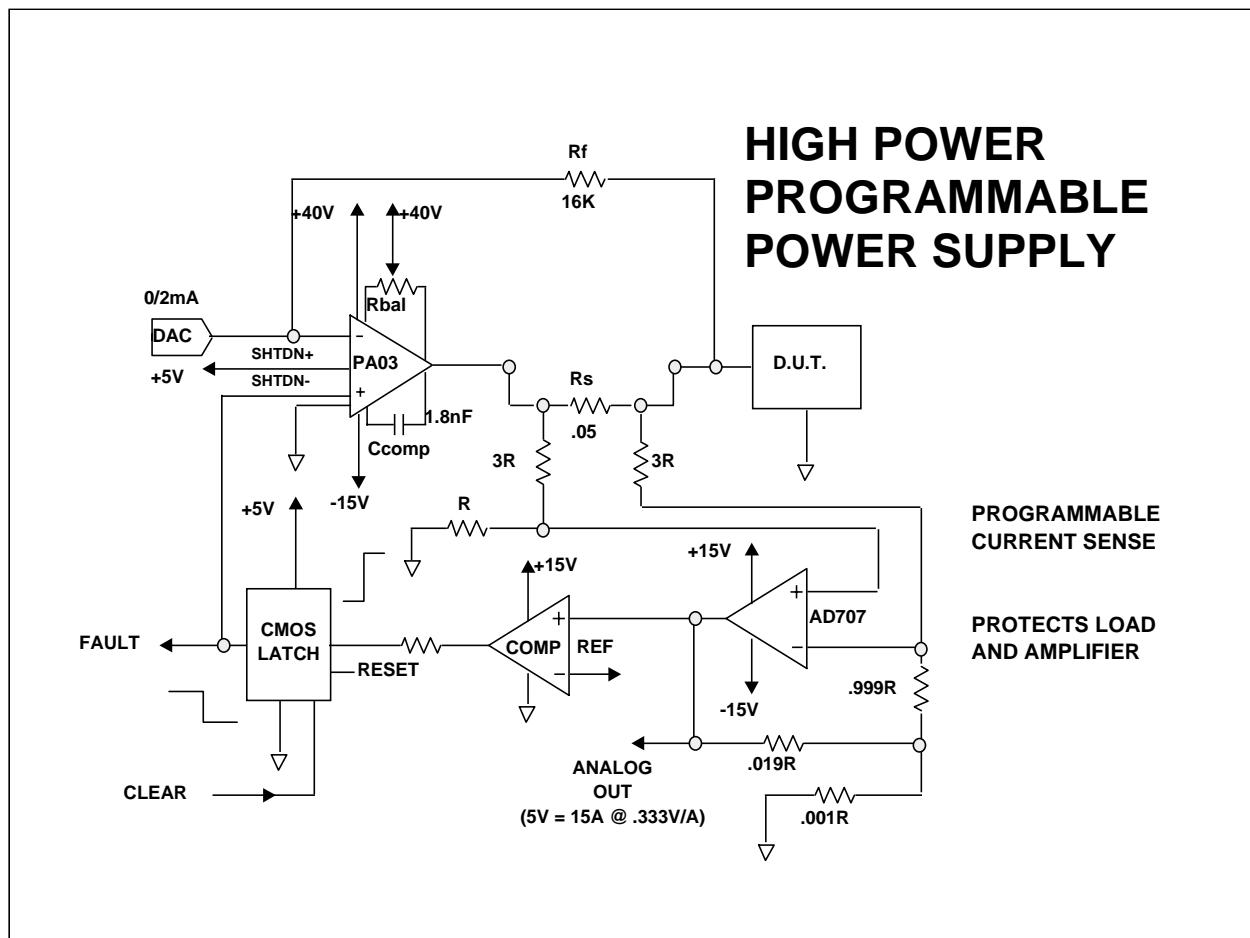

In this circuit the PA03 is being used in a simple, reliable programmable power supply which utilizes the PA03 shutdown features. It requires little calibration because the current to voltage conversion of the DA converter output is done by the power op amp itself while a 12 bit DAC (i.e. DAC80) provided accuracy levels high enough to eliminate the need for adjustment. R_s senses current to the DUT. The AD707 is configured as a difference amplifier which senses the voltage across R_s and develops an analog output signal proportional to DUT current through R_s . It is then compared to a reference voltage which determines the current level desired. The comparator will trip high once this current limit is exceeded thus tripping a CMOS latch low and resulting in a 5V differential signal between the two shutdown pins on the PA03. This circuit is explained in detail in Application Note 6 in the Apex Data Book.

PWM Alternative

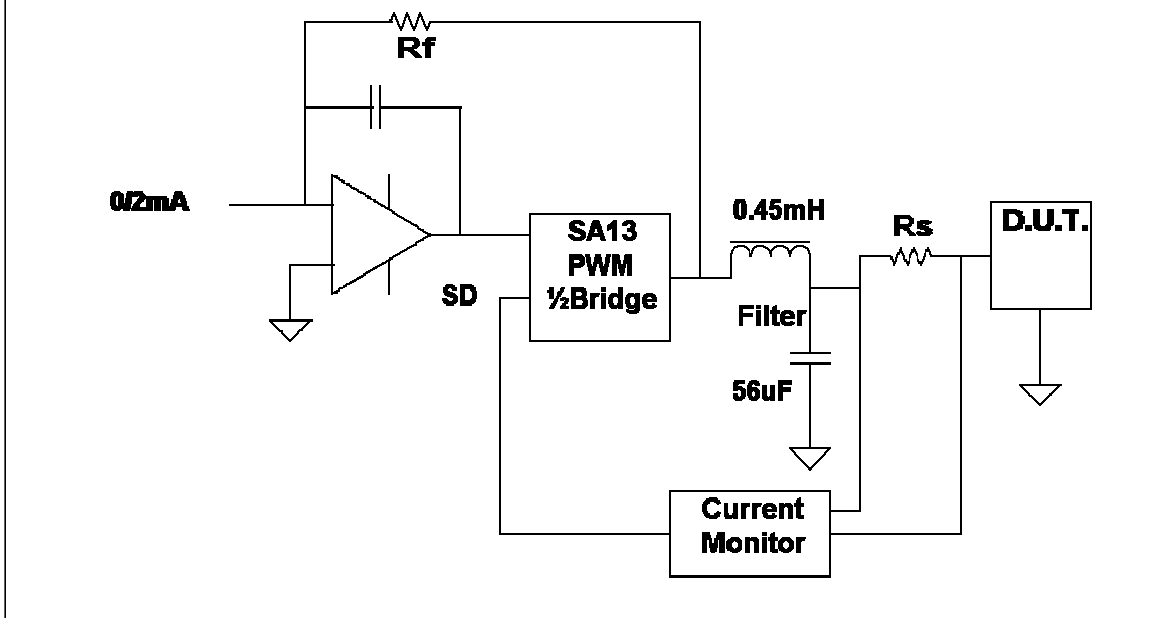

The PA03 works fine but is not suitable for longer duration or higher supply voltage.

This PWM alternative keeps the same overall function and programming but reduces power dissipation dramatically. For the same test sequence described in Ap Note 6, average power is reduced by a factor of 6. The better news is that the PWM version is capable of continuous operation while dissipating only 30W compared to 306W (liquid cooling is a must) for the linear counterpart. As an added benefit, a more standard 48V supply can be used while adding very little power dissipation.


As mentioned before, the PWM circuit has more noise than the linear. The simple filter shown is capable of keeping ripple down to 100mV peak. Higher order filters can do even better.

Speed differences between linear and PWM circuits will be less than you might think. ATE test sockets almost always have large bypass capacitors. This capacitance will demand large currents to charge quickly thus being the speed bottleneck for both types of circuits. Again, good news: A single capacitance can function as filter element and bypass for the DUT socket.

On an amplifier cost basis (@100): PA03 \$350


SA13 \$265

REMOTE SENSE

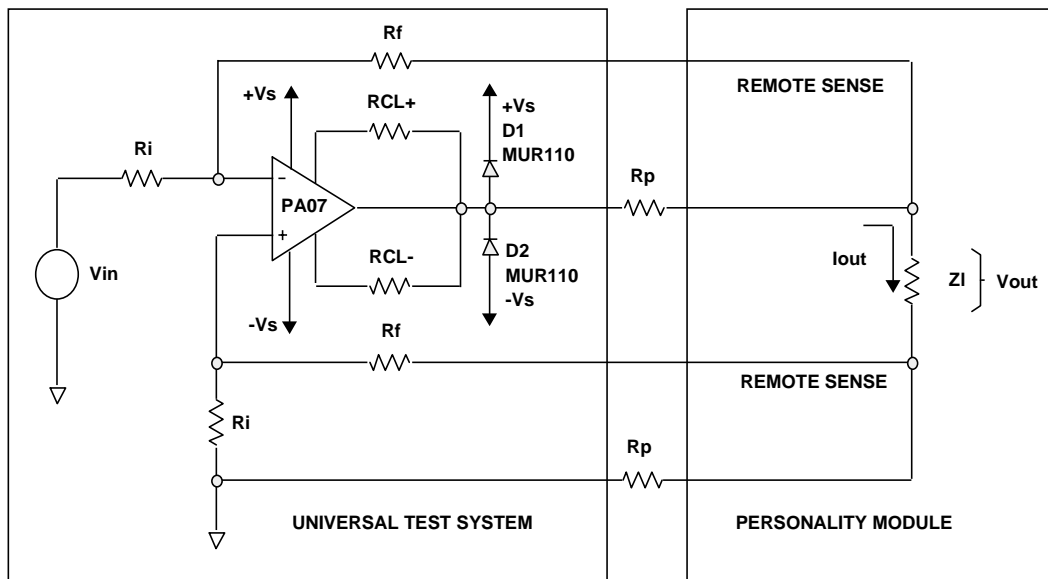


Universal test stations often contain a power op amp that is used to provide power to some remote load. If significant amounts of current are being delivered to this remote load, the parasitic resistance of the wiring can contribute significant errors to the measurements. For instance, 50 milliohms of wire resistance in the output and return line would result in an error voltage of 500mV with a 5A load current. When the power amplifier is configured as a differential amplifier, with the differential plus remote sense and minus remote sense lines being run directly to the load and connected across the load at the remote site, drops from the parasitic resistances become common mode signals to the difference amplifier and are rejected due to the high CMRR of the amplifier.

DRIVEN GROUND

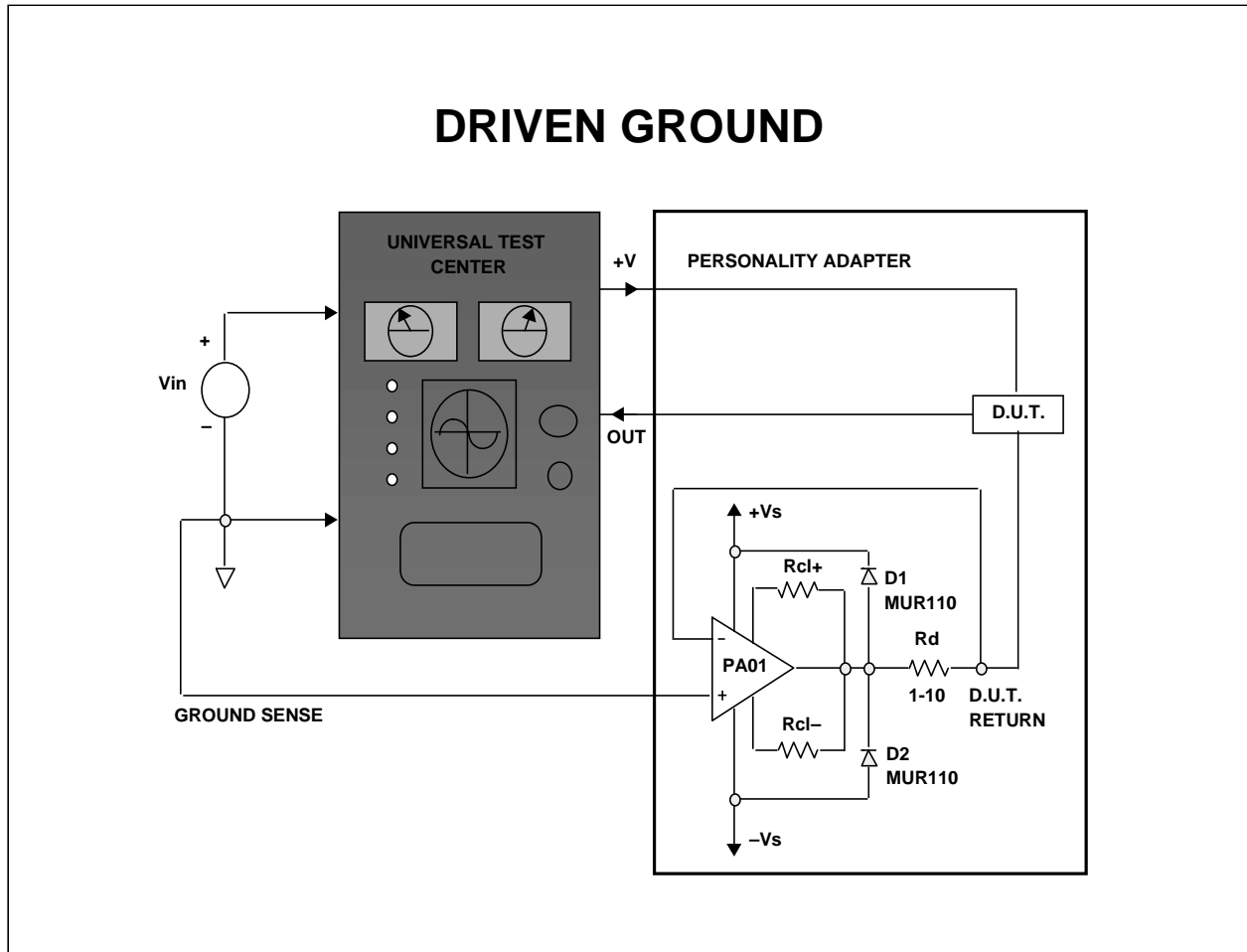

Often a test rack is located quite a distance away from the actual test head where the DUT is being excited, or where measurements are being made. When the equipment at the personality adapter or the test head dumps a significant amount of current into a ground return line, enough voltage may be developed between the personality adapter and the universal test station to contribute significant errors to whatever measurements are being made. One way to solve this problem is to eliminate current flow in the ground line. This circuit accomplishes that feat by taking the reference ground from the universal test station and running a "ground sense" line over the personality adapter. This line is now used as a reference voltage input to a unity gain follower — in this case the PA01. The PA01 is used to generate a "remote ground." Now the ground current from the DUT or remote test equipment is dumped into the output of the PA01 where it is returned to one of the remote supply lines. The 1-10 ohm series resistor is used to keep power dissipation outside of the amplifier and have it dissipated in the resistor instead. Its value should be chosen such that the I_{max} (ground current) $\times R_s = V_o$ max of the PA01.

HIGH VOLTAGE PPS

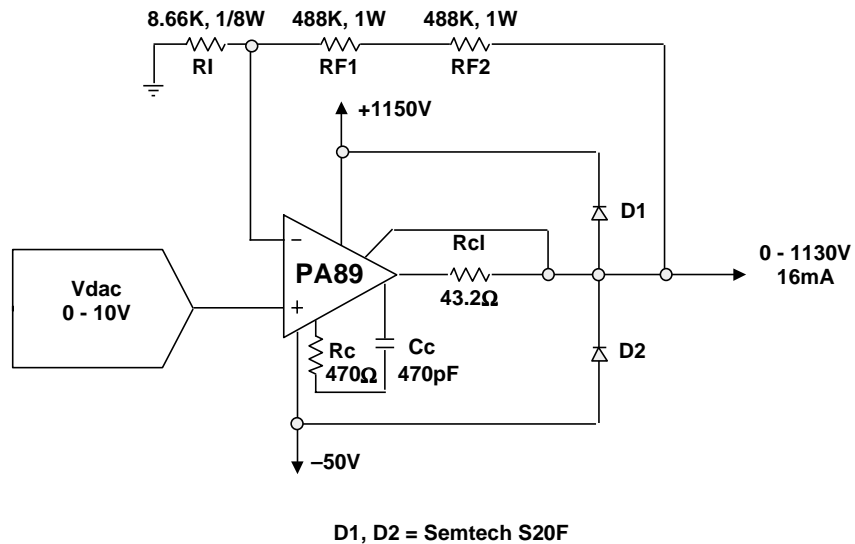

This high voltage programmable power supply utilizes the full voltage capability of the PA89. It uses asymmetrical power supplies to eliminate the necessity for biasing up the front end input DAC voltage to comply with common mode voltage requirements of the PA89, as well as providing adequate voltage headroom at the output so it can swing down to zero.

Although the PA89 can be used single supply, it ends up requiring large value resistors and high wattage resistors to bias the front end to comply with the input common mode voltage specification of $\pm V_s/2 + 50$. The output would only be guaranteed to swing within 20 volts of ground. Asymmetrical power supplies, as discussed earlier, eliminate both of these problems.

With the current limit set at 16mA the PA89 can withstand a fault condition of a short to ground on the output by using an Apex HS06 heatsink, a TW05 thermal washer, and in a 25°C ambient environment, free air convection cooling.


Although the PA89 generally works at low currents (<60mA), power dissipation is still a major design consideration due to the high voltage (remember $P = V \times I$).

As a high voltage amplifier the PA89 does present some unusual design considerations. The following is a quick check list of support components requiring special attention:

- 1) Cc—Compensation capacitor will see nearly the full supply voltage. In this case 1200V. Because of corona effects and partial discharge, this capacitor must be rated at twice the total supply voltage. Lower ratings can cause amplifier destruction.
- 2) RF1 and RF2—Feedback resistors must be selected for power dissipation, voltage coefficient of resistance, and voltage breakdown rating.
- 3) D1 and D2—Flyback diodes must have a peak inverse voltage rating of the total supply voltage. Here we need a 1200V PIV rating minimum.

Expandable AC PPS

150/300V 47/440Hz 750W

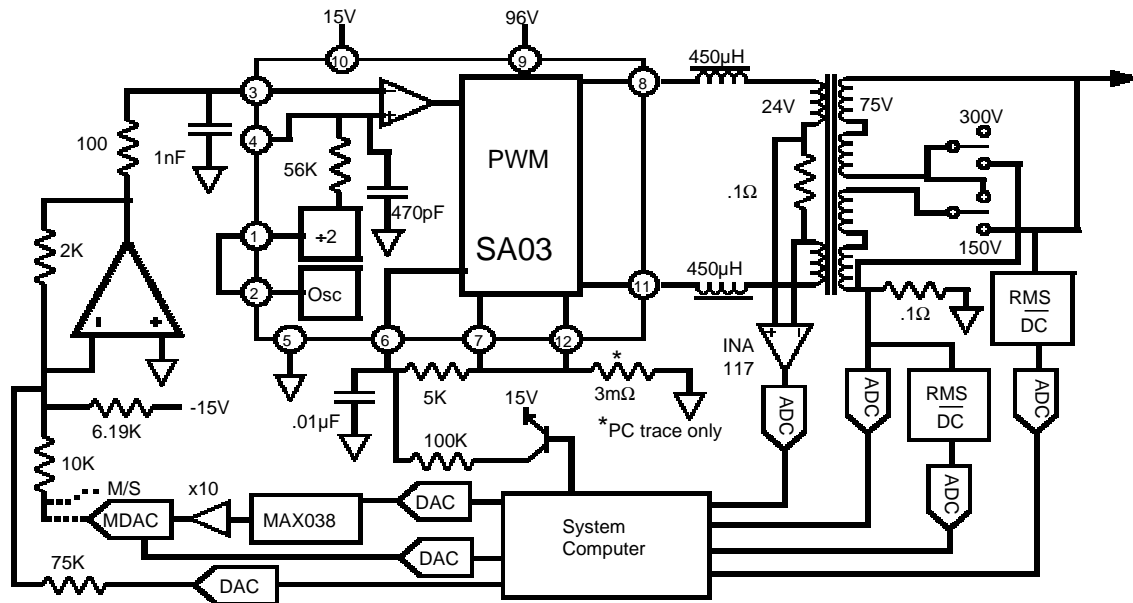


In local terms this SA03 is running open loop but overall operation is closed loop by virtue of the system computer monitoring performance and making adjustments per calibration tables and correction algorithms.

The MAX038 waveform generator 1Vpk is stepped up to 10Vpk going into the multiplying DAC. The summing amplifier is scaled for maximum peak output of 2V and is offset about 5V. The scaling for the DC correction signal is about $\pm 250\text{mV}$. The AC signal jumper allows master or slave operation of the module.

First order theory (only) dictates the power transformer should have more than enough inductance to do all the filtering. Cores used for low frequency power do not work well at all with 22KHz square waves, so some filtering is required. Using $450\mu\text{H}$ sets the pole at 435HZ and will keep 22KHz ripple current below 1.2Apk. This may need adjustment depending on the specific power transformer. The split primary allows current monitor signals containing very little AC common mode voltage.

Versions of this circuit with out programmable frequency have replaced variacs to increase voltage change speed thereby increasing value of the ATE. Another version uses step a down transformer testing very high current circuit breakers.

AC PPS Expansion

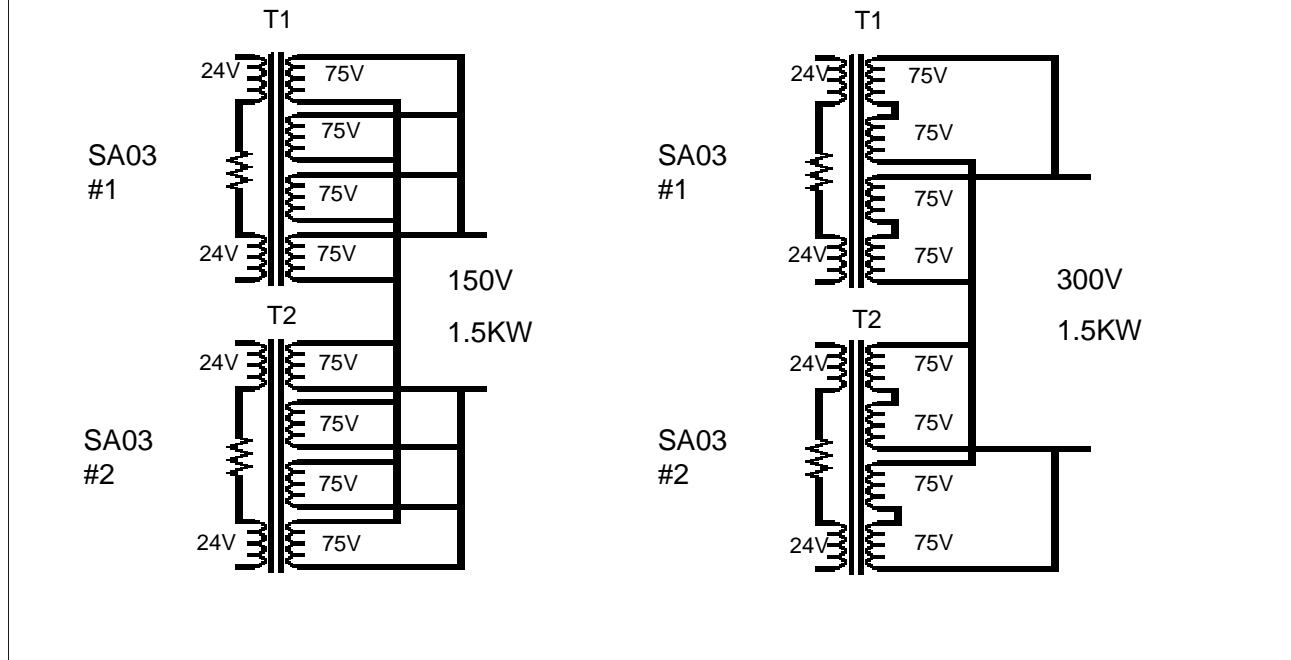


Yes, there really was a reason for four secondaries in the previous slide. With a slave module importing the AC signal from the master the two amplifiers will be in phase at the signal frequency even though they may not be in phase at the switching frequency.


Power doubling is achieved by adding at the transformer stage rather than actually paralleling the PWM amplifiers. Frequency and magnitude are controlled by the master only, but the slave does use its own DC correction loop. Shown here are basic hoop-up for two voltage ranges with 1.5KW power capability.

The master/slave approach allows interchangeable modules in 750W and 1500W test systems.

SOURCES

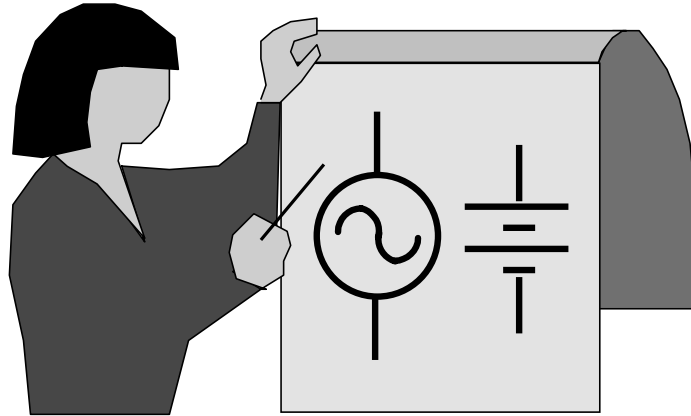

VOLTAGE REGULATOR WITH PB58

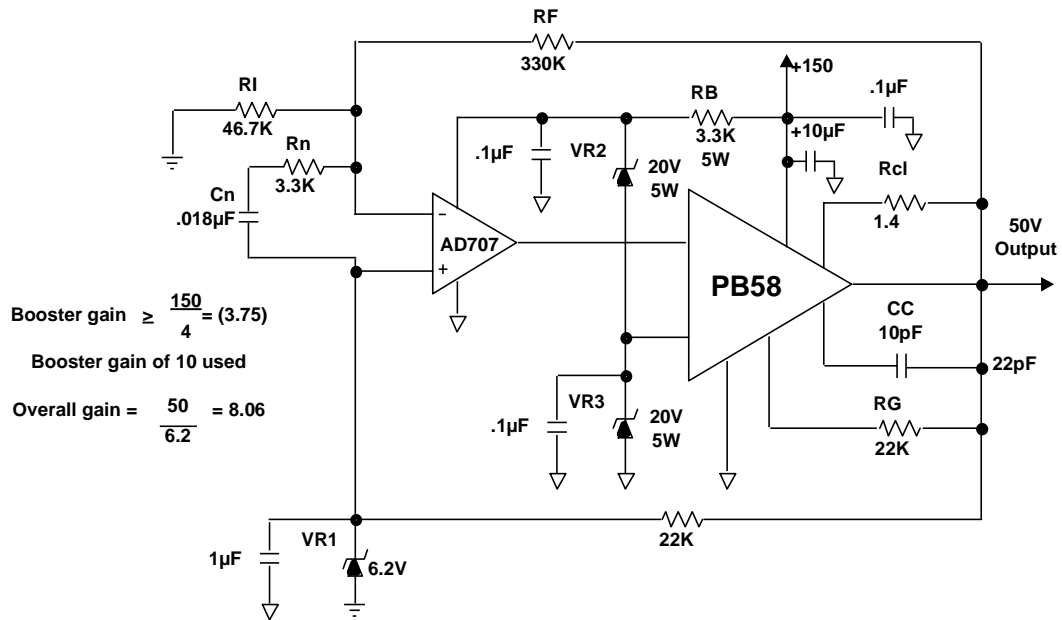


At first this may not seem to be the least costly approach to voltage regulator design. However, there is no packaged solution to regulating 150 volts down to 50 volts while being able to provide up to 500 mA (PB58 is rated up to 2A, but SOA limits us to 500 mA in this application). This regulator has both good source and good sink regulation characteristics.

This application does serve well to illustrate PB58 design techniques, and some of the limitations to be aware of. For instance, in normal applications the negative supply of PB58 must be 15 volts more negative than ground. In this application we have created a quasi-ground at the junction of VR2 and VR3 which meets this requirement. VR2 and VR3 also provide regulated supply voltage for the driver op amp.

The reference zener source is derived from the output of the regulator to improve supply rejection. The overall gain is whatever is necessary to multiply the 6.2 volt reference VR1, up to the required output voltage. In this case a gain of 8.06 for a 50 volt output. In the next few slides, we'll discuss stability considerations in the booster application.


COMPOSITE MAGNITUDE PLOT

 


This circuit is not battling capacitive loading or inductance in the feedback path and each part of the composite would be stable on its own but the composite open loop gain reaches a slope of -60db per decade before crossing 0db.

While a DC gain of 100 (A short in place of Cn) would have made the circuit stable, the DC errors due to offset and drift would have been objectionable. Including Cn keeps DC gain at the desired level and produces a stable circuit.


COMPOSITE OPEN LOOP PHASE PLOT

 

COMPOSITE OPEN LOOP PHASE PLOT

 

400 Hz SERVO SUPPLY

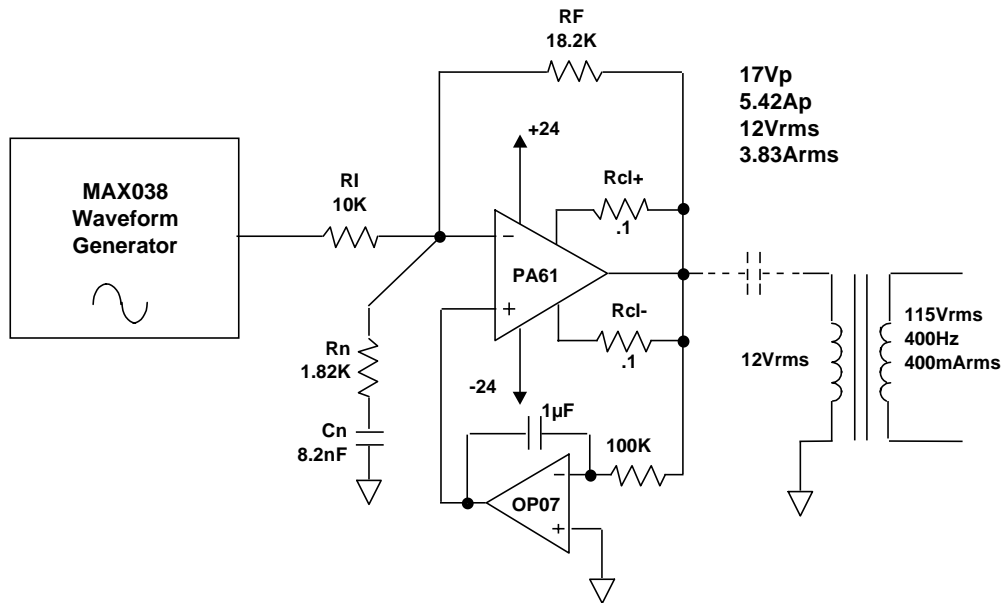


This 400Hz servo supply uses a separate oscillator to maintain oscillator stability under varying load conditions. The PA61 provides a gain of 1.8 to match the output of the industry standard 8038 waveform generator IC to the primary of a 12V to 115V step-up transformer.

The input R-C network is selected to provide unconditional stability on the PA61 with a phase margin of 45° in the 100Hz to 3kHz region. Phase margin increases to 90° at the 100kHz small signal bandwidth of this circuit. This extra phase margin allows for parasitic cable capacitance and/or capacitive loading on the output of the PA61 with guaranteed stability. The capacitor is selected for a corner frequency of 10KHz since this is well away from the 400Hz signal yet low enough to control any stability problems.

Note that the power supply is set to a value just large enough to accommodate the signal amplitude plus the amplifier's worst case output voltage swing specification. The use of minimum power supply voltage minimizes dissipation and improves efficiency.

If AC coupling should lead to unmanageable size bipolar capacitors, use an integrating amplifier (OP07 in this example) to compensate for offset voltage.

LOW POWER TELEPHONE RING GENERATOR

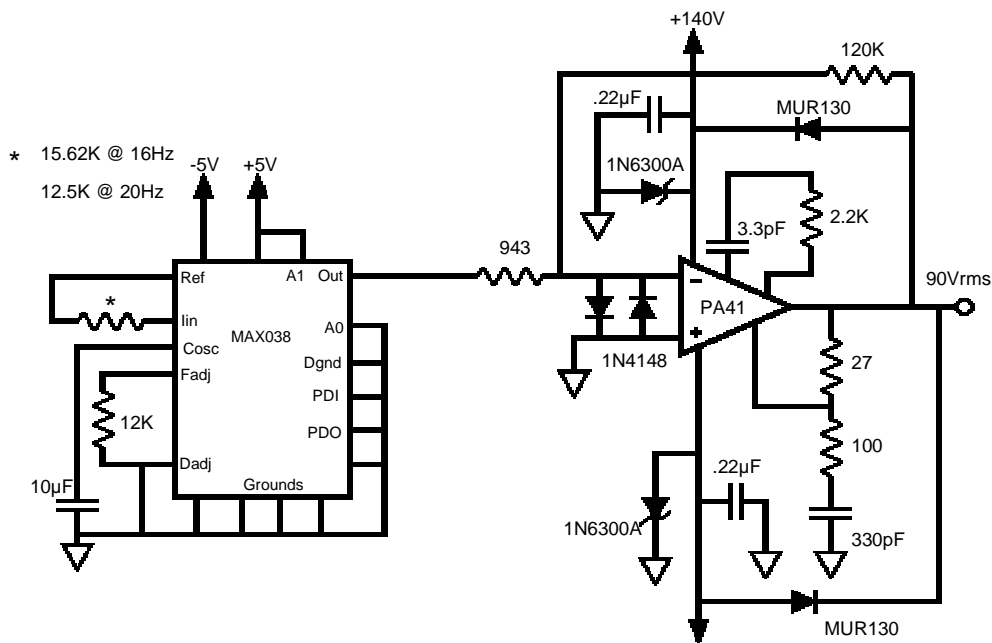


The MAX038 provides a 2Vp-p low distortion output signal. The PA41/42/44 is set for a gain of 127, boosting the overall output to 90Vrms. The recommended compensation for gains above 30 is used. If capacitive loading is at least 330pF at all times, the recommended snubber network may be omitted. The 27Ω resistor sets current limit to a nominal value of 111mA to insure peak currents of at least 88mA or 5.6W delivered to the load. This places total power dissipation at 3.8W, a level easily handled by the PA41 or PA42. Unless exotic heatsinking methods are employed, the PA44 is typically limited to about 2W. The 3.8W figure assumes resistive loading and ignores the possibility of a shorted output. Power levels must be reduced if reactive loads or shorted loads are to be encountered.

The MUR130 diodes shunt any energy on the output to the supply rails which are in turn protected against overvoltage transients by the IN6300A transient voltage suppressors.

With the high voltage stage being a simple inverting circuit, it is very easy to scale the output down or up to 115Vrms. Summing in a DC offset could be done just as easily.

HIGH POWER TELEPHONE RING GENERATOR

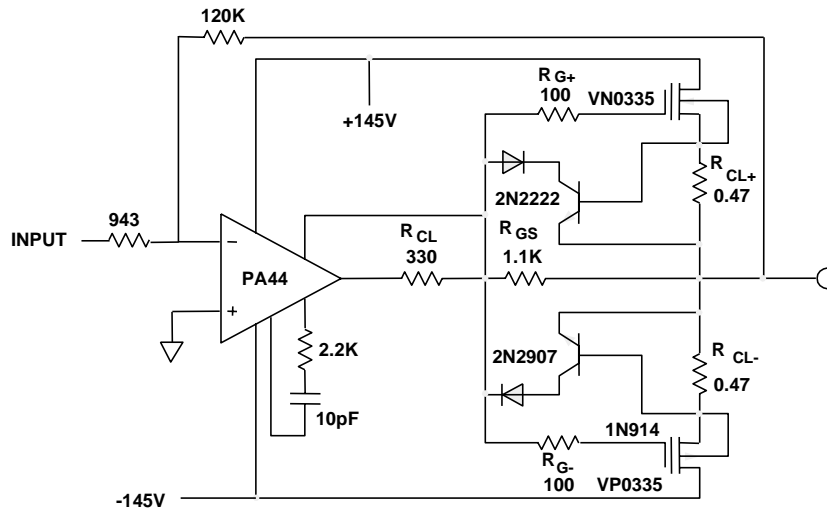


The signal source, protection requirements, and the basic operation shown here is the same as in the low power ring generator. Power supply bypassing and the use of a star grounding become much more important as power levels increase. To enable the ringing of more lines, external MOSFETs have been added. The choice of specific MOSFETs is determined entirely by current, voltage and power dissipation requirements. There are no radical differences among the different MOSFETs regarding threshold voltages or transconductance. Note that each MOSFET must be rated to handle the total supply voltage, 300 volts in this case.

Current limits have been set to a nominal of approximately 1.4A. Allowing for a 20% tolerance insures outputs of 1.1A pk or 0.78Arms. At 90Vrms, output power will be 70W and the peak dissipation requirement for each MOSFET will be 45W. At typical ringer frequencies the MOSFETs need to handle the 45W. Thermal averaging of the heatsink allows designing for 45W for the total amplifier or 22.5W per MOSFET if using multiple heatsinks.

The 330Ω current limit resistor sets the PA44 current limit to approximately 9mA. This current flowing across R_{GS} limits drive voltage on the MOSFETs to 10V. Worst case power dissipation in the PA44 will then be 1.3W due to output current plus .6W due to quiescent current totaling 1.9W. Unless you are willing to cut holes in the PC board to contact the bottom of the surface mount package with an air or liquid cooling system, this is about the limit. Typical operation will generate less than 1W in the op amp. Replacing R_{GS} with a bi-directional zener will allow a cooler running op amp at the cost of increased distortion.

THERMO-ELECTRIC COOLER

SINGLE
SUPPLY
BRIDGE

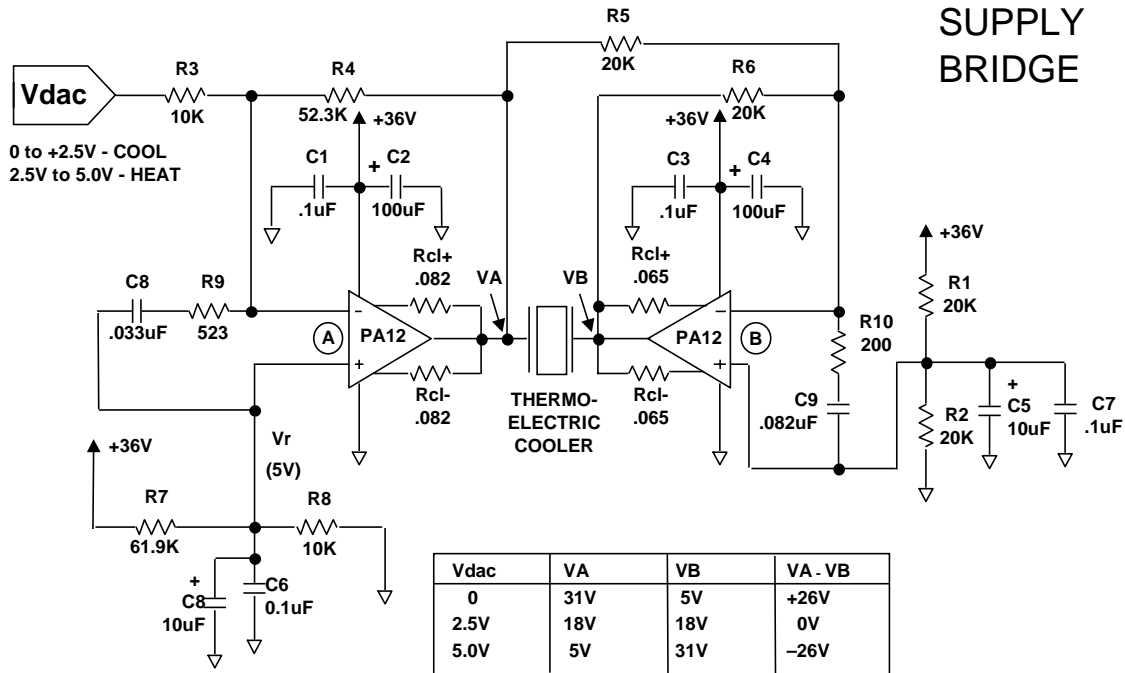

- $V_{out} = V_A - V_B$
 $MAX V_{out} = +V_s - V_{satA} - V_{satB}$
 $= 36V - 5V - 5V = 26V_p$
- $Gain = V_{outpp}/V_{inpp} = (V_A - V_B)_{pp} / V_{inpp}$
 $52V_{pp}/5V_{pp} = 10.4$

Gain = $2 R_4/R_3$ since we have a bridge configuration.

The voltage gain across the load is twice that of the master amplifier, A, since +1V out of the amplifier A yields -1V out of amplifier B, relative to the mid point power supply reference of +18V.

Therefore $R_4/R_3 = 5.2$

- Offset

$$V_A - V_B = +V_s(2(1 + R_4/R_3) \frac{R_8}{R_7 + R_8} - 1) - 2(R_4/R_3)V_{dac}$$

But when $V_{dac} = 0$ then $V_A - V_B = +26V$

Using $R_4/R_3 = 5.2$ and solving above yields $R_7 = 6.2 R_8$

Choosing $R_8 = 10K$ implies $R_7 = 61.9K$


- Check for common mode voltage compliance:
 $5V$ meets the minimum common mode voltage spec.

DEFLECTION

- Electromagnetic
- Electrostatic
- Dynamic Focus Control

High speed power op amps are ideal candidates for all types of deflection uses. High current, high speed models are ideal for electromagnetic deflection. Models with rapid slew rates and extended supply ranges allow rapid di/dt of the yoke being driven. High voltage models are especially useful for electrostatic deflection and/or focus.

MAGNETIC DEFLECTION AMPLIFIER SELECTION

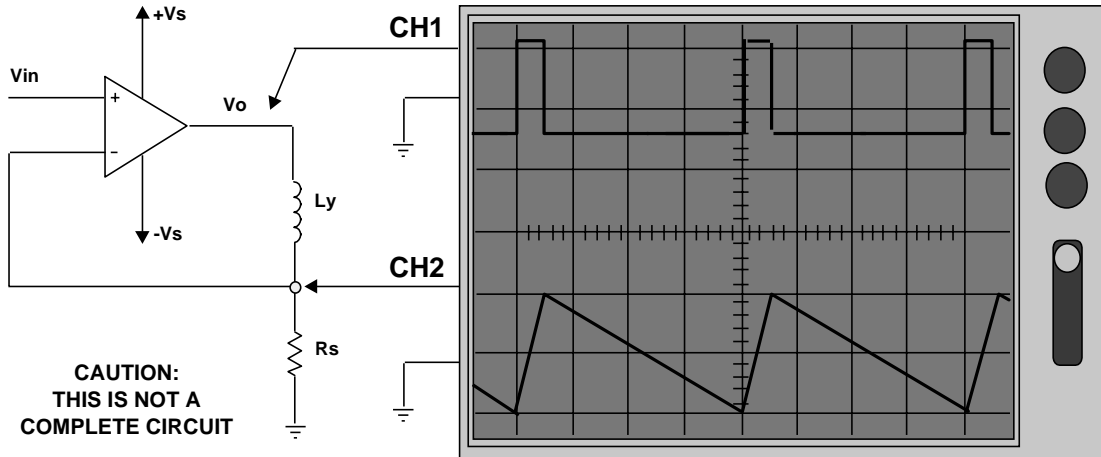


$$V_{rs} = I_o V_{rs} \quad V = L \frac{di}{dt}$$

An amplifier selected for magnetic deflection must have an adequate slew rate and voltage rating to slew the current in the yoke fast enough.

These two considerations go hand in hand since the rate-of-change of current in the yoke is proportional to applied voltage. And the amplifier must slew to this applied voltage at least 10 times faster than the rate of change of current to achieve truly fast and accurate magnetic deflection.

ELECTRONIC DEFLECTION (V - I CIRCUIT)

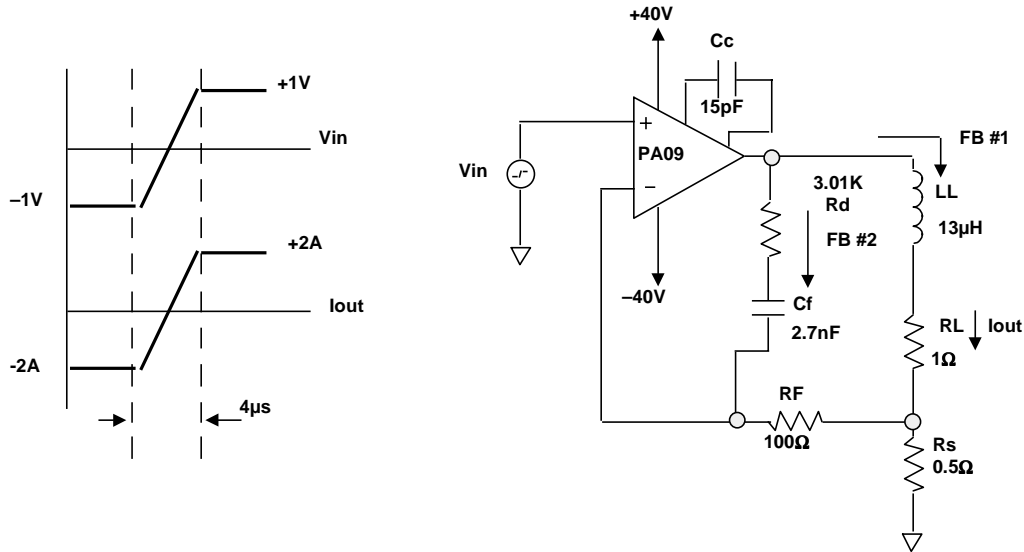

AMPLIFIER SELECTION

STEP 1: VOLTAGE

$$V_{LL} = LL \frac{Dip-p}{dt}$$

$$V_{LL} = 13\mu H \frac{4A \cdot 13V}{4\mu s}$$

$$V_s = V_{LL} + V_{RL} + V_{R_s} + V_{sat}$$

$$V_{s \text{ MIN}} = 13V + 2V + 1V + 8V$$

Where: $V_{RL} = I_p R_L$

$$V_{s \text{ MIN}} = 24V$$

$$V_{R_s} = I_p R_s$$

STEP 2: CURRENT From desired Iout, current must be 2A.

STEP 3: SPEED

A design rule of thumb for good performance is to select an amplifier with a minimum slew rate equal to 10 times faster than the desired current slew rate, faster will be better.



$$S.R. \text{ MIN} = \frac{V_{S \text{ MIN}}}{(.1) dt}$$

$$S.R. \text{ MIN} = \frac{24V}{(.1) (4\mu s)} = 60V/\mu s$$

STEP 4: PA09 and PA19 meet or exceed these requirements. PA09 is less expensive.

PA09 Deflection Setup

| STABILITY FOR INDUCTIVE LOADS | | | | | | |
|-------------------------------|----------------|----------|------------|-----------------------------|-------------------------------|------------------------------------|
| MODEL | PA09-150 | Note/PBs | Rin | 9999999999 Kohms | Estimated Closure Frequency = | 3162.278 KHz |
| Rs | 0.5 Ohms | Rf | 0.1 Kohms | Suggested maximum bandwidth | 177827.9 Hz | |
| Lload | 0.013 mH | Cf | 2.7 nF | Estimated Closure Rate = | 20.0 db/decade | |
| Rload | 1 Ohms | Rd | 3.01 Kohms | Estimated Phase Margin = | 45.63 Degrees | |
| Is this a Composite? | | | No | | | |
| Notes: | | | | | | |
| R-C Pole Calculator +: | | | | | | |
| 3.01 Kohms | Rd Kohms | 1.16509 | AC gain db | 30 | 28 Print Data, Bode & Phase | 29 Print Data, Bode, Phase & Parts |
| 20000 Hz | Rd Kohms | 2.9 | Rd Kohms | 3.062278 | | |
| 2.6438 nF | Cf nF | 2.081381 | | | | |
| Ri/(Ri+Rf) | 1 | | | | | |
| Equiv Z @ Rs | 0.5 Ohms | | | | | |
| Requiv/(Ri+Requiv) | 0.333333333 | | | | | |
| DC Beta | 0.333333333 | | | | | |
| DC Gain | 9.542425094 db | | | | | |
| Zero R/L | 18364.0319 Hz | | | | | |
| Rin Rf | 0.1 Kohms | | | | | |
| Zero Rd/Cf | 19583.48013 Hz | | | | | |
| AC Gain | 29.85520778 db | | | | | |
| Zero Cross | 177827.941 Hz | | | | | |

  



Set up the basic circuit in Power Design to see we have a 17 degree phase margin. Visualize the flat portion of feedback path #2 at about 30db. This is well below the intersection point and gives a nice round gain increase of 10x or 30 total. Estimate the line will cross the closed loop gain at about 200KHz.


Considering the inductor open and Cf shorted, AC gain will be roughly R_d/R_f . Put 3.01K and 20KHz (a decade below our estimated cross) in the R-C Pole Calculator. Enter 2.7nF for Cf.

We have good phase margin and an suggested maximum frequency of 178KHz. This suggestion is the lower of two criteria: The cross of the two feedback paths (the case here) or the frequency where loop gain is 20db (difference between open loop and closed loop gains).


V – I MAGNITUDE PLOT FOR STABILITY

 


V - I OPEN LOOP PHASE PLOT FOR STABILITY

 

V-I Phase Components for Stability

 

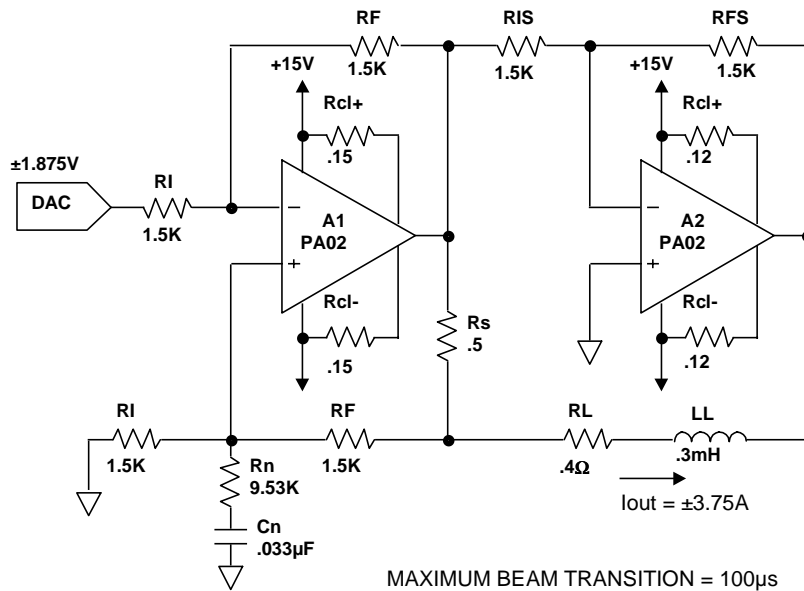ELECTRO-MAGNETIC DEFLECTION IMPROVED HOWLAND BRIDGE AMPLIFIER



VOLTAGE

$$V_{LL} = LL \frac{dip-p}{dt}$$

$$V_s = V_{LL} + V_{RL} + V_{R_s} + V_{sat}$$

Where: $V_{RL} = I_p R_L$
 $V_{R_s} = I_p R_s$

STEP 2: CURRENT From desired I_{out} , current must be 3.75A.

STEP 3: SPEED

A design rule of thumb for good performance is to select an amplifier with a minimum slew rate equal to 10 times faster than the desired current slew rate, faster will be better.

$$S.R. \text{ MIN} =$$


$$S.R. \text{ MIN} = \frac{V_s \text{ MIN}}{.1 dt} = 1.4V/\mu s$$

STEP 4: PA02 exceeds these requirements and has the best V_{sat} .

$$\frac{V_s \text{ MIN}}{(.1) dt}$$

$$\frac{14V}{(.1) (100\mu s)}$$

ELECTROSTATIC DEFLECTION AMPLIFIER

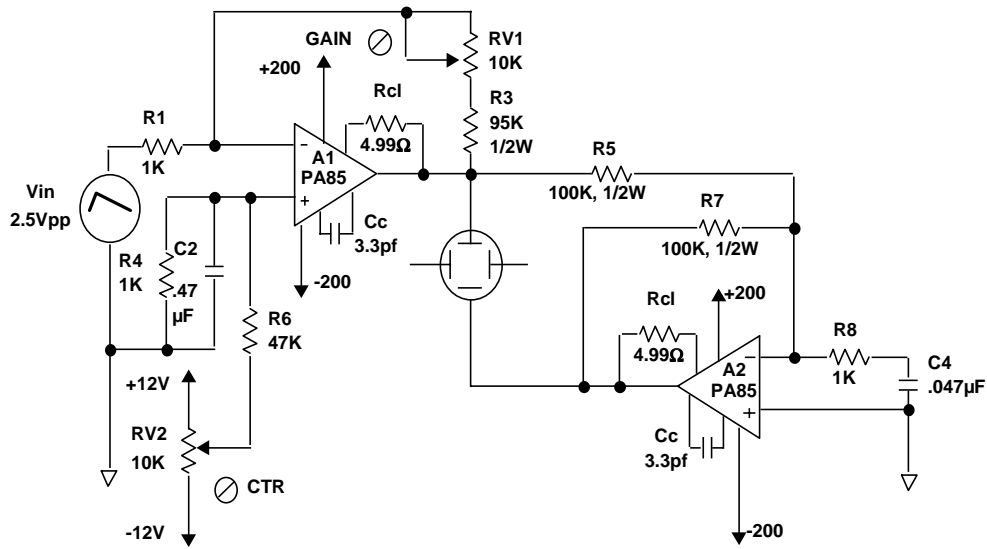


BALANCED TO MINIMIZE CRT DISTORTION

The PA85 was chosen for this application for its high voltage and high speed characteristics. Full bridge drive is utilized to provide a balanced drive to the CRT plate. Bridge drive is useful to reduce geometric distortion in electrostatic deflection applications.

A1 is the main amplifier operating at a gain of 100. This high gain permits minimal phase compensation for maximum speed performance.

Slave amplifier A2 is operated at a feedback factor of 1/2, that is an inverting unity gain. To get the same benefit of high speed that A1 enjoys due to the minimum compensation requirements, A2 is fooled into thinking it has a gain of 100 with the use of R8 and C4. This results in A2 having the same small signal bandwidth and high frequency gain as A1, which allows symmetrical bridge slew rates since A1 and A2 now use the same Cc compensation capacitor. This is the "Noise Gain Compensation" trick discussed earlier.

DYNAMIC FOCUSING

 

RAPID CORRECTION OF FOCUS FOR HIGH RESOLUTION DISPLAYS

In a flat screen display system the distance from the source of the beam to the screen changes as it deflects on the screen, from left to right, and from top to bottom. As a result of this a dynamic focus is required to keep the beam in focus, no matter where it is located on the screen.


A normal CRT screen does not have to overcome these distance differences, since the distance from the source of the beam and the screen are the same no matter where you are on the screen, by virtue of the curvature of the screen.

To achieve electrostatic dynamic focus requires an amplifier with high voltage and high slew rate, as it is important to rapidly change the focus to keep the beam focused, regardless of screen position. The 450V, 1000V/ μ s slew rate PA85 is the ideal choice.

X and Y location sweep information is summed and scaled to provide the proper focus bias to the focus electrode. A DC offset sets the focus at the center of the screen.


Don't forget the heatsinking on the PA85 as the high slew rate requires a high quiescent current which in combination with the high power supply voltage will result in 11.25W of quiescent power dissipation. A PA85 can cook, from a slew rate standpoint, and will literally cook without proper heatsinking!

PIEZO DRIVE APPLICATIONS

 

860 Vpp PIEZO DRIVE

SINGLE SUPPLY BRIDGE

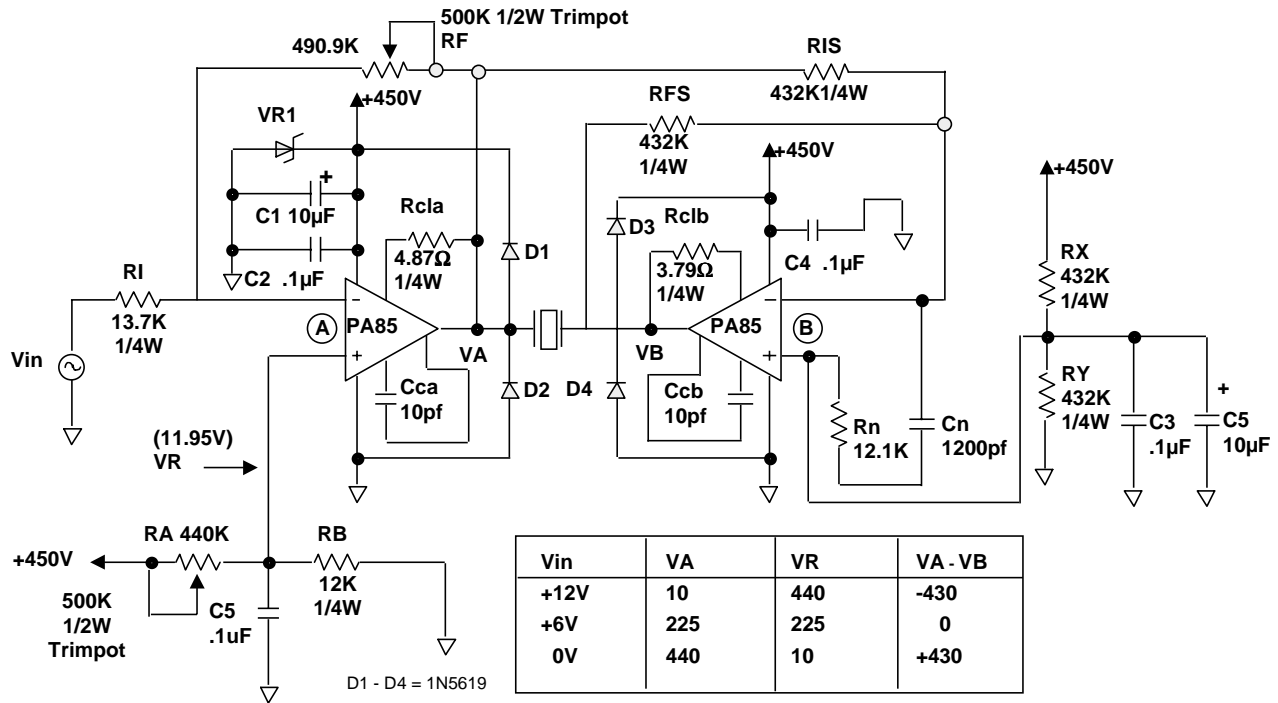

1. $V_{out} = V_A - V_B$

$$\begin{aligned} \text{Max } V_{out} &= V_s - V_{satA} - V_{satB} \\ &= 450V - 10V - 10V = 430V \end{aligned}$$

2. $\text{Gain} = \frac{V_{out\text{p-p}}}{V_{in\text{p-p}}} = \frac{(V_A - V_B)_{\text{p-p}}}{V_{in\text{p-p}}}$
 $860V_{\text{p-p}} / 12V_{\text{p-p}} = 71.67$

Gain = $2 R_F / R_I$ since we have a bridge configuration. That is the voltage gain across the load is twice that of the master amplifier, A, since +1V out of amplifier A yields -1V out of amplifier B, relative to the mid point power supply reference of +225V.

Therefore $R_F / R_I = 71.67 / 2 = 35.833$.

3. Offset:

$$V_A - V_B = V_s \left(2 \left(1 + \frac{R_F}{R_I} \right) \left(\frac{R_B}{R_A + R_B} \right) - 1 \right) - 2 \left(\frac{R_F}{R_I} \right) V_{in}$$


When $V_{in} = 0$ then $V_A - V_B = +430V$

Using $R_F / R_I = 35.833$ and solving above yields $R_A = 36.669R_B$

Choosing $R_B = 12K$ implies $R_A = 440K$.

4. Check for common mode voltage compliance: $11.95V > 10V$; OK.

+/- 1000V PIEZO BRIDGE

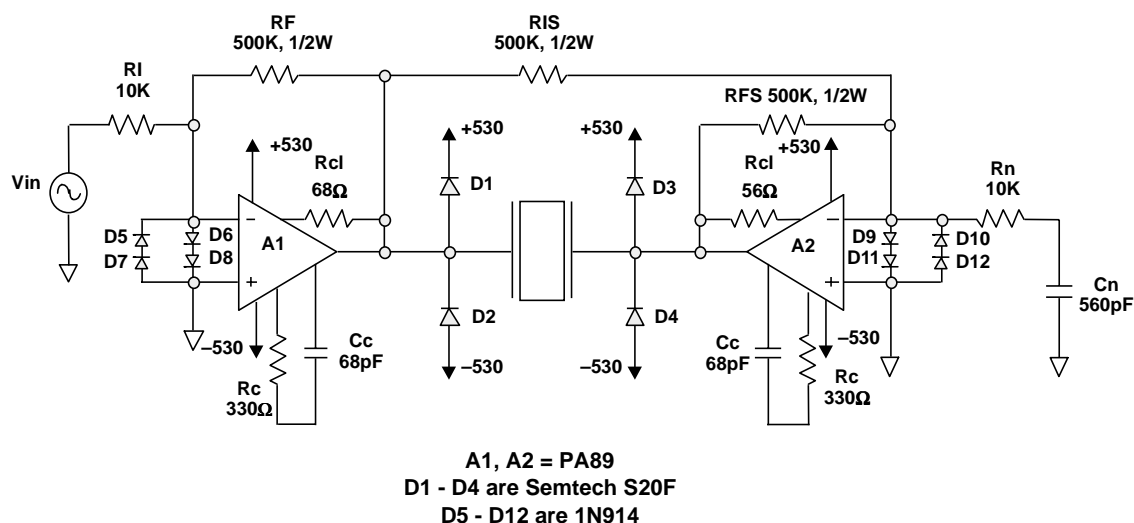

Piezo users appear to never have enough voltage. As soon as it was introduced the PA89 found its way into bridge circuits to drive piezos at +/-1100V and beyond.


In this application we use the dual supply bridge configuration to deliver up to almost twice the supply voltage of 530V across the load. A1 operates in a gain of 50 to translate the +/-10V input to +/-500V out of A1. A2 then inverts this output to add an additional +/-500V across the Piezo to yield a net +/-1000V.

A2 uses noise gain compensation to allow its V_o/V_{in} transfer function to remain at -1 , though its compensation capacitor C_c is set for a gain of 50. The noise gain will allow AC stability as well as a balanced bridge since both amplifiers are now compensated identically for the same slew rate.

Input protection diodes, output flyback diodes and proper component selection enhance reliability. Remember to select C_c capacitors with a voltage rating of at least 1100V, R_1 , R_F , R_{IS} , and R_{FS} with proper power dissipation and voltage coefficient of resistance, and D1 - D4 with a PIV of at least 1100V.

As a final note remember to check the amplifiers for AC stability due to capacitive loading depending upon the capacitance of the piezo being driven.

PA41 COMPOSITE PZT DRIVE

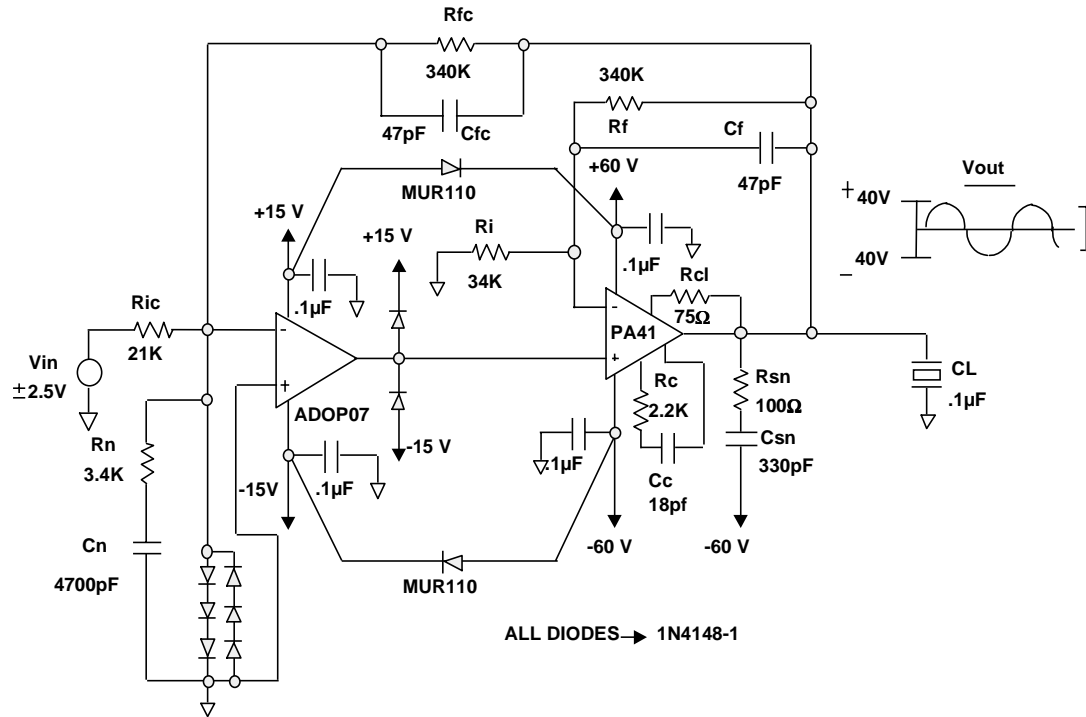


This circuit is included as an example in Power Design.xls. It is different from most power op amps in that current limit from positive side to negative side does not match well at all.

We will start by stabilizing the power stage, then the composite. Then we will examine current limit and frequency limitations imposed by this current limit.

1N4148 diodes on the input of the OP07 provide differential and common mode over voltage protection for transients through Cfc. Diodes on the output of the OP07 prevent over voltage transients that can occur through Cf, through the PA41 input protection diodes to the OP07 output through the PA41 internal input protection diodes.

Fast recovery diodes between pairs of supplies ensure that the PA41 input stage is protected from over voltage in the event the $\pm 15V$ supplies are up before the high voltage supplies.

POWER OP AMP MAGNITUDE PLOT

 


In any composite amplifier, make sure the power output stage is stable first. Any of the techniques we learned earlier can be used.

Composite Amplifier Set-up


| Composite Circuits | | | | 38 Goto Main Circuit | |
|-----------------------------|-------------|--------------------|---------------|-------------------------------|------------------|
| MODEL | OP07 | READ ME | | Estimated Closure Frequency = | 56.23413 KHz |
| Aol = | 135 db | Pole 1 = | 0.1 Hz | Suggested maximum bandwidth | 9.959633 KHz |
| Pole 2 = | 7.00E+05 Hz | Pole 3 = | 7.00E+06 Hz | Estimated Closure Rate = | 20.0 db/decade |
| Rin | 21 Kohms | Rn | 3.4 Kohms | Estimated Phase Margin = | 47.89155 Degrees |
| Rf | 340 Kohms | Cn | 4.7 nF | | |
| Cf | 47 pF | Using Look-Up data | | | |
| Notes: | | | | | |
| R-C Pole Calculator: | | | | | |
| | 340 Kohms | | 90 Kohms | | |
| | 8.7 KHz | | 0.43 nF | | |
| | 0.0538 nF | | 4.1125308 KHz | | |
| | | | | | |
| 1/Beta (DC) | | | 24.7 db | | |
| Noise Gain | | | 16.7 db | | |
| Pole Noise Gain | | | 9.9596332 KHz | | |
| Zero Noise Gain | | | 1.460962 KHz | | |
| Pole Cf/Rf | | | 9.9596335 KHz | | |
| Zero Rf/Cf | | | 1167.1742 KHz | | |
| | | | | | |
| Page Down for Plots. | | | | | |

| | |
|-----------------------------|------------------------------------|
| 30 Print Data, Bode & Phase | 31 Print Data, Bode, Phase & Parts |
|-----------------------------|------------------------------------|


Composite Amplifier Magnitude Plot

 

COMPOSITE AMPLIFIER OPEN LOOP PHASE PLOT

 


PA41 Negative Current Limit

 

If we can assume the PA41 never gets colder than 25°C, nominal current limit is 33mA. Again, thinking about 20% tolerance, we can count on 25mA output capability.


PA41 Positive Current Limit

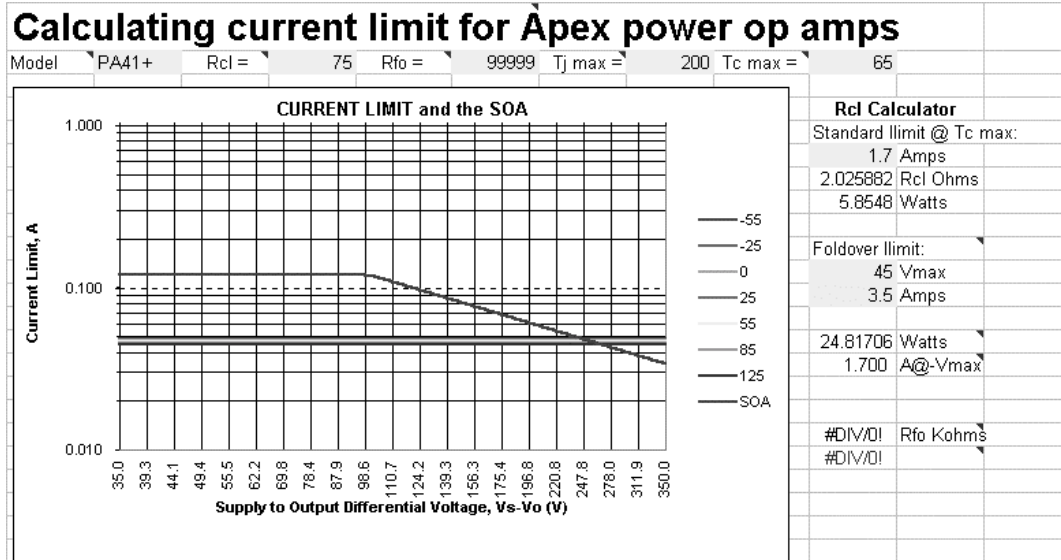

Here we see the difference in limiting on the positive side. While this will not have an effect on driving our normal load because we will calculate this based on the lower negative limit, we will want to know nominal positive limit is about 47mA if any fault conditions must be tolerated.

PA41 Power Question Setup

| Calculating Power Dissipation for Apex power op amps | | | | | | | | |
|------------------------------------------------------|-------------|-----------------------|-----------|-----|----------------|-----|----------|----|
| Model | PA41 | Note/PA46 | Ta max = | 30 | Tj max = | 150 | Tc max = | 85 |
| Power for Sine Wave Outputs | | Note/PA21,5,6 | | | | | | |
| Vs | 60 Volts | | | | | | | |
| Fmin | 0.01 KHz | | | | | | | |
| Fmax | 10 KHz | Is this a Bridge ckt? | | | | | | |
| Sig | 81 Units | No | | | | | | |
| Sig as ? | V p-p | | | | | | | |
| Res | 0 Ohms | | | | | | | |
| Cap | 0.1 uF | | | | | | | |
| Ind | 0 mH | | | | | | | |
| Rcap | 689 Ohms | | | | | | | |
| Rind | 0 Ohms | | | | | | | |
| Piq | 0.192 Watts | | | | | | | |
| Resonant Frequency = | | | 50329.212 | KHz | Max delta Tj = | | 120 | |
| At Fmax: | | | | | Max delta Tc = | | 55 | |
| Xc hi = | 159.15494 | Xc = | 159154.94 | | | | | |
| Xl hi = | 6.283E-06 | Xl = | 6.283E-09 | | | | | |

 


The amplifier selection, load and voltages have all been given. The only frequency that matters is the maximum (no current into a C load at DC). Our stability analysis suggested a maximum of about 10KHz (the Rf-Cf pole frequency).

Speed is Limited by Iout


| | At Fmin: | At Fmax: | | At Fmin: | At Fmax: | |
|------------------------------|-----------|-----------|-----------|------------------------|-----------|--------------|
| Z in Ohms | 159154.94 | 159.15 | | Maximum AC Pint | | |
| Phase angle | -90.00 | -90.00 | | 59.4 | 59.4 | Vpk |
| RMS Amperes | 0.0001799 | 0.1799368 | | 42.002143 | 42.002143 | Vrms |
| Peak Amperes | 0.0002545 | 0.254469 | | 0.0002639 | 0.2639072 | Arms |
| RMS Volts | 28.637825 | 28.637825 | | 0.0110847 | 11.08467 | Wrms |
| Peak Volts | 40.5 | 40.5 | | 6.966E-15 | 6.965E-09 | Wtrue |
| RMS Power | 0.005153 | 5.1529974 | | 0.0142557 | 14.255742 | Pin |
| Peak Power | 0.010306 | 10.305995 | | Minimum HS: | | 5.45 °C/W |
| Power factor | 0.000 | 0.000 | | Actual HS: | | 100 °C/W |
| Input power | 0.01 | 9.72 | | Results in Tjmax = | | 391.78 °C |
| True power | 0.00 | 0.00 | | Results in Tcmax = | | 327.35472 °C |
| Percent Efficiency = | 2.55 | 51.99 | | TOO *@&!# HOT!!!! | | |
| Vpk capability = | 48.99 | 42.64 | | CURRENT TOO HIGH! | | |
| Op amp internal dissipation: | | | | | | |
| Input power | 0.01 | 9.72 | | | | |
| Dissipation RMS | 0.01 | 9.72 | | | | |
| Dissipation Peak | 0.02 | 17.77 | | | | |
| Total in heatsink | 0.21 | 9.91 | | | | |
| WC watts & Rth | 9.9118238 | 6.5 | 5.4489283 | 5.5067527 | 5.4489283 | |

255mA would be required to drive the .1 μ F load at 10Kz! Notice the “CURRENT TOO HIGH!” flag at the lower right. This is based on data sheet maximum, not the current limit resistor used. Since this is 10x our capability, 1KHz will be the limit with a 75 Ω current limit resistor. When this is plugged in, we will find normal operation with no heatsink is possible. To analyze fault conditions, find the lowest impedance to be encountered, assume the current limit (47mA in this case) is driven into the load and calculate the output voltage. Subtract this from the supply voltage, compare to the SOA of the amplifier and calculate a larger heatsink as required.

AUDIO

 

WIDE BAND - LOW DISTORTION DESIGN

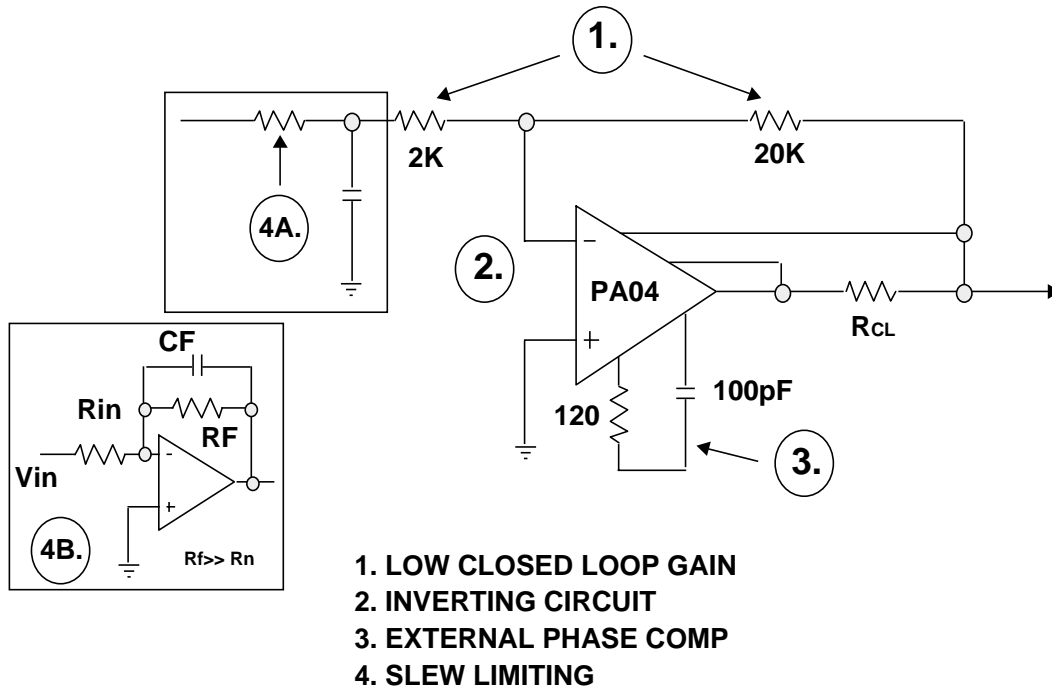

When audio or ATE applications demand the best in distortion and bandwidth, there are four basic rules to follow:

1. Low closed loop gain insures maximum reduction of distortion because of increased loop gain. However, the heavy negative feedback can cause transient response problems during rapid transitions (slew rate overload). Rule #4 will show how to solve the transient response problem.


2. The inverting configuration, by forcing both inputs to 0 (remember your basic op amp theory), eliminates common mode signals and the errors (read: nonlinearities) that they cause.

3. External phase compensation allows the designer to tailor the circuit to the minimum acceptable compensation. This increases high frequency loop gain to further reduce distortion, especially at high frequencies. Consider noise gain compensation to improve stability for low gain and small compensation capacitors.

4. Input slew rate limiting (4A) designed to keep input signal transitions within the slew rate limit of the amplifier will eliminate transient overload problems. 4B) You may use an integrator to accomplish this function, while R_F/R_1 pre-amplifies the input signal to accomodate a low powerstage gain. Then $C_f = V_{in}/R_{in} \cdot A_{cl} / SR$.

FOLD OVER CURRENT LIMITING FOR PA04

DOUBLES
|I_{cl}| AT V_o MAX

 

$$R_b = 270\Omega \quad R_f = \frac{V_s}{0.0025}$$


$$R_{cl} = \frac{0.7}{I_{cl}} \text{ for } 0 \text{ V}_{out}$$

The four wire current limit of PA04 is easily adapted to foldover current limiting with the addition of two external resistors.

This effectively doubles current available at full output swing compared to current available at 0V_{out}.

This provides an extra margin of safety in audio applications.

SA07 Aircraft Audio Amplifier

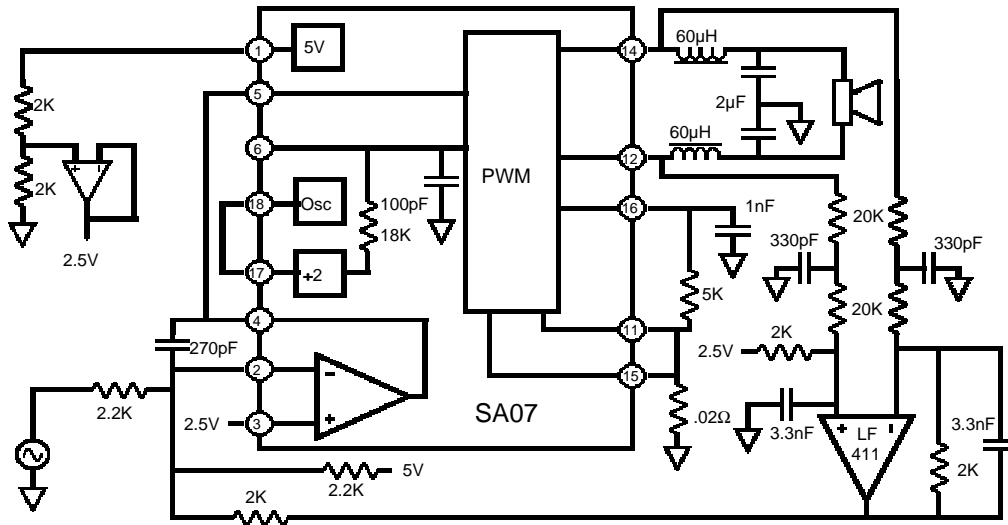


Weight is right at the top of the list of things airliners don't want. This is where the SA07 becomes the best choice for cabin audio. Heatsink concerns make PWM a natural choice and 500KHz switching cuts down the size of capacitors and even more important, the inductors. Not only is size and weight for a specific inductance reduced compared to a lower switching frequency, but having a wider band between switching and signal frequencies yields a filter with fewer components (a lower order filter). The filter is based on Power Design recommendations given 28V supply, 15KHz signal bandwidth and maximum ripple of 25mVpk.

The differential voltage amplifier has two poles at about 23.5KHz, a gain of 1/20 and the output is referenced to 2.5V. The integrator amplifier is also referenced to 2.5V and scaled to 1Vrms inputs which are ground referenced.

While not shown here, make no mistake about it, selection of bypass capacitors and careful layout make or break this application. In addition to 10µF per ampere low frequency bypass, use lower value ceramic chip capacitors to achieve low ESR well into the MHz region.

SA51 AUDIO AMPLIFIER

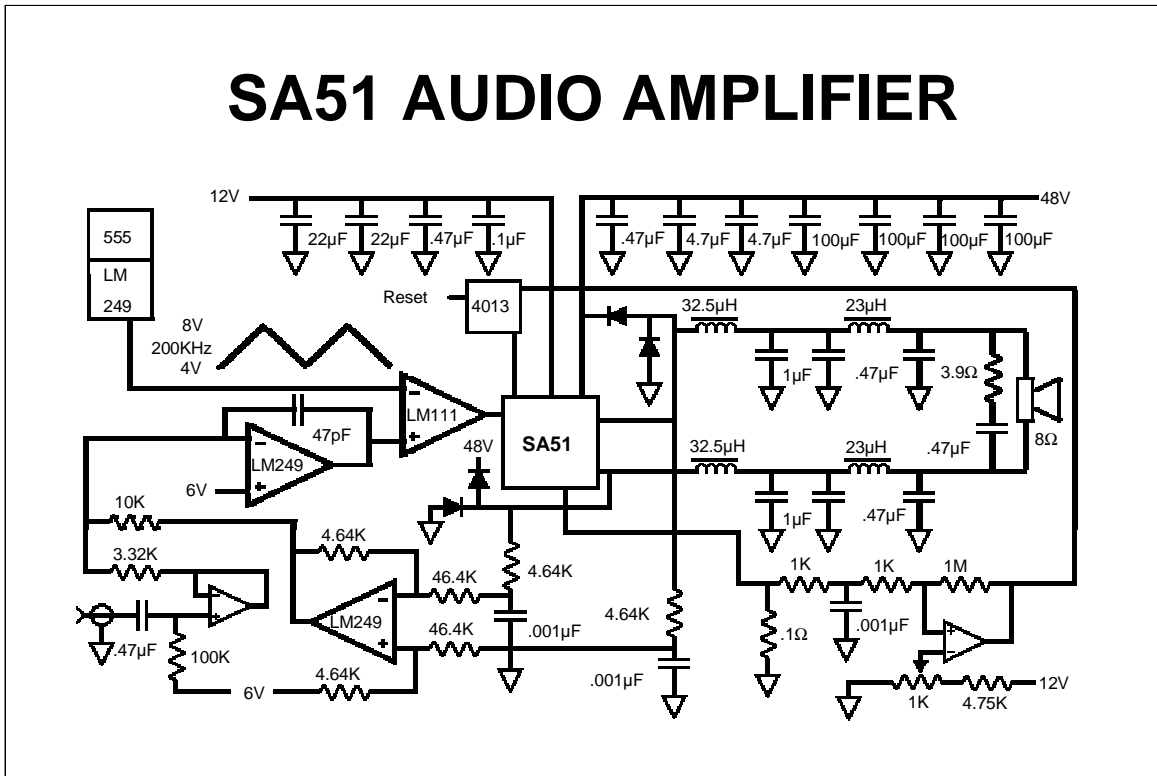

This class "D" audio amplifier is cost effective, cool running, good sounding and delivers up to 100W. Does any one know what this number would be if you bought the equipment as consumer audio gear?


Tested efficiency of this circuit was 80.6% at 60W output, meaning 14.4W wasted. A theoretical linear power stage would dissipate 72W delivering the same output from $\pm 48V$ supplies. Again, roughly that 5:1 heatsink savings of PWM over linear.

Operation of the overall circuit is similar to previous voltage output designs except there are more functions external to the PWM amplifier. The LM111 generates the PWM duty cycle based on the 6V referenced ramp and input signals. The SA51 converts this to power pulses. The filter removes most of the 200KHz switching frequency for the speaker. The differential amplifier also converts power pulses to an analog feedback signal. Over current is detected and latched to disable the power stage. Response time in the area of 5 μ s is required.

Capacitor arrays seen decoupling the supplies are not overkill. Larger values do a good job at lower frequency, lower values keep ESR low at the high end. Select capacitors specified for high current switching applications.

Diodes are schottky types for both high speed and low forward voltage drop.

SONAR TRANSDUCER DRIVE

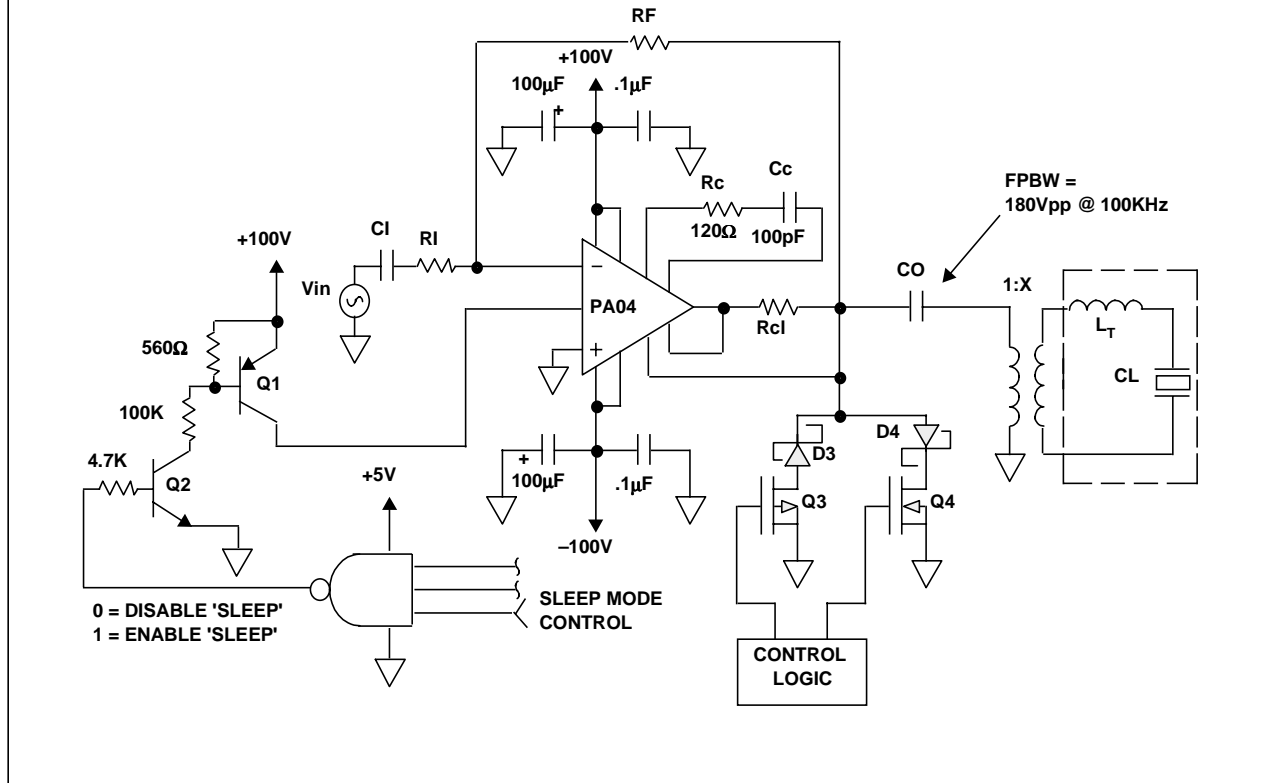

High current drive capability and wide power bandwidth make the PA04 ideally suited for sonar drive applications.

Often the amplifier is required to drive the primary of a transformer to step-up its output voltage to a desired high voltage for end drive to the sonar transducer. Because transformers do not work well when saturated it is essential to minimize DC current flow in them. AC coupling of the input signal and/or the output minimizes and/or eliminates the DC input offset voltage of the PA04 from becoming gained up by the gain of the amplifier, creating a large DC offset at the output.

Often times, either through the construction of the transformer or through an additional inductor, L_t , the sonar transducer, predominantly capacitive by nature, is tuned to look resistive for a narrow band of frequencies. This minimizes SOA stresses on the PA04. It is a good idea however to consider worst case capacitive loading reflected to the primary of the transformer onto the PA04 for AC stability considerations, should there be a possibility of non-resonant frequencies being applied to the sonar transducer drive circuit.

Another feature of the PA04 which is especially helpful in battery operations is its sleep mode function which can be used to turn the amplifier off during periods of non-use to minimize battery drain. Sleep mode quiescent current is only 5mA and the output is turned off into a high impedance state.

One caution when using sleep mode is to be aware of transients up to the supply rail that can occur during transitions into and out of sleep mode. There is no esoteric way to eliminate these internal to the op amp. If these transients would provide undesired transmissions, the problem can be cured through the use of two Schottky diodes (D3,D4) and two MOSFET switches (Q3,Q4). These components short the output of the PA04 to ground during the sleep mode transitions.

Timing logic going into sleep mode is to first command the input to zero, switch on Q3 and Q4 and then enable sleep mode. Coming out of sleep mode we would first ensure input signal is zero, ensure Q3 and Q4 are on, disable sleep mode, turn off Q3 and Q4, and finally begin transmitting with our input signal. Typical delay time to squelch the sleep mode transients is about 5-10 mS.

As a final note, to minimize SOA stresses it is advised to always start the input signal at zero crossing and exponentially ramp the amplitude if possible, since a transformer really doesn't look like a transformer until we have passed a few cycles of AC through it.

TOOLS AT YOUR COMMAND

- General Operating Considerations
- Subject Index
- Selector Guides
- Power Design.xls
- Evaluation Kits
- Sockets & Heatsinks
- Spice Files
- Data Sheets
- Application Notes
- Parameter Definitions and Test Methods
- Accessory Vendors
- Military Screening Flow
- Failure Analysis
- 800-546-2739

The Apex handbook is the world's most complete reference work when it comes to challenging power designs. Roughly a quarter of the book is application notes, a good source of "how to" and "how not to" tips and circuit ideas. Format is your choice; hard copy, CD-ROM or on line with all the latest and greatest.

Unless you're an old hand at power design, check out AN1, General Operating Considerations. It is the most important document in the entire book. While there is no substitute for *actually reading it*, at a very minimum, take note of the paragraph titles and look at the pictures.

In the back of the book is a Subject Index which may just point you to the specific information you need. Package drawings and marking information (Where's pin 1?) is also near the back of the catalog. You can also find many phone numbers, fax numbers and if you are inclined to visit Apex, a map.

Beat the Discrete Approach

- Time to market value?
 - Lost sales - engineering costs
- Value of 8 solder joints vs. 80?
 - Size, weight
 - Reliability
 - First pass yield, troubleshoot, rework, retest times
 - Field failure rate & serviceability
 - Logistics costs
 - Component spec, buying, stocking

Response to these design issue questions vary an amazing amount, both in time spent on the subject and in answers to specific items. Apex products are used in products where meeting the Christmas buying season is paramount, where cutting machine size by 2 doubles the value of the product and remotely located equipment where field failures would be a disaster.

This seminar has covered many of the technical issues involved with using hybrid power products but it remains your engineering challenge to integrate the various advantages into your business environment. Perhaps a few moments spent here will enhance value of your final product.



WEB:

<http://www.apexmicrotech.com>

AP NOTES, PRODUCT LITERATURE:

prodlit@apexmicrotech.com

ENGINEERING SUPPORT:

support@apexmicrotech.com

Blank

Blank

Thanks for attending/reading the Apex Technical Seminar!

Your comments would be appreciated:

What did you want to get from this seminar? _____

Did you get it? NO So-so YES _____

As a user of power components are you Novice Intermediate Expert

If you were giving or writing this seminar, how would you improve it?

DC Converters: _____

PWMs: _____

Op Amps: _____

Applications: _____

The book: _____

The slides: _____

The facilities: _____

The presentation: _____

In general: _____

Will you be considering using our product? Yes No _____

For: _____

Like to see any new products from Apex? _____

Critical parameters: _____

If you wish:

Name: _____

Company: _____